

THE No 1 UK MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

EPE EVERYDAY PRACTICAL ELECTRONICS

www.epemag.com

WIN A
MICROCHIP
Starter Kit
For Android

HIGH QUALITY STEREO DAC

- Accepts both optical and coaxial inputs
- Lets you use your DVD player to play CDs properly
- Eliminate poor sound quality, buzz and hum problems

OLD CASSETTE DECK + WOOD + VCR PARTS = LAND SPEED RECORD TOY CAR

Another five fun uses for salvaged parts

DIGITAL MEGOHM AND LEAKAGE CURRENT METER

An electronic megohm and leakage current meter,
for quick and easy testing of insulation in wiring

PLUS

TEACH-IN 2011 – PART 11

Summing up!



\$8.99US £4.25UK

SEPT 2011 PRINTED IN THE UK



World's Lowest Power Microcontrollers with USB OTG



Extend the battery life in your portable USB application using PIC® microcontrollers with integrated USB and XLP technology. Get the world's lowest power USB microcontrollers with the flexibility to communicate as an embedded host or device.

- Combine eXtreme Low Power with Full-Speed USB device, embedded host, dual role and On-The-Go
- Widely available through worldwide distribution channels
- Download FREE USB stacks and drivers including thumb drive support
 - Host, OTG and Device Stacks
 - Class Drivers (HID, Mass Storage, CDC Drivers)
 - Thumb Drive Support (Mass Storage Driver, SCSI Interface, File Management)

GET STARTED IN 3 EASY STEPS

1. Purchase a USB Starter Kit
2. Download Free USB Software
3. Order Free Samples

www.microchip.com/usb



Microchip USB Starter Kit

Family	Flash Program Memory (KB)	Pins	USB Type	Sleep Current (nA)	Sleep with Watchdog Timer (nA)	Sleep with Real Time Clock (nA)
PIC18F14K50	8-16	20	Device	24	450	790
PIC18F46J50	16-64	28-44	Device	13	813	813
PIC24FJ64GB004	32-64	28-44	OTG, Dual Role, Embedded Host, Device	20	220	520

microchip
DIRECT
www.microchipdirect.com

www.microchip.com/usb

MICROCHIP

ISSN 0262 3617

- PROJECTS • THEORY •
- NEWS • COMMENT •
- POPULAR FEATURES •

VOL. 40. No 9 September 2011

EPE EVERYDAY PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS TODAY INTERNATIONAL

www.epemag.com



© Wimborne Publishing Ltd 2011. Copyright in all drawings, photographs and articles published in *EVERYDAY PRACTICAL ELECTRONICS* is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our October 2011 issue will be published on Thursday 8 September 2011, see page 80 for details.

Everyday Practical Electronics, September 2011

Projects and Circuits

- BUILD A HIGH-QUALITY STEREO DAC FOR SUPERB SOUND FROM YOUR DVD PLAYER – PART 1** By Nicholas Vinen **10**
Versatile design accepts both optical and coaxial inputs
- DIGITAL MEGOHM AND LEAKAGE CURRENT METER** by Jim Rowe **22**
An electronic megohm and leakage current meter, for easy testing of insulation
- DELUXE 3-CHANNEL UHF ROLLING CODE REMOTE CONTROL – PART 2** by John Clarke **32**
Putting it all together and getting the two parts talking to each other – securely!
- AUTO-DIM ADD-ON FOR THE 6-DIGIT GPS CLOCK** by Jim Rowe **39**
A low-cost add-on for the Digital GPS Time Display published in May/June 2011
- INGENUITY UNLIMITED** **68**
Low-Battery Indicator – Go/No-go

Series and Features

- TECHNO TALK** by Mark Nelson **38**
Edible computing
- RECYCLE IT!** by Julian Edgar **43**
Six fun projects from salvaged parts
- TEACH-IN 2011** by Mike and Richard Tooley **46**
Part 11: Summing it all up
- CIRCUIT SURGERY** by Ian Bell **58**
Attending to noise and stability
- MAX'S COOL BEANS** by Max The Magnificent **62**
Acting mentor... Endless patience... Any ideas?
- PRACTICALLY SPEAKING** by Robert Penfold **64**
Sourcing components
- NET WORK** by Alan Winstanley **72**
Quick off the mark... Keep taking the tablets... Chrome-plated

Regulars and Services

- EDITORIAL** **7**
Ingenuity Unlimited – Pico prize winners
- NEWS** – Barry Fox highlights technology's leading edge **8**
Plus everyday news from the world of electronics
- MICROCHIP READER OFFER** **42**
EPE Exclusive – Win a Microchip Accessory Development Starter Kit For Android
- EPE BACK ISSUES** Did you miss these? **57**
- SUBSCRIBE TO EPE** and save money **63**
- CD-ROMS FOR ELECTRONICS** **69**
A wide range of CD-ROMs for hobbyists, students and engineers
- PIC RESOURCES CD-ROM** **74**
EPE PIC Tutorial V2, plus PIC Toolkit Mk3 and a selection of PIC-related articles
- DIRECT BOOK SERVICE** **75**
A wide range of technical books available by mail order, plus more CD-ROMs
- EPE PCB SERVICE** **78**
PCBs for EPE projects
- ADVERTISERS INDEX** **79**

Readers' Services • Editorial and Advertisement Departments **7**


PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

Programmer Accessories:

40-pin Wide ZIF socket (ZIF40W) £14.95
18Vdc Power supply (PSU121) £24.95
Leads: Parallel (LDC136) £3.95 / Serial (LDC441) £3.95 / USB (LDC644) £2.95


USB & Serial Port PIC Programmer



USB/Serial connection. Header cable for ICSP. Free Windows XP software. See website for PICs supported. ZIF Socket and USB lead extra. 18Vdc.

Kit Order Code: 3149EKT - £49.95
Assembled Order Code: AS3149E - £59.95
Assembled with ZIF socket Order Code: AS3149EZIF - £74.95


USB Flash/OTP PIC Programmer

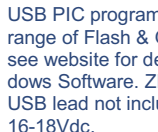

USB PIC programmer for a wide range of Flash & OTP devices—see website for details. Free Windows Software. ZIF Socket and USB lead not included. Supply: 16-18Vdc.

Assembled Order Code: AS3150 - £49.95
Assembled with ZIF socket Order Code: AS3150ZIF - £64.95


ATMEL 89xxxx Programmer



Uses serial port and any standard terminal comms program. 4 LED's display the status. ZIF sockets not included. Supply: 16Vdc.

Kit Order Code: 3123KT - £28.95
Assembled Order Code: AS3123 - £39.95

Introduction to PIC Programming

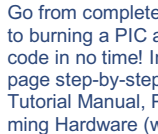


Go from complete beginner to burning a PIC and writing code in no time! Includes 49 page step-by-step PDF Tutorial Manual, Programming Hardware (with LED test section), Win 3.11—XP Programming Software (Program, Read, Verify & Erase), and 1rewritable PIC16F84A that you can use with different code (4 detailed examples provided for you to learn from). PC parallel port. Kit Order Code: 3081KT - £16.95
Assembled Order Code: AS3081 - £24.95

PIC Programmer Board



Low cost PIC programmer board supporting a wide range of Microchip® PIC™ microcontrollers. Requires PC serial port. Windows interface supplied. Kit Order Code: K8076KT - £39.95

PIC Programmer & Experimenter Board

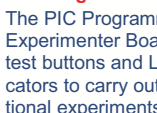

The PIC Programmer & Experimenter Board with test buttons and LED indicators to carry out educational experiments, such as the supplied programming examples. Includes a 16F627 Flash Microcontroller that can be reprogrammed up to 1000 times for experimenting at will. Software to compile and program your source code is included. Kit Order Code: K8048KT - £39.95

Assembled Order Code: VM111 - £59.95

Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. 12Vdc PSU for all units: Order Code PSU303 £9.95


USB Experiment Interface Board



5 digital input channels and 8 digital output channels plus two analogue inputs and two analogue outputs with 8 bit resolution.

Kit Order Code: K8055KT - £39.95
Assembled Order Code: VM110 - £64.95

Rolling Code 4-Channel UHF Remote

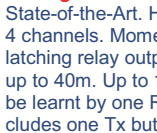


State-of-the-Art. High security. 4 channels. Momentary or latching relay output. Range up to 40m. Up to 15 Tx's can be learnt by one Rx (kit includes one Tx but more available separately). 4 indicator LED's. Rx: PCB 77x85mm, 12Vdc/6mA (standby). Two & Ten Channel versions also available. Kit Order Code: 3180KT - £54.95
Assembled Order Code: AS3180 - £64.95

Computer Temperature Data Logger



Serial port 4-channel temperature logger. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of free software applications for storing/using data. PCB just 45x45mm. Powered by PC. Includes one DS1820 sensor. Kit Order Code: 3145KT - £24.95
Assembled Order Code: AS3145 - £31.95
Additional DS1820 Sensors - £4.95 each

Remote Control Via GSM Mobile Phone

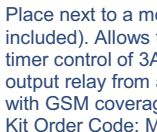

Place next to a mobile phone (not included). Allows toggle or auto-timer control of 3A mains rated output relay from any location with GSM coverage. Kit Order Code: MK160KT - £14.95

Most items are available in kit form (KT suffix) or pre-assembled and ready for use (AS prefix).

4-Ch DTMF Telephone Relay Switcher




Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, Rings to Answer, Auto Hang-up and Lockout. Includes plastic case. 130 x 110 x 30mm. Power: 12Vdc.

Kit Order Code: 3140KT - £79.95

Assembled Order Code: AS3140 - £94.95

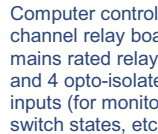8-Ch Serial Port Isolated I/O Relay Module




Computer controlled 8 channel relay board. 5A mains rated relay outputs and 4 opto-isolated digital inputs (for monitoring switch states, etc). Useful in a variety of control and sensing applications. Programmed via serial port (use our new Windows interface, terminal emulator or batch files). Serial cable can be up to 35m long. Includes plastic case 130x100x30mm. Power: 12Vdc/500mA.

Kit Order Code: 3108KT - £74.95

Assembled Order Code: AS3108 - £89.95

Infrared RC 12-Channel Relay Board



Control 12 onboard relays with included infrared remote control unit. Toggle or momentary. 15m+ range. 112 x 122mm. Supply: 12Vdc/0.5A

Kit Order Code: 3142KT - £64.95

Assembled Order Code: AS3142 - £74.95

Audio DTMF Decoder and Display



Detect DTMF tones from tape recorders, receivers, two-way radios, etc using the built-in mic or direct from the phone line. Characters are displayed on a 16 character display as they are received and up to 32 numbers can be displayed by scrolling the display. All data written to the LCD is also sent to a serial output for connection to a computer. Supply: 9-12V DC (Order Code PSU303). Main PCB: 55x95mm.

Kit Order Code: 3153KT - £37.95

Assembled Order Code: AS3153 - £49.95

3x5Amp RGB LED Controller with RS232



3 independent high power channels. Preprogrammed or user-editable light sequences. Standalone option and 2-wire serial interface for microcontroller or PC communication with simple command set. Suitable for common anode RGB LED strips, LEDs and incandescent bulbs. 56 x 39 x 20mm. 12A total max. Supply: 12Vdc.

Kit Order Code: 3191KT - £27.95

Assembled Order Code: AS3191 - £37.95

Copyright © 2010, Wimborne Publishing Ltd
(Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU, UK)
and TechBites Interactive Inc.,
(PO Box 857, Madison, Alabama 35758, USA)
All rights reserved.

WARNING!

The materials and works contained within *EPE Online* — which are made available by Wimborne Publishing Ltd and TechBites Interactive Inc — are copyrighted. You are permitted to make a backup copy of the downloaded file and one (1) hard copy of such materials and works for your personal use.

International copyright laws, however, prohibit any further copying or reproduction of such materials and works, or any republication of any kind. TechBites Interactive Inc and Wimborne Publishing Ltd have used their best efforts in preparing these materials and works. However, TechBites Interactive Inc and Wimborne Publishing Ltd make no warranties of any kind, expressed or implied, with regard to the documentation or data contained herein, and specifically disclaim, without limitation, any implied warranties of merchantability and fitness for a particular purpose. Because of possible variances in the quality and condition of materials and workmanship used by readers, *EPE Online*, its publishers and agents disclaim any responsibility for the safe and proper functioning of reader-constructed projects based on or from information published in these materials and works. In no event shall TechBites Interactive Inc or Wimborne Publishing Ltd be responsible or liable for any loss of profit or any other commercial damages, including but not limited to special, incidental, consequential, or any other damages in connection with or arising out of furnishing, performance, or use of these materials and works.

Hot New Products!

Here are a few of the most recent products added to our range. See website or join our email Newsletter for all the latest news.

4-Channel Serial Port Temperature Monitor & Controller Relay Board

4 channel computer serial port temperature monitor and relay controller with four inputs for Dallas DS18S20 or DS18B20 digital thermometer sensors (£3.95 each). Four 5A rated relay channels provide output control. Relays are independent of sensor channels, allowing flexibility to setup the linkage in any way you choose. Commands for reading temperature and relay control sent via the RS232 interface using simple text strings. Control using a simple terminal / comms program (Windows HyperTerminal) or our free Windows application software. Kit Order Code: 3190KT - **£84.95**
Assembled Order Code: AS3190 - **£99.95**




40 Second Message Recorder

Feature packed non-volatile 40 second multi-message sound recorder module using a high quality Winbond sound recorder IC. Stand-alone operation using just six onboard buttons or use onboard SPI interface. Record using built-in microphone or external line in. 8-24 Vdc operation. Just change one resistor for different recording duration/sound quality. sampling frequency 4-12 kHz. Kit Order Code: 3188KT - **£29.95**
Assembled Order Code: AS3188 - **£37.95**
120 second version also available



Bipolar Stepper Motor Chopper Driver

Get better performance from your stepper motors with this dual full bridge motor driver based on SGS Thompson chips L297 & L298. Motor current for each phase set using on-board potentiometer. Rated to handle motor winding currents up to 2 Amps per phase. Operates on 9-36Vdc supply voltage. Provides all basic motor controls including full or half stepping of bipolar steppers and direction control. Allows multiple driver synchronisation. Perfect for desktop CNC applications. Kit Order Code: 3187KT - **£39.95**
Assembled Order Code: AS3187 - **£49.95**

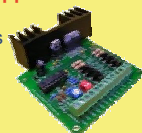

Video Signal Cleaner

Digitally cleans the video signal and removes unwanted distortion in video signal. In addition it stabilises picture quality and luminance fluctuations. You will also benefit from improved picture quality on LCD monitors or projectors. Kit Order Code: K8036KT - **£32.95**
Assembled Order Code: VM106 - **£49.95**



Most items are available in kit form (KT suffix) or assembled and ready for use (AS prefix).

Motor Speed Controllers

Here are just a few of our controller and driver modules for AC, DC, Unipolar/Bipolar stepper motors and servo motors. See website for full details.

DC Motor Speed Controller (100V/7.5A)



Control the speed of almost any common DC motor rated up to 100V/7.5A. Pulse width modulation output for maximum motor torque at all speeds. Supply: 5-15Vdc. Box supplied. Dimensions (mm): 60Wx100Lx60H. Kit Order Code: 3067KT - **£19.95**
Assembled Order Code: AS3067 - **£27.95**

Computer Controlled / Standalone Unipolar Stepper Motor Driver

Drives any 5-35Vdc 5, 6 or 8-lead unipolar stepper motor rated up to 6 Amps. Provides speed and direction control. Operates in stand-alone or PC-controlled mode for CNC use. Connect up to six 3179 driver boards to a single parallel port. Board supply: 9Vdc. PCB: 80x50mm. Kit Order Code: 3179KT - **£16.95**
Assembled Order Code: AS3179 - **£23.95**



Computer Controlled Bi-Polar Stepper Motor Driver

Drive any 5-50Vdc, 5 Amp bi-polar stepper motor using externally supplied 5V levels for STEP and DIRECTION control. Opto-isolated inputs make it ideal for CNC applications using a PC running suitable software. Board supply: 8-30Vdc. PCB: 75x85mm. Kit Order Code: 3158KT - **£24.95**
Assembled Order Code: AS3158 - **£34.95**



Bidirectional DC Motor Speed Controller

Control the speed of most common DC motors (rated up to 32Vdc/10A) in both the forward and reverse direction. The range of control is from fully OFF to fully ON in both directions. The direction and speed are controlled using a single potentiometer. Screw terminal block for connections. Kit Order Code: 3166v2KT - **£23.95**
Assembled Order Code: AS3166v2 - **£33.95**



AC Motor Speed Controller (600W)

Reliable and simple to install project that allows you to adjust the speed of an electric drill or 230V AC single phase induction motor rated up to 600 Watts. Simply turn the potentiometer to adjust the motors RPM. PCB: 48x65mm. Not suitable for use with brushless AC motors. Kit Order Code: 1074KT - **£15.95**
Assembled Order Code: AS1074 - **£23.95**



See www.quasarelectronics.com for lots more motor controllers



QUASAR
electronics
The Electronic Kit Specialists Since 1993

Electronic Project Labs

Great introduction to the world of electronics. Ideal gift for budding electronics expert!

500-in-1 Electronic Project Lab

Top of the range. Complete self-contained electronics course. Takes you from beginner to 'A' Level standard and beyond! Contains all the hardware and manuals to assemble 500 projects. You get 3 comprehensive course books (total 368 pages) - *Hardware Entry Course*, *Hardware Advanced Course* and a microprocessor based *Software Programming Course*. Each book has individual circuit explanations, schematic and connection diagrams. Suitable for age 12+. Order Code EPL500 - **£199.95**
Also available: 30-in-1 **£19.95**, 50-in-1 **£29.95**, 75-in-1 **£39.95** 130-in-1 **£49.95** & 300-in-1 **£89.95** (see website for details)



Tools & Test Equipment

We stock an extensive range of soldering tools, test equipment, power supplies, inverters & much more - please visit website to see our full range of products.

Advanced Personal Scope 2 x 240MS/s

Features 2 input channels - high contrast LCD with white backlight - full auto set-up for volt/div and time/div - recorder roll mode, up to 170h per screen - trigger mode: run - normal - once - roll ... - adjustable trigger level and slope and much more. Order Code: APS230 - ~~£499.95~~ **£399.95**



Personal Scope 10MS/s

The Personal Scope is not a graphical multimeter but a complete portable oscilloscope at the size and the cost of a good multimeter. Its high sensitivity - down to 0.1mV/div - and extended scope functions make this unit ideal for hobby, service, automotive and development purposes. Because of its exceptional value for money, the Personal Scope is well suited for educational use. Order Code: HPS10 - ~~£189.95~~ **£159.95**



See website for more super deals!



www.quasarelectronics.com

Secure Online Ordering Facilities • Full Product Listing, Descriptions & Photos • Kit Documentation & Software Downloads

CELEBRATING
30
YEARS
OF SERVICE

Everyday Practical Electronics

FEATURED KITS SEPTEMBER 2011

Everyday Practical Electronics Magazine has been publishing a series of popular kits by the acclaimed Silicon Chip Magazine Australia. These projects are 'bullet proof' and already tested Down Under. All Jaycar kits are supplied with specified board components, quality fibreglass tinned PCBs and have clear English instructions. Watch this space for future featured kits.

Studio 350 - High Power Amplifier

KC-5372 £63.50 plus postage & packing

The studio 350 power amplifier will deliver a whopping 350VRMS into 4 ohms or 200VRMS into 8 ohms. It offers real grunt using a high power MJ21193/4 transistor and is super quiet with a very low signal to noise ratio and harmonic distortion. This kit is supplied in short form with PCB and electronic components. Kit requires heatsink and (+/-) 70V power supply as described in instructions. See website for more specifications.

Featured in EPE October/ November 2006




45 Second Voice Recorder Module

KC-5454 £16.00 plus postage & packing

This kit has been improved and can now be set up easily to record two, four or eight different messages for random-access playback or a single message for 'tape mode' playback. Also, it now provides cleaner and glitch-free line-level audio output suitable for feeding an amplifier or PA system. It can be powered from any source of 9-14V DC.

- Supplied with silk screened and solder masked PCB and all electronic components.
- PCB: 120 x 58mm

Featured in EPE February 2011

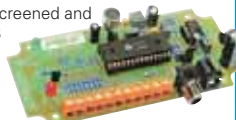

AV Booster Kit

KC-5350 £36.25 plus postage & packing

This kit will boost your video and audio signals preserving them for the highest quality transmission to your projector or large screen TV. It boosts composite, S-Video, and stereo audio signals. Kit includes case, PCB, silkscreened punched panels and all electronic components.

- 9VAC @ 150mA required - use our plugpack
- MP-3027 £9.00

Featured in EPE March 2006



Low Cost Programmable Interval Timer

KC-5464 £12.75 plus postage & packing

Here's a new and completely updated version of the very popular low cost 12VDC electronic timer. It is link programmed for either a single ON, or continuous ON/OFF cycling for up to 48 on/off time periods. Selectable periods are from 1 to 80 seconds, minutes, or hours and it can be restarted at any time. Kit includes PCB and all specified electronic components.

- PCB Dimensions: 102 x 42mm
- Featured in EPE August 2010



Tempmaster Fridge Controller Mk II

KC-5476 £12.00 plus postage & packing

Turn an old chest freezer into an energy-efficient fridge or beer keg fridge. Or convert a standard fridge into a wine cooler. These are just two of the jobs this low-cost and easy-to-build electronic thermostat kit can do without the need to modify internal wiring! Used also to control 12V fridges or freezers, as well as heaters in hatcheries and fish tanks. Short-form kit contains PCB, sensor and all specified components. You'll need to add your own 240V GPO, switched IEC socket and case.

- PCB Dimensions: 68 x 67mm
- Featured in EPE February 2011



UHF Remote Controlled Mains Switch

KC-5462 £36.25 plus postage & packing

This UHF system will operate up to 200m and is perfect for remote power control systems etc. The switch can be activated using the included hand held controller.

- Kit supplied with case, screen printed PCB, RF modules and all electronic components
- Featured in EPE January 2010



Hand held remote control!

240V 10A Deluxe Motor Speed Controller Kit

KC-5478 £36.25 plus postage & packing

The deluxe motor speed controller kit allows the speed of a 240VAC motor to be controlled smoothly from near zero to full speed. The advanced design provides improved speed regulation & low speed operation. Also features soft-start, interferences suppression, fuse protection and over-current protection. Kit supplied with all parts including pre-cut metal case.

Note: Requires UK mains socket or adaptor
Featured in EPE May 2011



3V to 9V DC to DC Converter Kit

KC-5391 £6.00 plus postage & packing

This great little converter allows you to use regular Ni-Cd or Ni-MH 1.2V cells, or alkaline 1.5V cells for 9V applications. Using low cost, high capacity rechargeable cells, the kit will pay for itself in no-time! You can use any 1.2 - 1.5V cells you desire. Imagine the extra capacity you would have using two 9000mAh D cells in replacement of a low capacity 9V cell. Kit supplied with PCB and all electronic components.

- PCB: 59 x 29mm
- Featured in EPE June 2007



Programmable High Energy Ignition Kit

KC-5442 £34.50 plus postage & packing

This advanced and versatile ignition system is suited for both two & four stroke engines. Used to modify the factory ignition timing or as the basis for a stand-alone ignition system with variable ignition timing, electronic coil control and anti-knock sensing (available separately).

- Timing retard & advance over a wide range
- Suitable for single coil systems
- Dwell adjustment
- Single or dual mapping ranges
- Max & min RPM adjustment
- Kit includes PCB with overlay, programmed micro, all electronic components and die cast box

Also available to suit:
Ignition Coil Driver Kit KC-5443 £17.25
Knock Sensor Kit KC-5444 £7.00
Featured in EPE November 2009



SFX Kits

Theremin Synthesiser Kit MkII KC-5475 £27.25 plus postage & packing

The ever-popular Theremin is better than ever! From piercing shrieks to menacing growls, create your own eerie science fiction sound effects by simply moving your hand near the antenna. It's now easier to build with PCB-mounted switches and pots to reduce wiring to just the hand plate, speaker and antenna and has the addition of a skew control to vary the audio tone from distorted to clean.

- Complete kit contains PCB with overlay, pre-machined case and all specified components
- PCB: 85 x 145mm

Featured in EPE March 2011



Starship Enterprise Door Sound Emulator KC-5423 £14.50 plus postage & packing

This easy to build kit emulates the unique sound of a cabin door opening or closing on the Starship Enterprise. The sound can be triggered by switch contacts or even fitted to automatic doors.

- Kit supplied with PCB with overlay, speaker, case and all specified components
 - 9 - 12VDC regulated
- Featured in EPE June 2008



Improved Low Voltage Adaptor

KC-5463 £6.75 plus postage & packing

This handy regulator will let you run a variety of devices such as CD, DVD or MP3 players, digital cameras or even powered speakers from the power supply inside your PC. This unit can supply either 3V, 5V, 6V, 9V, 12V or 15V from a higher input voltage at up to four amps (with a suitable heatsink). Kit includes screen printed PCB and all specified components.

Note: To ensure trouble free 4 amp output, a heatsink with a thermal resistance of 1.4 degrees C per watt, and an input voltage 3VDC above the output voltage is required.

- PCB Dimensions: 108 x 37mm
- Featured in EPE November 2007



Jaycar
Electronics

Freecall order: 0800 032 7241

HOT Selling

Kits for Electronic Enthusiasts

KIT OF THE MONTH

12/24VDC 20A Motor Speed Controller Kit KC-5502 £14.50 plus postage & packing

Control the speed of 12 or 24VDC motors from zero to full power, up to 20A. Features optional soft start, adjustable pulse frequency to reduce motor noise, and low battery protection. The speed is set using the onboard trimpot, or by using an external potentiometer (available separately, use RP-3510 £0.98).

- Kit supplied with PCB and all onboard electronic components
- Suitable enclosure UB3 case, HB-6013 £1.50



NEW 2011

SECURITY KITS

UHF Rolling Code Remote Switch Kit KC-5483 £36.25 plus postage & packing

High-security 3-channel remote control that can be used for keyless entry into residential or commercial premises or for controlling garage doors and lights. Features rolling code/code hopping, the access codes can't be intercepted and decoded by undesirables. The transmitter kit includes a three button key fob case and runs on a 12V remote control battery. The receiver is a short-form kit without case so you can mount it in the location or enclosure of your choice.

- Receiver 12VDC @ 150mA (1A for door strike use)
- PCB: Transmitter: 34 x 56mm
- Receiver: 110 x 141mm

Also available to suit:
Additional Transmitter Kit
KC-5484 £14.50

Rolling Code Infrared Keyless Entry System KC-5458 £23.75 plus postage & packing

This keyless entry system features two independent door strike outputs and will recognise up to 16 separate key fobs. The system keeps the coded key fobs synchronised to the receiver and compensates for random button presses while the fobs are out of range. Supplied with solder masked and silk screen printed PCB, two programmed micros, battery and all electronic components.

- Receiver requires a 12VDC 1.5A power supply
- Some SMD soldering is required
- PCB: 61 x 122mm



MORE INFO AVAILABLE ONLINE

Don't just sit there BUILD SOMETHING!

Speedo Corrector MkII Kit

KC-5435 £20.00 plus postage & packing

When you modify your gearbox, diff ratio or change to a large circumference tyre, it may result in an inaccurate speedometer. This kit alters the speedometer signal up or down from 0% to 99% of the original signal. With this improved model, the input setup selection can be automatically selected and it also features an LED indicator to show when the input signal is being received. Kit supplied with PCB with overlay and all electronic components.

- PCB: 105 x 61mm
- Recommended box UB5 use HB-6013 £1.50



Universal Voltage Switch

KC-5377 £12.00 plus postage & packing

This is a universal module which can be adapted to suit a range of different applications. It will trip a relay when a preset voltage is reached. It can be configured to trip with a rising or falling voltage, so it is suitable for a wide variety of voltage outputting devices. For example throttle position sensor, air flow sensor, EGO sensor. You could even use it to trigger an extra fuel pump under high boost, anti-lag wastegate shutoff, and much more. Kit supplied with PCB, and all electronic components.

- PCB: 105 x 60mm



Universal Power Supply Regulator

KC-5501 £5.50 plus postage & packing

This is an upgraded version of the original universal power supply kit published in August 1988. One small board and a handful of parts will allow you to create either a regulated $\pm 15V$ rail or $\pm 15VDC$ single voltage from a single winding or centre tap transformer (not included). See website for more details.

- Includes all PCB and components for board, transformer not included
- PCB: 72(L) x 30(W)mm



NEW 2011

Ultrasonic Antifouling for Boats

KC-5498 £90.50 plus postage & packing

Marine growth electronic antifouling systems can cost thousands. This project uses the same ultrasonic waveforms and virtually identical ultrasonic transducers mounted in sturdy polyurethane housings. By building yourself (which includes some potting) you save a fortune! Standard unit consists of control electronic kit and case, ultrasonic transducer, potting and gluing components and housings. The single transducer design of this kit is suitable for boats up to 10m (32ft); boats longer than about 14m will need two transducers and drivers. Basically all parts supplied in the project kit including wiring. (Price includes epoxies).

- 12VDC
- Suitable for power or sail
- Could be powered by a solar panel/wind generator
- PCB: 78 x 104mm



Hundreds Sold!

"Minivox" Voice Operated Relay

KC-5172 £6.00 plus postage & packing

Voice operated relays are used for 'hands free' radio communications and some PA applications etc. Instead of pushing a button, this device is activated by the sound of a voice. This tiny kit fits in the tightest spaces and has almost no turn-on delay. 12VDC @ 35mA required. Kit is supplied with PCB electret mic, and all specified components.

- PCB: 47 x 44mm



An excellent way for new comers to dip their toes into the wonders of electronics!

SHORT CIRCUITS - VOLUME 1

This volume will teach you everything you need to get started in electronics and is suitable for ages 8+. We give you the option of buying the book on its own, or together with the accompanying kit that contains the components for each of the 20-odd projects described in the book. Some of the exciting projects include a Police Siren, Electronic Organ, Sound Effects Unit, Light Chaser and many, many more! The full colour 96 page book, is lavishly illustrated with over 100 drawings and diagrams. No prior knowledge of electronics is needed, projects are fun and totally safe to build.

Short Circuits Book
BJ-8502 £3.75

Short Circuits Project Kit
KJ-8504 £12.50

Short Circuits Book
and Project Kit
KJ-8502 £14.85



MORE INFO AVAILABLE ONLINE
AGES 8+



Post & Packing Charges

Order Value	Cost	Note: Products are despatched from Australia, so local customs duty & taxes may apply.
£10 - £49.99	£5	
£50 - £99.99	£10	
£100 - £199.99	£20	
£200 - £499.99	£30	
£500+	£40	
Max weight 12lb (5kg)		• All pricing in Pounds Sterling
Heavier parcels POA		• Minimum order £10
Minimum order £10		Prices valid until 30/9/2011

HOW TO ORDER

WEB: www.jaycarelectronics.co.uk
PHONE: 0800 032 7241*
FAX: +61 2 8832 3118*
EMAIL: techstore@jaycarelectronics.co.uk
POST: P.O. Box 107, Rydalmere NSW 2116 Australia

*Australian Eastern Standard Time
(Monday - Friday 09.00 to 17.30 GMT + 10 hours)
Expect 10-14 days for air parcel delivery



Order online: www.jaycarelectronics.co.uk

Jaycar
Electronics

**velleman®****0845 251 4363****cebek®****UK's No 1 source for VELLEMAN® Kits****Kit Catalogue Available****Self Assembly Kits & Ready made Modules - See our web site for details on the whole range, Data sheets, Software and more.****www.esr.co.uk****Now Available - Cebek Modules**
*All modules assembled & tested.***Digital Echo Chamber Kit**A compact sound effects kit, with built-in mic or line in, line out or speaker (500mW). 4 Adjustment controls.
Power: 9Vdc 150mA**MK182 Velleman kit £11.43****3rd Brake Light Flasher Kit**Works with any incandescent or LED rear centre brake light. Flashes at 7Hz for 5 or 10 times, adjustable re-triggering.
Power: 12Vdc max load 4A**MK178 Velleman kit £6.30****Digital Clock Mini Kit**Red 7 Segment display in attractive enclosure, automatic time base selection, battery back-up, 12 or 24Hr modes.
Power: 9Vac or dc**MK151 Velleman kit £15.09****Proximity Card Reader Kit**

A simple security kit with many applications. RFID technology activates a relay, either on/off or timed. Supplied with 2 cards, can be used with up to 25 cards. Power: 9Vac or dc

**MK179 Velleman kit £14.25****Running Microbug Kit**Powered by two subminiature motors, this robot will run towards any light source. Novel shape PCB with LED eyes.
Power: 2 x AAA Batteries**MK127 Velleman kit £9.02****200W Power Amplifier**A high quality audio power amp, 200w music power @ 4Ω 3-200kHz. Available as a kit without heatsink or module including heatsink.
K8060 Velleman kit £12.85
Heatsink for kit £9.95
VM100 Module £38.54**MP3 Player Kit**

Plays MP3 files from an SD card, supports ID3 tag which can be displayed on optional LCD. Line & headphone output. Remote control add-on. Power: 12Vdc 100mA

**K8095 Velleman kit £39.99****DC to Pulse width Modulator**A handy kit to accurately control DC motors etc. Overload & short circuit protection. Input voltage 2.5-35Vdc, Max output 6.5A.
Power: 8-35Vdc**K8004 Velleman kit £9.95****Audio Analyser Kit**

A small spectrum analyser with LCD. Suitable for use on 2, 4 or 8Ω systems. 300mW to 1200W(20) 20-20kHz Panel mounting, back-lit display. Power: 12Vdc 75mA

**K8098 Velleman kit £31.65****USB DMX Interface**

512 DMX Channels controlled by PC via USB. Software & case included. Available as a kit or ready assembled module.

**K8062 Velleman kit £47.90**
VM116 Module £67.15**USB Interface Board**

Featuring 5 in, 8 digital outputs, 2 in & 2 analogue outputs. Supplied with software. Available as a kit or ready assembled module.

**K8055 Velleman kit £24.80**
VM110 Module £34.90**8 Channel USB Relay Board**

PC Controlled 16A relays with toggle, momentary or timed action. Test buttons included, available in a kit or assembled.

**K8090 Velleman kit £39.95**
VM8090 Module £58.40**Multifunction Up/Down Counter**An up or down counter via on-board button or ext input. Time display feature. Alarm count output. 0-9999 display.
Power: 9-12Vdc 150mA**K8035 Velleman kit £17.85****Nixie Clock Kit**Gas filled nixie tubes with their distinctive orange glow. HH:MM display, automatic power sync 50/60Hz
Power: 9-12Vac 300mA**K8099 Velleman kit £64.96****Mini USB Interface Board**

New from Velleman this little interface module with 15 inputs/outputs inc digital & analogue in, PWM outputs. USB Powered 50mA. Software supplied

**VM167 Module £26.80****Thermostat Mini Kit**General purpose low cost thermostat kit. +5 to +30°C Easily modified temperature range/min/max/hysteresis 3A Relay
Power: 12Vdc 100mA**MK138 Velleman Kit £4.55****Velleman Function Generator**

PC Based USB controlled function generator. 0.01Hz to 2MHz Pre-defined & waveform editor. Software supplied. See web site for full feature list.

**PCGU1000 Velleman £118.38****Velleman PC Scope**

PC Based USB controlled 2 channel 60Mhz oscilloscope with spectrum analyser & Transient recorder. 2 Scope probes & software included. See web site for full feature list.

**PCSU1000 Velleman £249.00****Velleman PC Scope/Generator**

PC Based USB controlled 2 channel oscilloscope AND Function generator. Software included. See web site for full feature list.

**PCSGU250 Velleman £113.67****RF Remote Control Transmitter**

Single channel RF keyfob transmitter with over 13,122 combinations. Certified radio frequency 433.92MHz. Power: 12Vdc 2mA (inc) For use with TL-1,2,3,4 receivers.

**TL-5 Cebek Module £14.64****RF Remote Control Receiver**Single channel RF receiver with relay output. Auto or manual code setup. Momentary output, 3A relay
Power: 12Vdc 60mA For use with TL-5 or TL-6 transmitters.**TL-1 Cebek Module £28.25****Keypad Access Control**An electronic lock with up to ten 4 digit codes. Momentary or timed (1-60sec/1-60min) output. Relay 5A
Power: 12Vdc 100mA Keypad included.**DA-03 Cebek Module £54.26****AC Motor Controller**A 230Vac 375W motor speed control unit giving 33 to 98% of full power.
Power: 230Vac**R-8 Cebek Module £12.14****Digital Record/Player**Non volatile flash memory. Single 20 sec recording via integral mic, 2W output to 8Ω speaker.
Power: 5Vdc 100mA**C-9701 Cebek Module £7.89****2 Digital Counter**Standard counter, 0 to 99 from input pulses or external signal. With reset input, 13.5mm Displays.
Power: 12Vdc 90mA.**CD-9 Cebek Module £12.99****1.8W Mono Amplifier**

Compact mono 1.8W RMS 4Ω power stage, short circuit & reverse polarity protection. 30-18kHz, Power: 4-14Vdc 150mA

**E-1 Cebek Module £5.87****20W 2 Channel Amplifier**

Mono amplifier with 2 channels (Low & High frequency). 20W RMS 4Ω per channel, adjustable high level. 22-22kHz, short circuit & reverse polarity protection. Power: 8-18Vdc 2A

**E-14 Cebek Module £22.11****5W Stereo Amplifier**Stereo power stage with 5W RMS 4Ω. 30-18kHz, short circuit & reverse polarity protection.
Power: 6-15Vdc 500mA**ES-2 Cebek Module £21.54****12Vdc Power Supply**

Single rail regulated power supply complete with transformer. 130mA max, low ripple, 12Vdc with adjustment.

**FE-103 Cebek Module £13.16****1-180 Second Timer**Universal timer with relay output. Time start upon power up or push button. LED indication. 5A Relay
Power: 12Vdc 60mA**I-1 Cebek Module £12.92****Cyclic Timer**Universal timer with relay output. Time start upon power up or push button. On & Off times 0.3-60 Seconds, LED indication. 5A Relay
Power: 12Vdc 80mA**I-10 Cebek Module £14.12****Light Detector**Adjustable light sensor operating a relay. Remote sensor & terminals for remote adjustment pot. 5A Relay
Power: 12Vdc 60mA**I-4 Cebek Module £13.98****Liquid Level Detector**A liquid level operated relay. Remote sensor operates relay when in contact with a liquid. 5A Relay
Power: 12Vdc 60mA**I-6 Cebek Module £13.08****Thermostat**A temperature controlled relay. Adjustable between -10 to 60°C Sensor on remote PCB. Connector for external adjustment pot. 5A Relay
Power: 12Vdc 60mA**I-8 Cebek Module £12.80****Start / Stop Relay**Simple push button control of a relay. Either 1 or 2 button operation 5A Relay
Power: 12Vdc 60mA**I-9 Cebek Module £12.83**

Components	Hardware	Soldering	Switches	Test Equipment	Transformers	Motors
PCB Equipment	Connectors	Power Supplies	Enclosures	Relays		

www.esr.co.uk

Tel: 0191 2514363
Fax: 0191 2522296
sales@esr.co.uk

Station Road
Cullercoats
Tyne & Wear
NE30 4PQ



Prices Exclude Vat @20%.
UK Carriage £2.50 (less than 1kg)
£6.50 greater than 1kg or >£30
Cheques / Postal orders payable to
ESR Electronic Components Ltd.
PLEASE ADD CARRIAGE & VAT TO ALL ORDERS

Editorial Offices:
 EVERYDAY PRACTICAL ELECTRONICS
 EDITORIAL Wimborne Publishing Ltd., 113 Lynwood
 Drive, Merley, Wimborne, Dorset, BH21 1UU
Phone: (01202) 880299. **Fax:** (01202) 843233.
Email: enquiries@wimborne.co.uk
Website: www.epemag.com

See notes on **Readers' Technical Enquiries** below
 – we regret technical enquiries cannot be answered
 over the telephone.

Advertisement Offices:
 Everyday Practical Electronics Advertisements
 113 Lynwood Drive, Merley, Wimborne, Dorset,
 BH21 1UU
Phone: 01202 880299 **Fax:** 01202 843233
Email: stewart.kearn@wimborne.co.uk

Editor: MATT PULZER
Consulting Editor: DAVID BARRINGTON
Subscriptions: MARILYN GOLDBERG
General Manager: FAY KEARN
Graphic Design: RYAN HAWKINS
Editorial/Admin: (01202) 880299
**Advertising and
 Business Manager:** STEWART KEARN
 (01202) 880299

On-line Editor: ALAN WINSTANLEY
EPE Online
 (Internet version) **Editors:**

CLIVE (Max) MAXFIELD
 and ALVIN BROWN
 MIKE KENWARD

READERS' TECHNICAL ENQUIRIES

Email: techdept@wimborne.co.uk
 We are unable to offer any advice on the use, purchase,
 repair or modification of commercial equipment or the
 incorporation or modification of designs published
 in the magazine. We regret that we cannot provide
 data or answer queries on articles or projects that are
 more than five years' old. Letters requiring a personal
 reply must be accompanied by a stamped self-
 addressed envelope or a self-addressed envelope and
 international reply coupons. We are not able to answer
 technical queries on the phone.

PROJECTS AND CIRCUITS

All reasonable precautions are taken to ensure that
 the advice and data given to readers is reliable. We
 cannot, however, guarantee it and we cannot accept
 legal responsibility for it.

A number of projects and circuits published in EPE
 employ voltages that can be lethal. You should not
 build, test, modify or renovate any item of mains-
 powered equipment unless you fully understand the
 safety aspects involved and you use an RCD adaptor.

COMPONENT SUPPLIES

We do not supply electronic components or kits for
 building the projects featured, these can be supplied
 by advertisers.

We advise readers to check that all parts are still
 available before commencing any project in a back-
 dated issue.

ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY
 PRACTICAL ELECTRONICS take reasonable
 precautions to protect the interests of readers by
 ensuring as far as practicable that advertisements are
 bona fide, the magazine and its publishers cannot give
 any undertakings in respect of statements or claims
 made by advertisers, whether these advertisements
 are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances
 will the magazine accept liability for non-receipt of
 goods ordered, or for late delivery, or for faults in
 manufacture.

TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio
 transmitting and telephone equipment which may
 be advertised in our pages cannot be legally used in
 the UK. Readers should check the law before buying
 any transmitting or telephone equipment, as a fine,
 confiscation of equipment and/or imprisonment can
 result from illegal use or ownership. The laws vary from
 country to country; readers should check local laws.

EPE EVERYDAY PRACTICAL ELECTRONICS

Ingenuity Unlimited – Pico prize winners

One of the nicest perks of being editor of *EPE* is reading the many designs that readers dream up and send in for *Ingenuity Unlimited*. Every 20 or so published entries, *EPE* awards a couple of very desirable prizes. The lucky winners receive superb PC-based Oscilloscopes, generously donated by Pico Technology, to whom we again extend our thanks and appreciation for sponsoring the column. For more information about Pico's range of test equipment, visit their website at www.picotech.com, or see their advertisement on page 45 of this issue.

EPE publisher and former editor Mike Kenward and I considered a wonderfully varied collection of published *Ingenuity Unlimited* entries, and after much deliberation, we have decided that the prize winners are: as follows.

Winner – receives a superb PicoScope 3206 Digital Storage Oscilloscope worth £799: Murray Ward – *Regulating Grandfather By Radio* (February 2010). This project really displayed the kind of 'ingenuity' that gives the column its name. Murray combined a radio time signal, a cheap radio clock, analogue electronics and electromechanical components to regulate the pendulum of his 18th century grandfather clock (without altering the clock's precious 'works'). Murray is a worthy winner, well done.

Runner up – a PicoScope 2105 Handheld 'Scope worth £199: Ivan Eamus – *PCB Track Probing Unit* (July 2011). An excellent circuit design for tracing printed circuit tracks between components, IC pins, and sockets, even if components populate the PCB, but without power being connected. This is a genuinely useful bit of kit for project assemblers.

Choosing winners is never easy, especially with the design quality, originality and usefulness of many of the entries. So, while the following didn't make it to winner status, we wish to give them 'honourable mentions for displaying great ingenuity':


Nick Dossis – *Universal Remote Control Receiver* (April 2011) – for finding a handy use for discarded IR 'remotes'.

Thomas Scarborough – *Seeing Eye* (November 2010) – designing a very sensitive detector of light level changes.

M Forbes – *Tuner Control* (January 2009) – a nice design for where a voltage controlled function is required with good resolution and noiseless operation.

Walter Gray – *Simplified Stroboscope* (October 2009) – a useful project that uses high-intensity LEDs instead of a traditional gas discharge lamp.

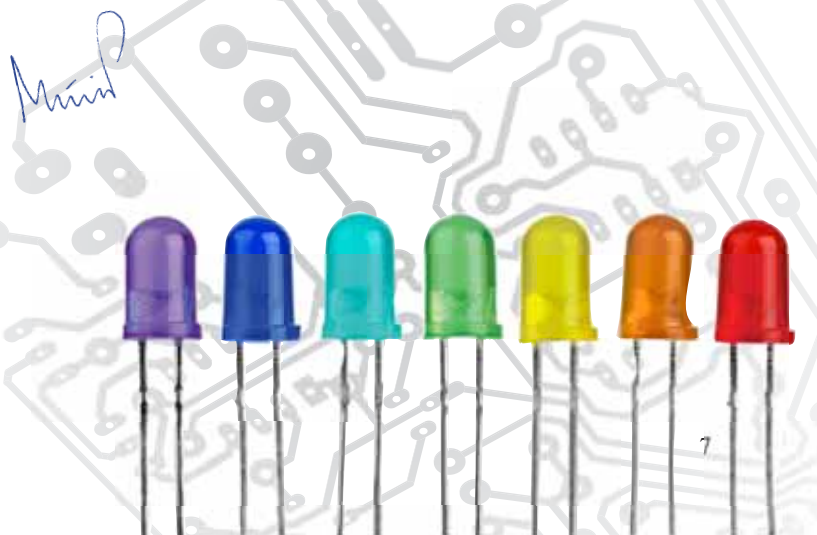Last, but not least, do please keep sending in your designs, we really enjoy reading them, and you never know – you might just win a fabulous prize!



NEWS

A roundup of the latest Everyday News from the world of electronics



Be sure of your facts by Barry Fox

Company bosses traditionally give keynote speeches at industry conferences to enhance their standing. But sometimes the policy can backfire – which it did at the recent annual consumer electronics conference hosted by Intellect, the UK trade association for the technology industry.

Sony dismisses hacking as an 'incident'

Gildas Pelliet, new managing director at Sony UK, presented the keynote speech with his view of the new 'connected world'. But he surprised the audience by referring to the recent disastrous hacking of Sony's Playstation network, in which over 100 million accounts were comprised, only as an 'incident' and hoping the network was 'now robust'.

Pelliet then strongly urged the UK's Digital TV Group to talk again to the European Hybrid Broadcast Broadband TV or 'HbbTV' consortium about the standard for Connected TV, but failed to explain why. He said he was 'disappointed' by the UK's broadband service, but pleased that the UK government had committed to 2Mbps broadband for everyone by 2013. He also referred to Blu-ray starting in 2000, when in fact the format launched in 2006.

At the end of his speech, Pelliet was visibly shocked to be 'corrected' by conference moderator Rory Cellan-Jones, BBC Technology Correspondent, who said firmly: 'I am sorry to tell you your slide was wrong, because the government has now changed the broadband for all date to 2015'.

Then asked by Cellan-Jones to explain what he thought the DTG was doing wrong over Connected TV and HbbTV, Pelliet had to admit he 'didn't



Wired by a five-year old? Too many cable companies claim great technology credentials but seem incapable of even basic installation tasks, blighting the British urban landscape with this kind of mess. Photo: Barry Fox



A North London street earlier this year; 'bombproof' might be excessive, but a cabinet that uses mains power (see fuse and meter lower right) and houses delicate and important equipment ought to be good enough to keep its doors shut. A design that can't is simply not fit for purpose. Photo: Barry Fox

know enough about the subject'.

When asked by Cellan-Jones about the PSN hacking 'incident', which 'destroyed trust in Sony', Pelliet insisted Sony had 'reacted with high speed' and 'the good news is no one has been a victim of fraud'.

Finally, when asked from the floor to elaborate on his reference to the new Ultraviolet standard for downloading music, movies and books to a personal Digital Locker, Pelliet admitted he was 'not familiar with it'.

Virgin media cabinets

At the same conference, Neil Berkett, Virgin Media CEO, gave a separate keynote speech on 'The changing relationship between content and platforms' 'The Killer App for broadband is bandwidth', said Berkett. 'Virgin is a trusted brand. Our fibre optic network passes over half of UK homes. We have invested in next generation infrastructure to build a Digital Britain'.

But Berkett was also visibly shocked when reminded that anyone waking the streets in a Virgin area will see two kinds of telecoms street furniture – bombproof steel boxes installed by BT, and flimsy cabinets owned by Virgin and often open to rain and snow with the electronics and wiring exposed to the elements and hackers. Even worse situations can be seen on the roofs of blocks of flats.

'I have never had that question before' admitted Berkett, obviously taken off guard. 'Open cabinets can cause higher fault rates. We do need to address leakage, which can affect upload speeds. But I can't do anything about our predecessors' 550,000 boxes. I am not going to spend money on making them bombproof.'

IET introduces updated wiring standard

The Institution of Engineering and Technology (IET, formerly the IEE) has launched *The IET Wiring Regulations, 17th Edition, BS 7671:2008* incorporating Amendment No.1, 2011. The amended *IET Wiring Regulations* set out the national standard for which all new electrical installations are to comply.

The amended *Wiring Regulations* have been jointly published



by the IET and the British Standards Institution (BSI) and feature important changes to the 17th Edition, which was published in 2008.

The amended *IET Wiring Regulations* can be purchased from www.theiet.org/amend1. You can find out more about the new requirements for electrical installations, or speak to an expert at the IET on: 01438 765599 or email: technical@theiet.org

North-south, or 1-0?

According to a report from Berkeley University in California, future computers may rely on magnetic microprocessors that consume the least amount of energy allowed by the laws of physics.

Today's silicon-based microprocessor chips rely on electric currents, or moving electrons, that generate a lot of waste heat. But microprocessors employing nanometre-sized bar magnets – like tiny refrigerator

magnets – for memory, logic and switching operations theoretically would require no moving electrons.

Such chips would dissipate only 18 millielectronvolts of energy per operation at room temperature, the minimum allowed by the second law of thermodynamics and called the Landauer limit. That's one million times less energy per operation than consumed by today's computers.



Armchair miracle

While much of the debate around electrical power focuses on choosing the best sources, from coal, nuclear or renewable supplies, other important areas are now the focus of research, in particular looking to crack down on the power lost in transmission lines, however it is generated. Scientists from Rice University in Texas have achieved an important breakthrough in the development of a cable that may make possible a much more efficient electric grid of the future.

A prime technical hurdle in the development of this 'miracle cable', or armchair quantum wire (AQW), is the manufacture of massive amounts of metallic single-walled carbon nanotubes, which are dubbed 'armchairs' for their unique shape, said Rice chemist Andrew Barron.

The AQW will be a weave of metallic nanotubes that can carry electricity with negligible loss over long distances. It will be an ideal replacement for a nation's copper-based grid, which leaks electricity at an estimated 5% per 100 miles of transmission, said Barron, author of a paper about the latest step forward, published online by the American Chemical Society journal *Nano Letters*.

Armchairs are best for carrying current, but can't yet be made alone. They



Nanotube researchers are aiming to revolutionise the transmission of power

grow in batches with other kinds of nanotubes and have to be separated out, which is a difficult process, given that a human hair is 50,000 times larger than a single nanotube.

Barron's lab demonstrated a way to take small batches of individual nanotubes and make them dramatically longer. Ideally, long armchair nanotubes could be cut, re-seeded with catalyst and regrown indefinitely.

Amplification of nanotubes was seen as a key step toward the practical manufacture of AQW by the late Rice professor, nanotechnology pioneer and Nobel laureate Richard Smalley.

The key was finding the right balance of temperatures, pressures, and reaction times to promote growth, Barron said.

Parallax GPS receiver module

Parallax have launched a new GPS receiver module. The VPN1513 provides a fully open source and customisable GPS receiver solution for microcontroller projects. It uses a SiRF Star III chipset capable of tracking up to 20 satellites. The module supports both 'raw' output mode for NMEA 0183 strings and the default 'smart' mode for specific user-selected data via a serial interface.

The VPN1513 also features a Propeller coprocessor for easy interface with any BASIC Stamp 2 module. The Propeller is also fully reprogrammable and includes access to all 32 IO pins, allowing the GPS receiver module to be easily transformed into a standalone device.

Microchip brings advanced control to cost-sensitive designs with new devices



Microchip has announced a new series of 16-bit PIC microcontrollers (MCUs) and dsPIC digital signal controllers (DSCs) that bring advanced control to cost-sensitive general purpose and motor-control designs. The new devices enable low-cost, sensor-less motor control designs, with support for a wide range of motor-control algorithms, plus an on-chip charge time measurement unit (CTMU), 10-bit analogue-to-digital converter (ADC) and mTouch capacitive touch sensing to enable intelligent sensor applications.

The devices are supported by three new plug-in modules and a single-board motor control starter kit that includes capacitive-touch sliders and an onboard brushless DC motor. This makes it easy for designers to create high-performance personal projects or appliances, such as washing machines, medical products such as infusion pumps, and industrial AC-induction motors, as well as other cost-sensitive applications.

For more information, visit Microchip's website at: www.microchip.com/get/PFG6. A video demo of the kit can be viewed on YouTube at: www.microchip.com/get/RUBM



Versatile design accepts b

Are you listening to CDs via your DVD player? Does your DVD player have average sound quality or worse, cause buzz and hum problems when hooked up to your hifi system? Either way, you need this high-quality Stereo Digital-To-Analogue Converter (DAC) to get first class sound and zero hum.

THIS 24-BIT, 96kHz-capable stereo DAC provides sound quality equal to the best high-end CD players, regardless of price. It has one coaxial S/PDIF input and two TOSLINK (optical) inputs, to which you can connect a DVD player, set-top box, DVR, computer or any other source of linear PCM digital audio. It also has left and right RCA phono sockets for connection to a stereo amplifier or home theatre receiver.

If you already own a DVD player of average quality or better, you can hook

it up to this DAC and immediately upgrade the sound quality.

Unfortunately, most DVD players have mediocre audio quality from their audio outputs, especially in terms of distortion. So why are typical DVD players so poor in audio performance? Partly, it is because they are designed down to a very low price, and while their on-board DAC might be quite a reasonable component, the supporting circuitry has been cut to the bone in order to keep the overall price as low as possible. It is also true that many cheap (and not so

cheap) DVD players are plagued with quite strong extraneous RF in the audio outputs, mainly related to the video output signals that they continuously produce, regardless of whether they are playing DVDs or CDs.

In addition, virtually all DVD players, except the most expensive models, use switch-mode power supplies. These have the advantage of being very efficient and especially with respect to recent models, have very low standby power consumption. The drawback of switch-mode power supplies is that

Build a high-quality stereo DAC for superb sound from your DVD player

Part 1: Design by NICHOLAS VINEN

both optical and coaxial inputs

they produce lots of switching harmonics, which can work their way into the audio outputs.

Finally, because all DVD players these days are double-insulated and come with two-core power cords, they inevitably cause hum and buzz when connected to the audio inputs of high-fidelity amplifiers, which are usually earthed via a three-core mains cord. There is no simple way to fix any of these problems, but this new DAC project fixes them all and provides first-class audio performance into the bargain.

Main features

Our prototype DAC is housed in a one-unit high rack-mount case. The front-panel controls are just an on/off switch and three LED-illuminated momentary pushbuttons.

In operation, the DAC scans for a valid signal on one of its three digital

inputs, and when one is detected, it immediately locks onto it and works. Alternatively, you can select the wanted input signal by pressing the relevant button, or you can do it with a Philips RC5-compatible remote control (such as most universal remotes) which can also be used to control the volume from the left and right outputs.

As previously stated, the unit accepts both TOSLINK (optical) and coaxial (S/PDIF) inputs, while a pair of RCA phono sockets is used for the left and right stereo outputs.

User interface

The user interface provides two functions – display of the DAC status and control over its configuration, primarily selecting between inputs.

Status display is provided by the five LEDs on the front panel. The LEDs in the three illuminated pushbuttons show

which of the three channels is currently selected. They correspond, left-to-right, to the inputs on the rear panel – the RCA S/PDIF input is number 3.

The two other LEDs indicate whether there is a valid S/PDIF signal detected on that channel (yellow LED) and whether any audio data is present (green LED). The yellow LED also flashes to acknowledge signals from the remote control.

Holding down various combinations of the buttons on the front panel allows you to enter a set-up mode where you can assign remote control functions and configure the automatic input switching.

The automatic input switching system allows the DAC to select whichever input has a valid signal. It allows you to leave the DAC on and switch between various input sources, without the need to manually change channels.

Specifications

Signal-to-noise ratio:	–108dB (unweighted, 22Hz to 22kHz) –114dB (A-weighted), both with respect to 2V RMS
Total harmonic distortion:	<0.0018% @ 1kHz and 2V RMS
Channel separation:	–105dB @ 100Hz and 1kHz –85dB @ 10kHz –73dB @ 20kHz
Linearity:	within 1dB @ –90dB
Frequency response:	+0.0, –0.15dB, 20Hz to 20kHz
Supported sample rates:	28 to 108kHz
Supported bit depths:	16-bit, 20-bit and 24-bit
Supported channel formats:	stereo PCM
Clock jitter:	jitter tolerant; clock jitter is typically < 50ps

For example, if you have a DVD player and set-top box connected, and after watching a DVD you switch the DVD player off and the set-top box on, the DAC will change inputs by itself about 10 seconds after you've turned the DVD player off. This delay can be changed, depending on your preference.

How it works

In operation, the DAC constantly monitors the current input status for two parameters: (1) the presence of an S/PDIF signal, and (2) the presence of audio data (non-silence). This is the same information which is displayed via the status LEDs. After a user-defined period (default 10 seconds) without a valid signal, the input channels will enter a 'scanning' mode, where each input is rapidly selected in turn. This scanning continues until a valid signal is detected, at which point it stops on that input.

There is also a user-defined period of silence (default one minute) after which scanning will begin, even with a valid signal present. This is because many devices with digital audio outputs keep their outputs active, even when they are not playing any material; for example, when the DVD is stopped. Thus, the only reliable way to determine if content is actually being played is to look for an audio signal.

Of course, you don't want it to start scanning the instant there is silence, as there are often short silent periods between tracks, or you may be changing discs or briefly pausing playback.

The two delays can be configured from 100ms up to several hours, or disabled entirely. In addition, it's pos-

sible to configure different delays if the current channel has been manually selected, either from the front panel buttons or the remote control. This is so that you can set the automatic scan times fairly short without having it start scanning too soon after you force it to a particular channel.

By default, these delays are set to five minutes without a signal and scan on silence after a manual channel change is disabled.

Default input and volume control

There is also the matter of which input is active when power is first applied. By default, the first input is selected, but you can configure it so that the default is any of the three inputs, or so that it immediately scans, or even so that it starts up with whichever input last had a valid signal before it was powered off.

Finally, there is a built-in volume control in the DAC, and it is possible to use the remote control to change the volume. This has a 30dB range, but we don't recommend using it if you want the very best sound quality. Because the volume control is digital, total harmonic distortion will become worse as the volume is reduced.

If you do control the volume using a remote, it will remember the last setting the next time it is powered on. The initial default is maximum volume and that's where it should be left for best sound quality.

Note also that multi-channel audio formats like DTS or Dolby Digital are not supported, and in any case, many DVD players turn off the TOSLINK (optical) output when multi-channel

modes are employed. This means you have two choices when using this DAC with a DVD player in a home-theatre configuration. One option is to connect the DVD player's outputs directly to your amplifier, along with the DAC outputs, using a separate set of cables and switch between them, depending on whether you are playing multi-channel or stereo content.

Alternatively, if you only have stereo speakers, you can configure your DVD player to convert multi-channel content to stereo on the digital output and play all content via the DAC. Some, but not all, DVD players have such a feature, which is usually configured via an on-screen menu. If you just want to use a DVD player to play CDs you can ignore the DVD player's stereo outputs altogether, and just use the digital output. It is also possible to use a CD player with digital outputs, although they are becoming less common.

Because the DAC supports 24-bit 96kHz content, as well as CD quality (16-bit, 44.1kHz) and other common audio formats, it is also possible to play higher definition audio content. The supported range of sample rates is 28-108kHz, and recognised bit depths are 16, 20 and 24 bits (although in reality 16-bit content is always promoted to 20 bits when sent via S/PDIF). This covers most common linear audio formats. De-emphasis is also supported, although very few CDs are recorded with it enabled. However, de-emphasis has been included, since it is part of the CD Audio 'Red Book' standard.

While the ability to play back 24-bit 96kHz content is attractive, there is a catch: many devices capable of playing back audio of this quality disable their digital outputs when doing so! This often includes all 'DVD Audio' players, which is a great pity. Presumably, the music industry was worried about people making digital copies of such content and thus deny us the ability to use the digital output for high-quality content at all. No wonder DVD Audio failed to take off! However, even plain old CDs will sound great played back through this DAC, as long as they were properly recorded and mastered.

Clock jitter

Regarding the audio quality, not only does the DAC chip itself provide high-quality audio output, but also the

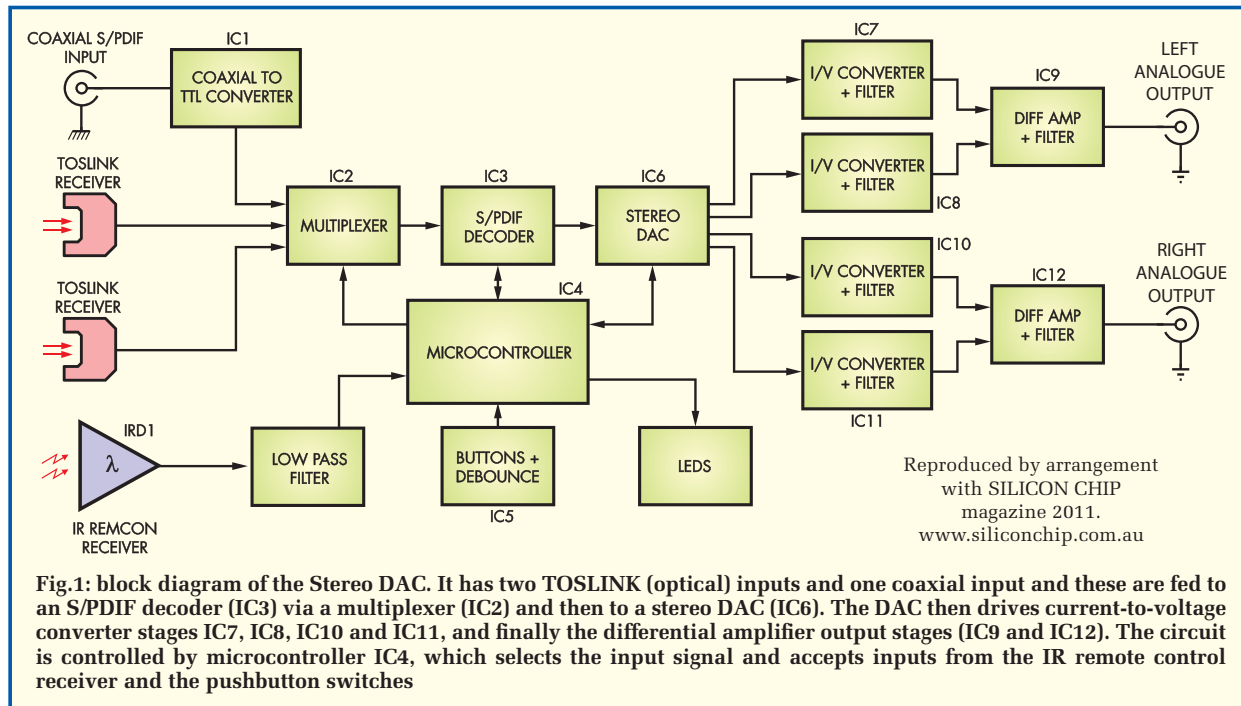


Fig.1: block diagram of the Stereo DAC. It has two TOSLINK (optical) inputs and one coaxial input and these are fed to an S/PDIF decoder (IC3) via a multiplexer (IC2) and then to a stereo DAC (IC6). The DAC then drives current-to-voltage converter stages IC7, IC8, IC10 and IC11, and finally the differential amplifier output stages (IC9 and IC12). The circuit is controlled by microcontroller IC4, which selects the input signal and accepts inputs from the IR remote control receiver and the pushbutton switches

S/PDIF decoder ‘re-clocks’ the audio data to remove ‘clock jitter’. Clock jitter refers to the fact that the clock frequency of the data being transmitted over the digital link varies somewhat from sample to sample. Ideally, there will be no jitter, meaning the clock pulses (and thus data bits) come at exactly the same interval, but consumer equipment often doesn’t have the best clock stability, and this can prejudice the dynamic range.

The decoder solves this by re-clocking the data using a ‘phase-locked loop’ (PLL). The PLL’s frequency is locked to the sample frequency of the data being received, but because only the average clock frequency determines the PLL frequency, if the PLL is sufficiently stable it will reject most of the jitter. The DIR9001 decoder from Texas Instruments/Burr Brown claims a typical specification of around 45 picoseconds (ps) jitter at 44.1kHz, and 30ps jitter at 96kHz when the master clock is running at 512fs, which is how it is configured.

You may be wondering why the decoder IC chosen isn’t capable of handling sample rates up to 192kHz. After all, the DSD1796 DAC supports this sample rate and some content is available at 192kHz, so it would be nice to support it.

The main reason is that Burr Brown does not make a 192kHz S/PDIF

decoder, and other choices such as the Crystal CS8416 have inferior specifications, including jitter tolerance. For the CS8416, the output jitter is quoted as around 100ps – twice that of the DIR9001. Since most content available is still 44.1kHz or 48kHz, and since the difference in quality between 96kHz and 192kHz audio is minimal, we feel that the DIR9001 is the superior device.

PC board line-up

Inside the chassis, the circuitry is accommodated on four PC boards: an Input and Control Board, a Front-Panel Switch Board, a Stereo DAC/Analogue Board and a Power Supply Board. In the block diagram of Fig.1, the Stereo DAC and all blocks to its right are mounted on the DAC/Analogue Board, while the circuitry to the left is on the control board. The front panel board carries the buttons, LEDs and an infrared remote control receiver.

Not shown on Fig.1 is the power supply board. This is available from Jaycar (Cat. KC-5418) as a kit. It can be run from a small 15V-0V-15V toroidal transformer, or from a 15V AC plugpack.

Block diagram

Fig.1 shows the main circuit sections. To the left are the two TOSLINK inputs, the S/PDIF input and the infrared (IR)

remote control receiver. These are fed into multiplexer IC2, and then to the S/PDIF decoder IC3. The output of the decoder in turn feeds the stereo DAC (IC6), while all three are under the control of the microcontroller (IC4). IC4 also accepts inputs from the illuminated pushbutton switches and from the IR remote receiver (after filtering) and it drives the LEDs.


The DAC has two sets of differential outputs, and these drive four current-to-voltage converter stages involving IC7, IC8, IC10 and IC11. The four balanced voltage outputs from these stages then drive differential op amps IC9 and IC12 to derive the left and right audio outputs, respectively.

Circuit details

Now let’s have a detailed look at the circuitry of the Input and Control Board – see Fig.2. The two TOSLINK optical receivers each deliver a TTL (5V peak) output signal. The coaxial input is a little more tricky because S/PDIF over coaxial cable (75Ω) is a fairly low level signal – around 0.5V peak-to-peak and even less after cable termination. Therefore, the coaxial signal receiver circuit consists of an amplifier which boosts this signal to TTL levels.


The resulting three TTL S/PDIF signals, one from each input, are then

Constructional Project

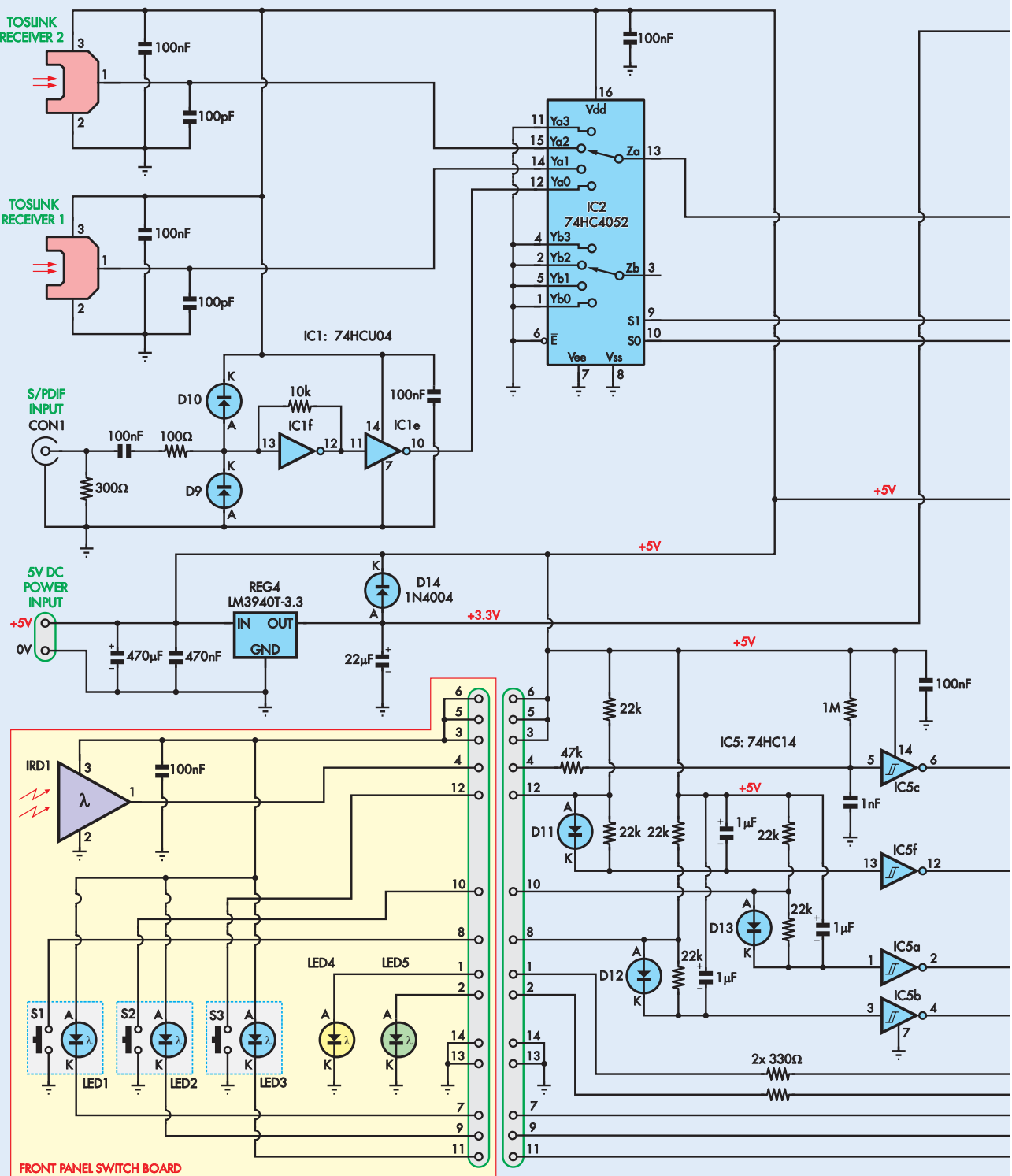

STEREO DIGITAL-TO-ANALOGUE CONVERTER INPUT AND FRONT PANEL BOARDS

Fig.2: the Input Board carries the TOSLINK and S/PDIF inputs, the multiplexer (IC2), the S/PDIF decoder (IC3) and the microcontroller (IC4). The Front Panel Switch Board (yellow background) carries the switches, LEDs and IR receiver

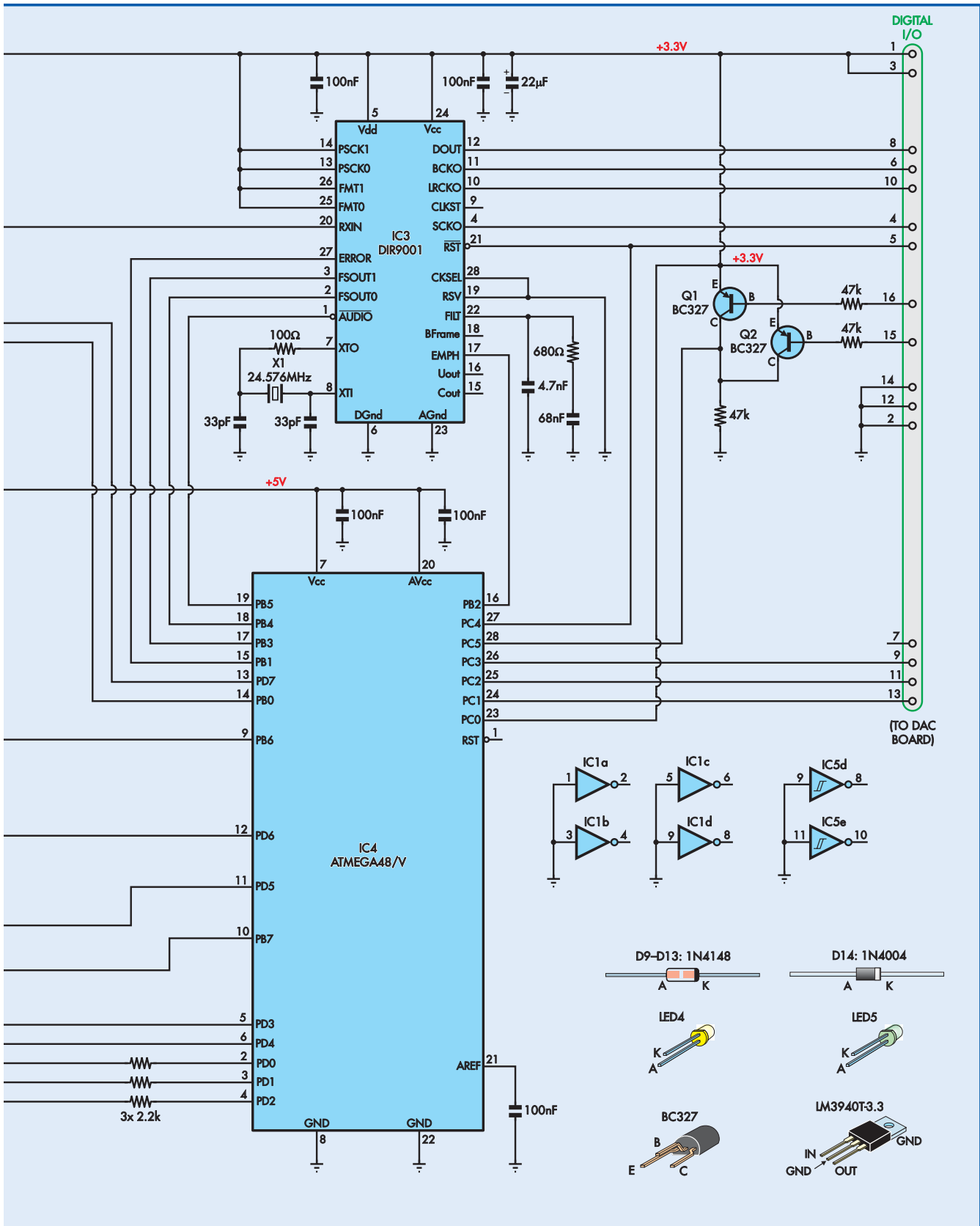

What are S/PDIF and TOSLINK?

The acronym S/PDIF (or SPDIF) stands for 'Sony/Philips Digital Interface'. Basically, it is a standardised serial interface for transferring digital audio data between consumer-level equipment such as DVD and CD players, DAT and DVD recorders, surround-sound decoders and home-theatre amplifiers.

S/PDIF is very similar to the AES3 serial digital interface used in professional recording and broadcasting environments. In operation, each digital audio sample (16-24 bits) is packaged along with status, control and error-checking information into a 32-bit binary word. This is then modulated or encoded into a serial bitstream using the biphase mark code (BMC).

BMC involves combining the data bits with a clock signal of twice the data bit rate, in such a way that a binary '1' results in two polarity reversals in one bit period, while a binary '0' results in a single polarity reversal. This double bit-rate signal is self-clocking at the receiving end and has no DC component.

The BMC encoded serial bitstream is then transmitted as a 400mV peak-to-peak signal along a single 75-ohm coaxial cable. In most cases, the cable connectors used are standard RCA phono or 'Cinch' connectors, as also used for analogue audio and composite video.

Although originally developed for conveying linear PCM (LPCM) digital audio signals, as used in CD and DAT audio,

Digital Audio Bitstream Formats

SOURCE & CODING	CD-Audio (LPCM)	DVD-Video & DAT (LPCM)	DVD-Video (COMPRESSED)		
			DOLBY DIGITAL (AC-3)	MPEG-2 AUDIO	DTS AUDIO
SAMPLING RATE	44.1kS/s	48kS/s	48kS/s	48kS/s	48kS/s
MAX DATA BIT RATE	2822kb/s	3072kb/s	448kb/s	456kb/s	754.5kb/s
SPDIF (TOSlink) BMC BIT RATE	5644kb/s	6144kb/s	896kb/s	912kb/s	1509kb/s

S/PDIF has also been adapted for conveying compressed digital audio, including Dolby Digital (AC-3), DTS and MPEG-2 audio.

TOSLINK is essentially just the S/PDIF signal format converted into the optical domain, for transfer along optical-fibre cables. The accompanying table (above) shows the most common domestic audio bitstream formats and the S/PDIF/TOSLINK bit rates for each one. Note that LPCM audio is rarely used for DVD-Video, because even a stereo audio track requires a BMC bit rate of 6.1Mb/s.

Many current-model DVD players and recorders are provided with either coaxial S/PDIF or TOSLINK digital audio inputs and outputs, or quite often a mixture of both. Similarly, many home-theatre amplifiers are provided with coaxial S/PDIF and/or TOSLINK inputs. This is also the case with many up-market PC sound cards.

fed into the 74HC4052 analogue/digital multiplexer (IC2). Just think of IC2 as a selector switch under the control of the microcontroller (IC4).

Depending on which input is selected by the microcontroller, one of them is fed into the DIR9001 Digital Audio Interface Receiver (IC3). This does the S/PDIF decoding. The DIR9001 requires a 3.3V supply, which is provided by an LM3940T-3.3 3-terminal voltage regulator (REG4).

IC3 employs a 24.576MHz crystal, together with two 33pF load capacitors and a 100Ω current-limiting resistor. This provides a frequency reference for the decoder to determine the actual sampling rate of the audio signal. This is necessary in order to provide the ability to apply digital de-emphasis, since the digital filter response needs to match the sample frequency.

The DIR9001 also requires two 5% metal-film capacitors (4.7nF and 68nF) and a 1% metal-film resistor (680Ω) to form the PLL loop filter. The remaining decoder-associated components are power supply bypass capacitors.

The DIR9001 decoder converts the digital signal into a serial PCM stream (DOUT) which is passed directly to the DAC chip (IC6) itself, along with three clock signals. These are the sample

clock (LRCKO), bit clock (BCKO) and master clock (SCKO). The sample clock matches the audio signal's sample rate, while the bit clock is generally 64 times that rate and is used to clock the actual data. The master clock signal is also a multiple of the sample rate – in this case, 512 times.

The master clock is used to time the DAC's oversampling, which not only makes the post-DAC analogue filters easier to design, but is also required for a delta-sigma architecture DAC such as used in this circuit.

The decoder also outputs a number of flags which are set according to the contents of the S/PDIF stream. These indicate whether there is a valid signal present (AUDIO, ERROR) and whether the audio has been pre-emphasised (EMPH). In addition, FSOUT0 and FSOUT1 indicate the detected sample rate.

There is one additional connection to the DIR9001 and that is a reset line (RST) from the microcontroller. According to the DIR9001 data sheet, an external reset is required each time power is applied. The microcontroller provides this reset signal by monitoring the 3.3V line with its ADC and holding reset low until the supply rises above 2.7V, as specified in the data sheet.


Atmel microcontroller

Controlling the whole circuit is the Atmel Mega48/V microcontroller (IC4). This is powered by the main +5V rail which comes from the power supply board described later.

Note that the switch buttons (S1 to S3) are not connected directly to the micro, but rather via some RC filters and a 74HC14 hex Schmitt trigger inverter (IC5). This is because when a button is pressed, the contacts tend to 'bounce' and switch rapidly on and off for a short period.

Each RC filter, and its associated diode, delays the button press detection long enough to allow the bounce to cease and the Schmitt trigger inverter adds hysteresis to provide a minimum 'on' pulse to the microcontroller. De-bouncing can also be performed in software, but the hardware method has its advantages and it's one less task for the microcontroller to perform.

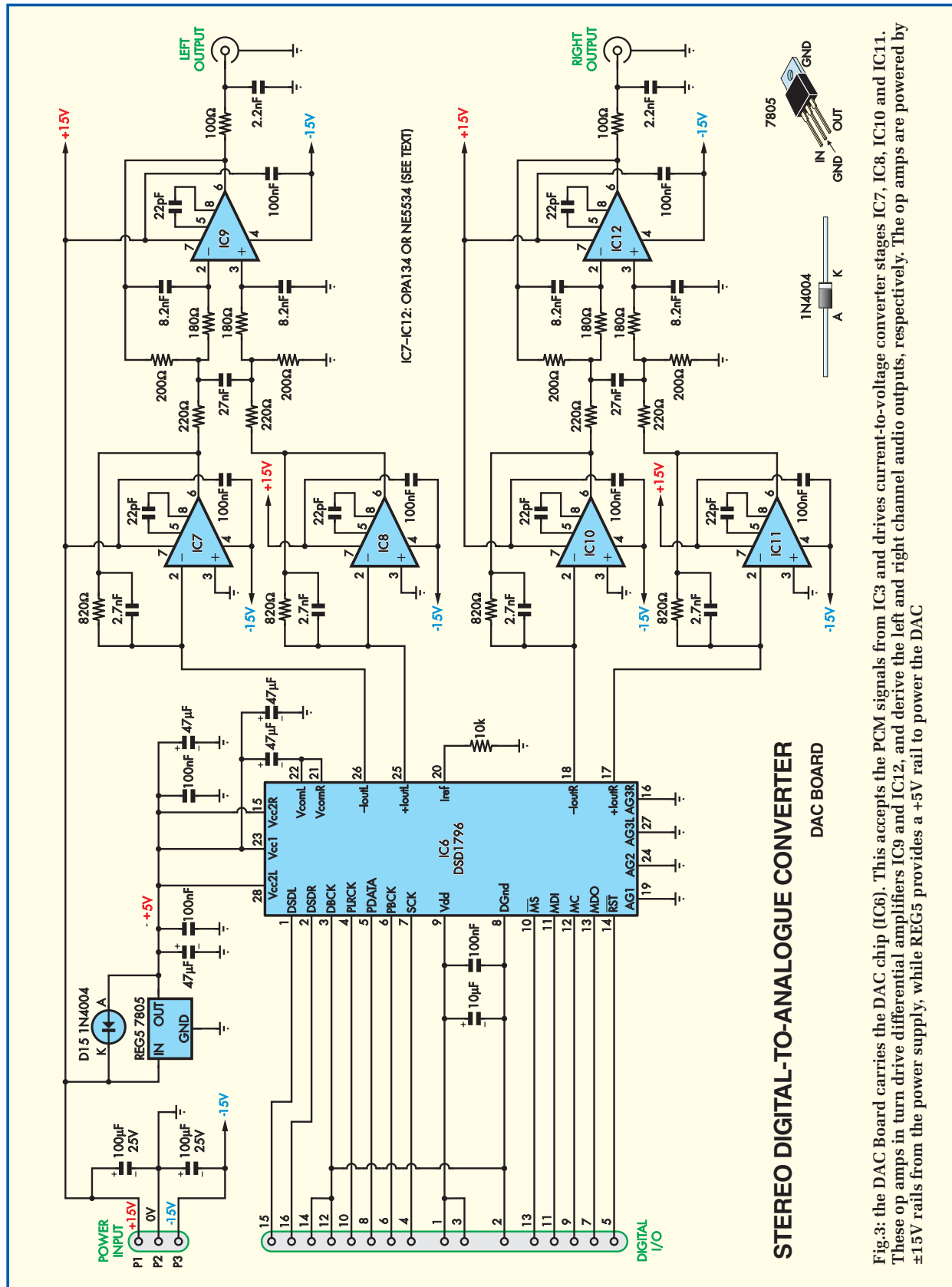Similarly, the IR receiver's output is fed to microcontroller IC4 via an RC filter and Schmitt trigger IC5c. This is done to filter out any noise generated by other IR sources in the room (apart from the remote), which could cause false triggering in the microcontroller. By filtering the IR receiver's output,



Constructional Project



The front panel is uncluttered and carries just the power switch, the three input selector pushbuttons (with their integral blue LEDs) and the valid signal and audio data indicator LEDs. The hole in the panel immediately to the left of the pushbuttons is for the IR detector (IRD1)



The rear panel carries the left and right audio output sockets, the coaxial and TOSLINK input sockets, the fuseholder and the IEC mains connector

we ensure that only signals with a minimum pulse width are detected.

Basically, the Philips RC5 code 'on-time' is a minimum of around $889\mu\text{s}$ (32 pulses at 36kHz), so the filter is designed to reject any shorter IR pulses. Again, this is not strictly necessary, but it only requires a few parts and results in more reliable remote control operation.

DAC board

Fig.3 shows the DAC Board circuit. The DAC chip itself is a Texas Instruments/Burr Brown DSD1796 (IC6) and, as previously stated, has two pairs of differential current outputs rather than voltage outputs. These are current sinks, and the current is directly proportional to the sample value after conversion.

This allows for higher performance than would be possible with a voltage-output DAC of similar design, as the

external op amps can run at higher supply voltages (ie, $\pm 15\text{V}$) and with separate supply bypassing.

There are a number of support components around the DSD1796, most of them supply bypass capacitors. In addition, there is a $10\text{k}\Omega$ resistor on pin 20 which sets the output level of the DAC, while a $47\mu\text{F}$ capacitor between pins 21 and 22 and the supply at pin 23 stabilises the DAC's internal reference voltage.

The first analogue stage following each of the four outputs from IC6 is a current-to-voltage converter and low-pass filter. Each stage consists of a single op amp (IC7, IC8, IC10 and IC11) plus an 820Ω resistor and 2.7nF capacitor. The low-pass filter is the first of three, the total effect of which rolls off the frequency response at 18dB/octave above about 24kHz.

In operation, the left channel differential outputs from the DAC (IC6), are converted from current to voltage using op amps IC7 and IC8. Their outputs are in turn fed to a passive filter which consists of 220Ω resistors and a common 27nF capacitor. The filtered differential outputs are then combined by op amp IC9, which acts as a differential amplifier and active low-pass filter.

Op amps IC10, IC11 and IC12 function in exactly the same manner to produce the right channel audio output.

Output op amps

Virtually all of the circuit for the DAC Board circuit is as suggested in the Texas Instruments' data sheet for the DSD1796. However, we did make some important changes.

First, after extensive testing, we decided that OPA134 op amps are the best

Our second departure from the recommended 'Texas Instruments' DSD1796 circuit was to use a single 100nF bypass

Fig-4: the low-noise linear supply for the DAC is based on common 3-terminal regulators. It provides $\pm 15\text{V}$ rails to power the audio op amps, plus a $+5\text{V}$ rail to power the Input and Control Board

Parts List – Stereo Digital-To-Analogue Converter (DAC)

Chassis Hardware

- 1 1U-high custom steel case with screened front and rear panels
- 1 15V+15V 30VA or 20VA toroidal transformer (Jaycar MT-2086)
- 1 SPST 6A 250VAC slimline rocker switch (Jaycar SK-0975)
- 1 male chassis-mount IEC socket (Jaycar PP-4005)
- 1 panel-mounting fuseholder, with 250V AC 500mA SB fuse (Jaycar SZ-2028)
- 1 230V AC 3-pin IEC mains power lead
- 5 5.3mm ID insulated crimp eyelets (Jaycar PT-4614)
- 4 M4 × 10mm machine screws
- 8 M4 nuts
- 8 M4 shakeproof washers
- 5 4.8mm fully-insulated female spade crimp connectors
- 20 small nylon cable ties
- 1 40mm-length of 16mm-ID heatshrink tubing (to cover rear of fuseholder)
- 1 30mm-length of 20mm-ID heatshrink tubing (to cover mains switch)

Wire and Cable

- 1 400mm-length heavy-duty red hook-up wire
- 1 240mm-length heavy-duty green hook-up wire
- 1 320mm-length heavy-duty black hook-up wire
- 1 350mm-length 7.5A 250V AC brown wire for mains cabling
- 1 500mm-length 7.5A 250V AC green/yellow wire for mains cabling

Input Board

- *1 PC board, code 820, size 113mm × 93mm

- 2 PC-mount TOSLINK (optical) receivers (Jaycar ZL-3003)
- 1 black PC-mount RCA socket
- 1 14-pin PC-mount IDC header socket
- 1 16-pin PC-mount IDC header socket
- 1 14-pin IDC line socket
- 1 16-pin IDC line socket
- 1 3-pin header and shorting jumper
- 1 500mm-length 16-way IDC ribbon cable
- 1 2-way screw terminal block, 5.08mm pitch
- 2 14-pin DIP machined IC sockets
- 1 16-pin DIP machined IC socket
- 1 28-pin DIP machined IC socket
- 5 M3 × 10mm tapped spacers
- 10 M3 × 6mm machine screws
- 1 500mm-length 0.71mm tinned copper wire (for links)
- 1 24.576MHz crystal (HC/49 or HC/49US)

Semiconductors

- 1 74HCU04 hex inverter (IC1) – **do not** use 74HC04
- 1 74HC4052 analogue/digital multiplexer (IC2)
- 1 DIR9001PW Digital Audio Interface Receiver (IC3)
- 1 ATMEGA48V or ATMEGA48P programmed microcontroller (IC4)
- 1 74HC14 hex Schmitt trigger inverter (IC5)
- 1 LM3940T-3.3 LDO 3-terminal regulator (REG4)
- 2 BC327 PNP transistors (Q1,Q2)
- 5 1N4148 diodes (D9-D13)
- 1 1N4004 diode (D14)

Capacitors

- 1 470µF 6.3V electrolytic

- 2 22µF 6.3V electrolytic
- 3 1µF 6.3V electrolytic
- 1 470nF MKT metallised polyester
- 11 100nF MKT metallised polyester
- 1 68nF MKT metallised polyester
- 1 4.7nF MKT metallised polyester
- 1 1nF MKT metallised polyester
- 2 33pF ceramic
- 2 100pF ceramic

Resistors (0.25W, 1%)

- 1 1MΩ 1 680Ω
- 4 47kΩ 2 330Ω
- 6 22kΩ 1 300Ω
- 1 10kΩ 2 100Ω
- 3 2.2kΩ

DAC Board

- *1 PC board, code 821, size 94mm × 110mm
- 1 red PC-mount RCA socket
- 1 white PC-mount RCA socket
- 1 16-pin PC-mount IDC header socket
- 1 16-pin IDC line socket
- 1 3-way screw terminal block, 5.08mm pitch
- 4 M3 × 10mm tapped spacers
- 8 M3 × 6mm machine screws
- 1 500mm-length 0.71mm tinned copper wire (for links)
- 6 8-pin DIP machined IC sockets

Semiconductors

- 1 DSD1796 24-bit audio DAC (IC6)
- 6 OPA134 op amps (IC7 to IC12) (or use NE5534 op amps for slightly reduced performance)
- 1 7805 +5V regulator (REG5)
- 1 1N4004 diode (D15)

Capacitors

- 2 100µF 25V electrolytic

capacitor across the supply pins (7 and 4) of each amp. This avoids coupling supply noise into the signal ground and also provides effectively twice as much capacitance.

Third, we added a fourth low-pass (passive) filter stage to the outputs of op amps IC9 and IC12. This consists of a 2.2nF capacitor following the 100Ω current-limiting resistors and provides a rolloff (pole) at roughly 800kHz. This will slightly attenuate any high-frequency switching artefacts present on the output of the DAC. In addition, since this is a passive filter, it will be effective at

filtering any very high-frequency noise which some of the active filter stages may pass through.

Power supply

As noted, this design uses a low-noise power supply. It provides regulated ±15V and +5V outputs.

The power supply board accepts a 30V AC centre-tapped input from the specified toroidal transformer, formed by joining the two 15V AC secondary windings. Diodes D1 to D4 and two 2200µF capacitors rectify and filter the input to give ±21V DC (nominal) rails.

LM317 and LM337 adjustable regulators (REG1 and REG2) generate the complementary positive and negative supply rails. Their outputs are programmed to ±15V by the 100Ω and 1.1kΩ resistors connected to their OUT and ADJ terminals. We've used adjustable regulators because the ADJ terminals can be bypassed to ground (0V) to improve ripple rejection, which we've done using 10µF capacitors. Diodes D5 and D7 provide a discharge path for the capacitors should an output be accidentally shorted to ground.

4 47 μ F 16V electrolytic
 1 10 μ F 6.3V electrolytic
 9 100nF MKT metallised polyester
 2 27nF MKT metallised polyester
 4 8.2nF MKT metallised polyester
 4 2.7nF MKT metallised polyester
 2 2.2nF MKT metallised polyester
 6 22pF ceramic

Resistors (0.25W, 1%)

1 10k Ω 4 200 Ω
 4 820 Ω 4 180 Ω
 4 220 Ω 2 100 Ω

Front Panel Switch Board

- *1 PC board, code 822, size 103mm \times 34mm
 - 3 vertical PC-mount momentary pushbutton switches with blue LEDs (S1-S3) (Jaycar SP-0622)
 - 1 14-pin PC-mount IDC header socket
 - 1 14-pin IDC line socket
 - 4 M3 \times 6mm tapped nylon spacers
 - 4 M3 \times 15mm black-anodised pan-head machine screws
 - 4 M3 star washers
 - 4 M3 nuts
 - 1 100mm-length 0.71mm tinned copper wire (for links)
 - 1 100nF MKT metallised polyester capacitor
- ## Semiconductors
- 1 infrared receiver module (IRD1) (Jaycar ZD-1952)
 - 1 5mm yellow LED (LED4)
 - 1 5mm green LED (LED5)

Power Supply Board

- *1 PC board, code 823, size 54.6mm \times 80mm
- 3 Micro-U 19°C/W TO-220 finned heatsinks
- 2 3-way terminal blocks, 5.08mm pitch (CON1, CON2)
- 1 2-way terminal block, 5.08mm pitch (CON3)
- 4 6mm untapped Nylon spacers
- 5 M3 \times 6mm pan-head screws
- 1 M3 nut and flat washer

Semiconductors

- 1 LM317T adjustable positive regulator (REG1)
- 1 LM337T adjustable negative regulator (REG2)
- 1 7805 +5V regulator (REG3)
- 8 1N4004 diodes (D1-D8)

Capacitors

- 2 2200 μ F 25V PC electrolytic
- 2 100 μ F 16V PC electrolytic
- 1 47 μ F 25V PC electrolytic
- 3 10 μ F 16V PC electrolytic
- 2 100nF 50V MKT metallised polyester

Resistors (0.25W, 1%)

- 2 1.1k Ω
- 2 100 Ω
- 1 330 Ω 5W 5% (R2)
- 1 100 Ω 5W 5% (R1)

* These boards will be available as a set from the *EPE PCB Service*

Two reverse-connected diodes, D6 and D8, across the outputs prevent their respective rails from being driven to the opposite polarity (eg. if a regulator fails), something that should never occur during normal operation.

A 7805 regulator (REG3) is used to generate the +5V rail. The 100 Ω 5W resistor in line with REG3 reduces power dissipation in the regulator. As the +5V supply draws power from only the positive side of the unregulated DC input, a 330 Ω 5W resistor across the negative input is included to balance the rails so that they decay at similar rates at power off.

The +5V rail provides the power to the circuitry on the main Control Board, as well as driving the LM3940T-3.3 regulator which provides power for the DIR9001 decoder. This regulator also provides a +3.3V rail (Vdd) for the DAC.

It might seem strange to use a 7805 for REG3 when we want a low-noise


supply, but in fact this series of regulators has quite low output noise when used with a decent-sized output capacitor.

Finally, the +5V rail for the analogue section of the DAC does not come from REG3 on the power supply board. Instead, we use another LM7805 5V regulator on the DAC board, and this is powered from the +15V rail from the power supply. This is so that digital switching noise in the 5V digital supply does not affect the DAC's performance.

Software

The software program files for the *Stereo Digital-to-Analogue Converter* will be available from the *EPE* website at: www.epemag.com.

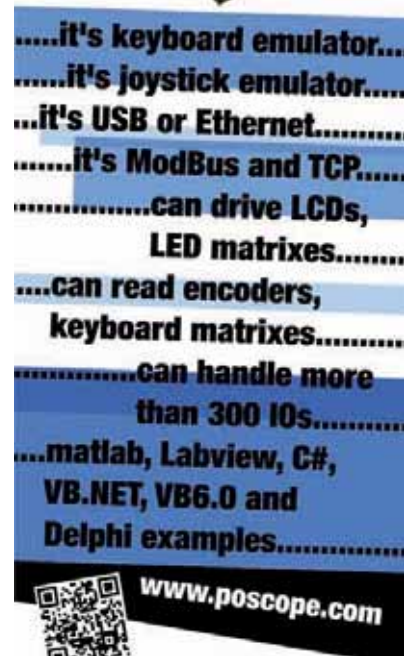Next month, we'll show you how to assemble the four PC boards and mount them in the case.



Digital Megohm and Leakage Current Meter

By JIM ROWE

Looking for an electronic megohm and leakage current meter, for quick and easy testing of insulation in wiring and equipment? Here's a new design which allows testing at either 500V or 1000V. It can measure insulation resistances up to 999M Ω and leakage currents to below 1 μ A. It uses a PIC microcontroller and displays the results on a 2-line LCD panel.

DOMESTIC and industrial equipment operating from the 230V or 400V AC power mains needs to have its insulation checked regularly, so that users can be assured that it doesn't pose a shock hazard. After all, exposure to voltages of this magnitude can be fatal!

But what sort of test gear do you need to carry out this type of safety check? You'll get a fair idea by reading the text in the 'Insulation testing' panel on the opposite page.

In a nutshell, you need a portable and isolated meter that is capable of providing a nominal test voltage of 500V or 1000V DC, and able to measure leakage current or insulation resistance or both.

Our new Megohm and Leakage Current Meter design is intended to meet these requirements. It is compact, portable and isolated and provides a choice of either 500V or 1000V DC as the test voltage.

It also allows you to measure insulation resistances from below 1M Ω up to virtually 999M Ω , as well as leakage currents from below 1 μ A to over 100 μ A (103 μ A, to be precise).

We should point out that because it can only measure leakage currents up to 103 μ A, it will indicate that Class I

equipment (with earthed external metalwork) is effectively unsafe if it has a leakage current of more than 100 μ A – even though, strictly speaking, this kind of equipment is still regarded as 'safe' providing its leakage current is below 5mA.

So the test performed by this meter is more rigorous than the official safety standards – but where safety is involved it's better to be too tough than not tough enough, surely?

The new meter is easy to build, with most of the major components mounted on a small PC board.

This fits inside a compact UB1-size plastic box, along with a small power transformer used in the test voltage generation circuit and the 4-AA battery holder used to supply the meter's power.



Warning – read this first!

- 1) This is an educational project that lets you investigate electrical safety and insulation in portable equipment. It is NOT a substitute for a professionally built and certified 'PAT' tester.
- 2) It was designed for use in Australia / New Zealand. While their requirements are very similar to the those in the UK, you cannot assume they are identical.
- 3) If you are in any doubt about the safety of a piece of equipment then you MUST get it checked professionally.
- 4) This is NOT a beginner's project – only use it if you know what you are doing or are suitably supervised.

How it works

The block diagram, Fig.1, shows what is inside the new meter. It's split into two distinct sections: the left-hand side generates the test voltage of 500V or 1000V, while the metering section on the right-hand side is used to measure any leakage current which flows between the test terminals, and from this calculates the external resistance connected between them.

In more detail, the test voltage generation section has a DC-AC inverter which converts 6V DC from the battery into AC, so it can be stepped up to a few hundred volts AC. This is fed to a voltage-multiplying rectifier circuit to produce the 500V or 1000V DC test voltage.

We use a negative feedback loop to control the inverter's operation and maintain its output voltage to the correct level. This works by using a high-ratio voltage divider (RD1 and RD2) to feed a small proportion of the high voltage DC output back to one input of comparator IC2b, where it is compared with a 2.50V voltage reference.

The comparator is then used to turn off the DC/AC inverter when the high voltage reaches the correct level and to turn the inverter on again when the voltage is below the correct level.

The basic voltage divider using RD1 and RD2 alone is used to set the high voltage level to 500V, with multiturn trimpot VR1 allowing the voltage to be set very closely to this level. To change the test voltage level to 1000V, switch S1 is used to connect RD3 in parallel with RD2, doubling the division ratio of the divider and hence doubling the output voltage maintained by the feedback loop.

Note that the inverter only operates to generate the 500V or 1000V test voltage when TEST button switch S2 is pressed and held down. As soon as the button is released, the inverter stops and the high voltage leaks away via RD1 and RD2/RD3. This is a safety feature and also a simple way to achieve maximum battery life.

Meter section

Referring back to Fig.1, the meter section is at lower right. It uses a $10\text{k}\Omega$ resistor as a 'shunt', to sense any leakage current (I_L) which may flow between the test terminals. Since the shunt has a value of $10\text{k}\Omega$, this

means that a leakage current of $100\mu\text{A}$ produces a voltage drop of 1.00V . It is the voltage across this resistor which we measure, to determine the leakage current.

First, the voltage is fed through a DC amplifier (IC2a), where it is given a voltage gain A of 3.1 times. Then it is passed to IC3, a PIC16F88 microcontroller, which is used here as a 'smart' digital voltmeter.

The amplified voltage from IC2a is fed to one input of the ADC (analogue-to-digital converter) inside the micro (IC3), where it is compared with a reference voltage of 3.2V. The digital output of the ADC is then mathematically scaled, to calculate the level of the leakage current in microamps (μA). The micro is then also able to use this calculated current level to work out the insulation resistance, because it can sense the position of switch S1 and hence 'knows' whether the test voltage being used is 500V or 1000V.

So all it has to do is calculate the total resistance, which will draw that level of leakage current from the known test voltage, and then subtract the 'internal' 10M Ω and 10k Ω resistors from this total value to find the external resistance between the test terminals. The calculated leakage current and insulation resistance values are then displayed on the LCD panel, along with the test voltage of 500V or 1000V.

The 10M Ω resistor connected between the high voltage generation circuit and the positive test terminal (ie, inside the meter), is included mainly to limit the maximum current that can be drawn from the HV generator – even in the

event of a short circuit between the test terminals. In fact it's the $10\text{M}\Omega$ resistor which limits the maximum current to $100\mu\text{A}$ with the 1000V test voltage, or $50\mu\text{A}$ at 500V .

Another function of the 10M Ω resistor is to make the meter safer to use; if you accidentally become connected between the test terminals yourself, you will get a shock, but it won't kill you. Mind you, that shouldn't happen, because you would have to be simultaneously holding down the TEST button to get a shock.

Insulation testing

Testing the insulation of mains-powered cables and equipment is an important step in ensuring that they are safe to use and don't pose a shock hazard.

According to the Australian and New Zealand standards for safety inspection and testing of electrical equipment (AS/NZS 3760:2003), tests on the insulation of 'domestic' cables and equipment operating from 230V AC should be carried out with a testing voltage of 500V DC. Similarly, the recommended testing voltage for insulation tests on 'industrial' equipment like ovens, motors and power converters operating from 3-phase 415V AC is 1000V DC.

Insulation tests on domestic 230V AC equipment can be performed by measuring either the leakage current or the insulation resistance. For Class I equipment with accessible earthed metal parts, the leakage current should be no greater than 5mA, except for portable RCDs (residual current devices) where it should not be greater than 2.5mA. The insulation resistance for these devices should be not less than 1M Ω , or not less than 100k Ω for a portable RCD.

For Class II (double-insulated) equipment, the insulation resistance with the power switch 'on' measured between the live supply conductors (connected together) and external unearthed metal parts should again be not less than 1MΩ.

The same insulation resistance figure of $1\text{M}\Omega$ applies to extension cables and power boards (between the live conductors and the earth conductor), to power packs (between the live input pins and both output connections) and also to portable isolation transformers (between the primary winding and external earthed or unearthed metal parts, between primary and secondary windings, and also between the secondary winding and external earthed or unearthed metal parts).

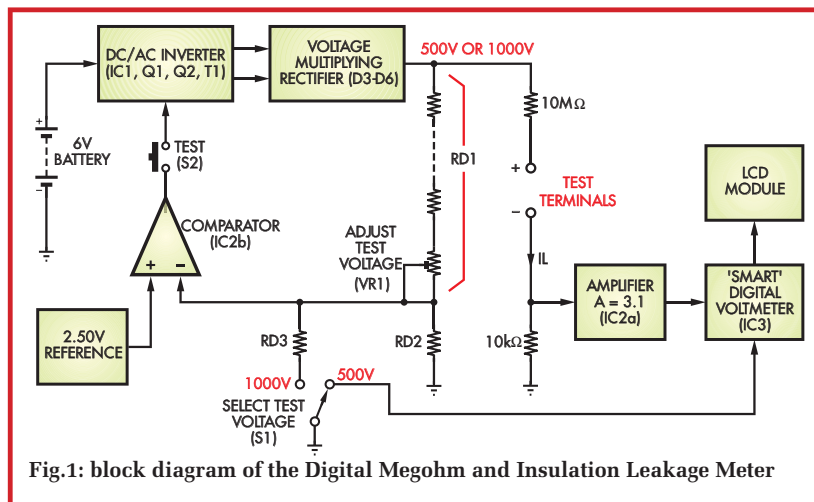


Fig.1: block diagram of the Digital Megohm and Insulation Leakage Meter

Constructional Project

As you can see from the above explanation of the way the meter's smart voltmeter works, there is no problem having the 10M Ω current limiting resistor in series with the test terminals, just as there's no problem using a 10k Ω current measuring 'shunt'. The program inside the PIC knows that both of these resistors are in series with the external resistance being measured and simply subtracts 10.01M Ω from the total resistance to find the external value.

Circuit details

The full circuit diagram for the Digital Megohm and Leakage Current Meter is shown in Fig.2. The DC/AC inverter section of the circuit uses IC1, a quad Schmitt NAND gate, to drive switching transistors Q1 and Q2. When the inverter is operating, the transistors switch about

5.6V DC alternately to either end of the low voltage winding of a standard mains transformer, T1.

This is used as a step-up to produce a much higher AC voltage to feed the voltage-multiplying rectifier comprising diodes D3 to D6 and their associated 47nF/630V capacitors.


Oscillator IC1d runs continuously at about 6kHz, and its output is inverted by IC1a and IC1c. IC1c drives inverter IC1b, while IC1a and IC1b apply the alternating signals to the bases of transistors Q1 and Q2. But gates IC1a and IC1b have their pins 2 and 6 pulled down by a common 22k Ω resistor, and so they are disabled until the TEST button (S2) is pressed.

When that happens, comparator IC2b will pull IC1a's pin 2 and IC1b's pin 6 high and the inverter will run until the

output of the voltage multiplying rectifier reaches the correct voltage level. As soon as the high voltage output reaches the correct level, the comparator's output will switch low and gates IC1a and IC1b will be turned off, stopping the inverter, even if switch S2 is still being held down. The feedback network will maintain this process as long as S2 is pressed.

The collectors (C) of Q1 and Q2 are supplied with the full battery voltage. All of the remaining circuitry in the meter operates from a regulated +5V supply line, derived from the battery via an LM2940 regulator, REG1.

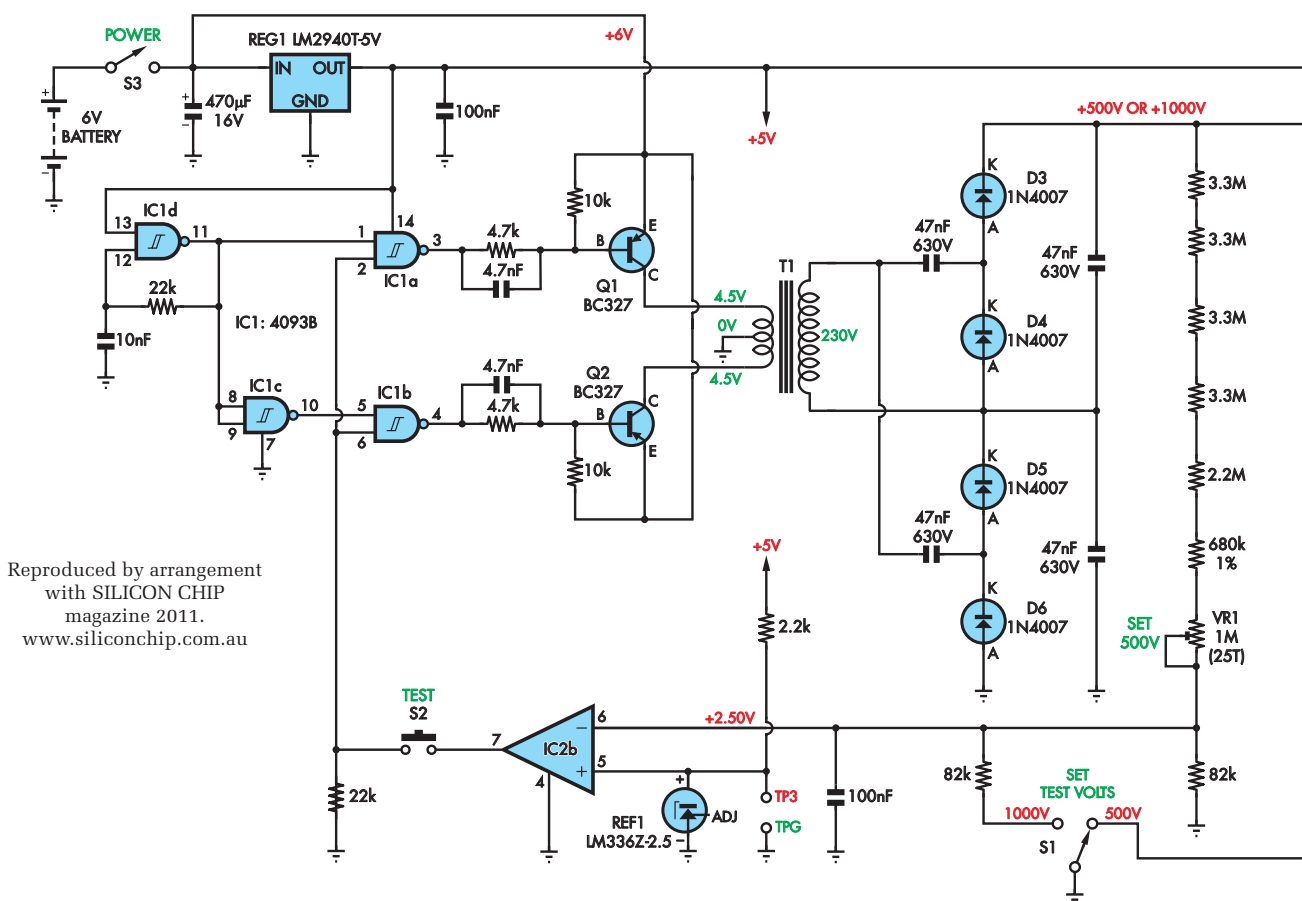The metering side of the circuit is performed by the PIC16F88 micro, IC3. The voltage developed across the 10k Ω 'shunt' resistor (in response to the current between the test terminals) is amplified by op amp IC2a, which has a gain of 3.1.



DIGITAL MEGOHM & INSULATION LEAKAGE METER

Fig.2: the circuit is essentially two parts – the left side generating the high voltage needed to perform the tests and the right side using this voltage to perform the required measurements

The amplified voltage is fed to pin 1 of IC3 (AN2) which is configured as an ADC input. The 3.2V reference voltage for the ADC is fed to pin 2 of IC3, being derived from the 5.0V supply line via the voltage divider using the 3.3k Ω , 5.6k Ω and 270 Ω resistors.

As noted before, the ADC inside IC3 measures the voltage applied to pin 1 by comparing it with the reference voltage fed to pin 2. The micro then calculates the leakage current through the test terminals.

Because it is able to sense the position of test voltage selector switch S1 (high or low) via pin 3 (RA4), it is able to deduce the actual test voltage (500V or 1000V) and hence calculate the total resistance connected across it via the test terminals. Finally, it works out the external resistance between the

terminals by subtracting the $10.01\text{M}\Omega$ internal resistance.

The calculated current and resistance values are then displayed on the LCD module, along with the test voltage being used.

In this circuit, IC3 is using its internal clock oscillator, running at very close to 8MHz. This gives an instruction cycle time of 2MHz, which may be monitored using a scope or frequency counter at test point TP2.

The micro drives the LCD module in the standard 'four-bit nibble' fashion, which involves a minimum of external components.

Trimpot VR2 allows the LCD module's contrast to be adjusted for optimum visibility, while the 22 Ω resistor connected to pin 15 sets the current level for the module's inbuilt LED back-lighting. This

was chosen as a compromise between display brightness and battery life.


Software

The software program files for the Stereo Digital Megohm and Leakage Current Meter will be available from the *EPE* website at: **www.epemag.com**

Construction

Most of the components are mounted directly on the PC board. This measures 84mm × 102mm and is coded 818. This board is available from the *EPE PCB Service*.

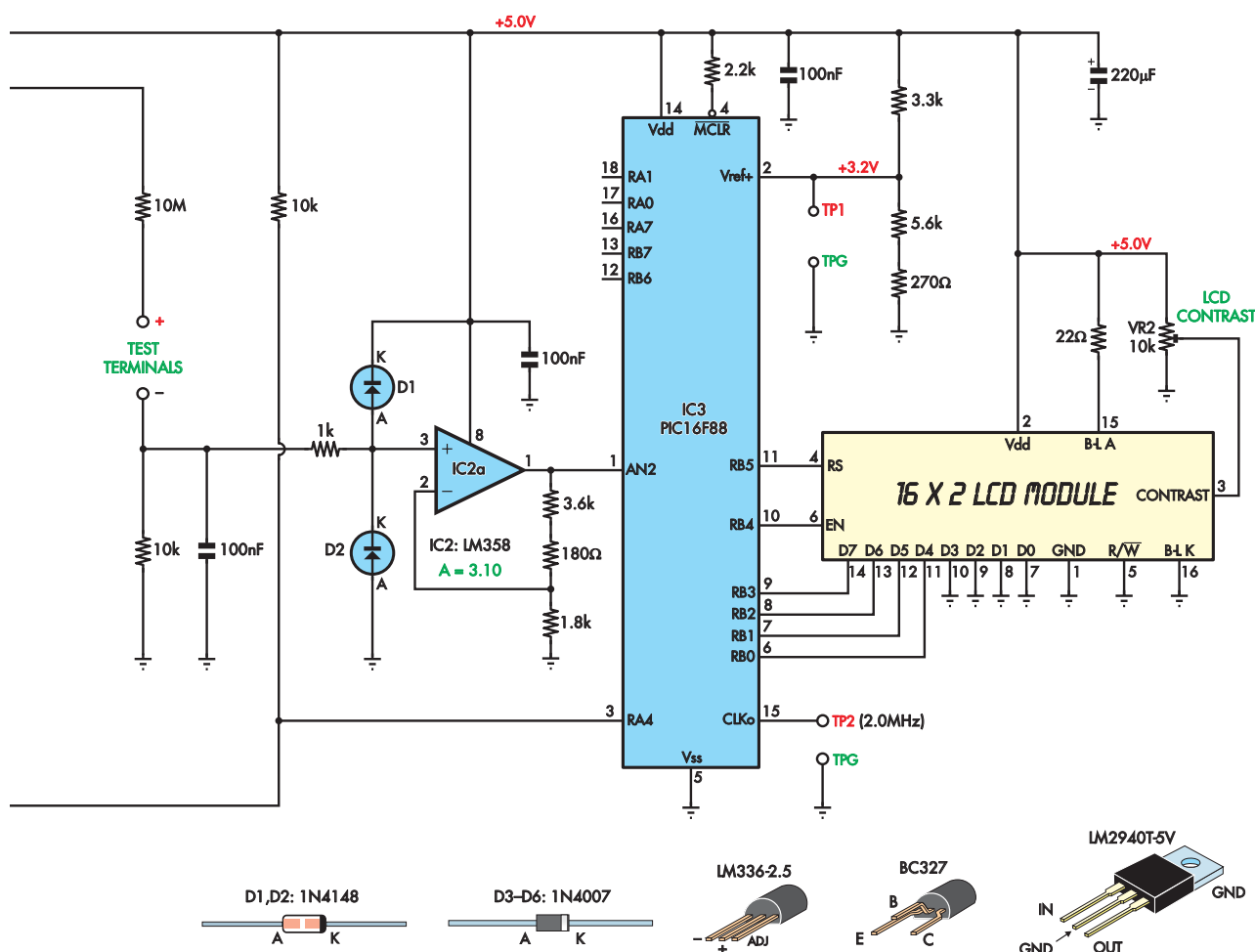The only components not mounted on the board are transformer T1 and the 6V battery holder, which are both mounted in the lower part of the case, the test terminals and switches S1 to S3. The board assembly mounts



Constructional Project

behind the lid via four 25mm long tapped spacers.

The diagram of Fig.3 shows all of the components mounted on the board, together with the wiring to the off-board transformer.

There are only two wire links to be fitted, and these are best fitted first so they won't be forgotten. One goes to the left of board centre, while the other goes just below the position for IC2. After both links are fitted you can fit the six terminal pins for test points TP1 to TP3 and their reference grounds, followed by the sockets for IC1, IC2 and IC3, taking care with their orientation.

Next, fit all of the fixed resistors, taking particular care to fit each value in its correct position. Follow these with the two trimpots, making sure you fit VR1 with the correct orientation, as shown in Fig.3.

The capacitors are next, starting with the lower value ceramic and metallised polyester caps and following these with the two polarised electrolytics – again matching their orientation to that shown in Fig.3. The 47nF 630V polyester caps can be fitted also at this stage.

Next, fit diodes D1 to D6, taking care to orientate them correctly. Make sure you fit the 1N4007 diodes in positions D3 to D6. Then install transistors Q1 and Q2, plus the LM336Z-2.5 voltage reference, REF1.

Then fit the LM2940 regulator, REG1. This TO-220 package mounts flat against

A same-size photo of the PC board, assembled and ready for mounting in the box. The two test terminals and the 'TEST' pushbutton switch are not shown here, as they mount on the front panel and connect by wires. Compare this photo to Fig.3, far right, which shows the complete component layout/wiring (in this case with the test terminals and 'TEST' switch)



the top of the board, with its leads bent down by 90° about 6mm from the body, so they pass down through the board holes. The regulator is then attached to the board using a 6mm long M3 screw and nut, passing through the hole in its tab. The screw and nut should be tightened to secure the regulator in position *before* its leads are soldered to the pads underneath.


LCD mounting

The final component to be mounted directly on the board is the 16-way

length of SIL (single in-line) socket strip, used as the 'socket' for the specified LCD module.

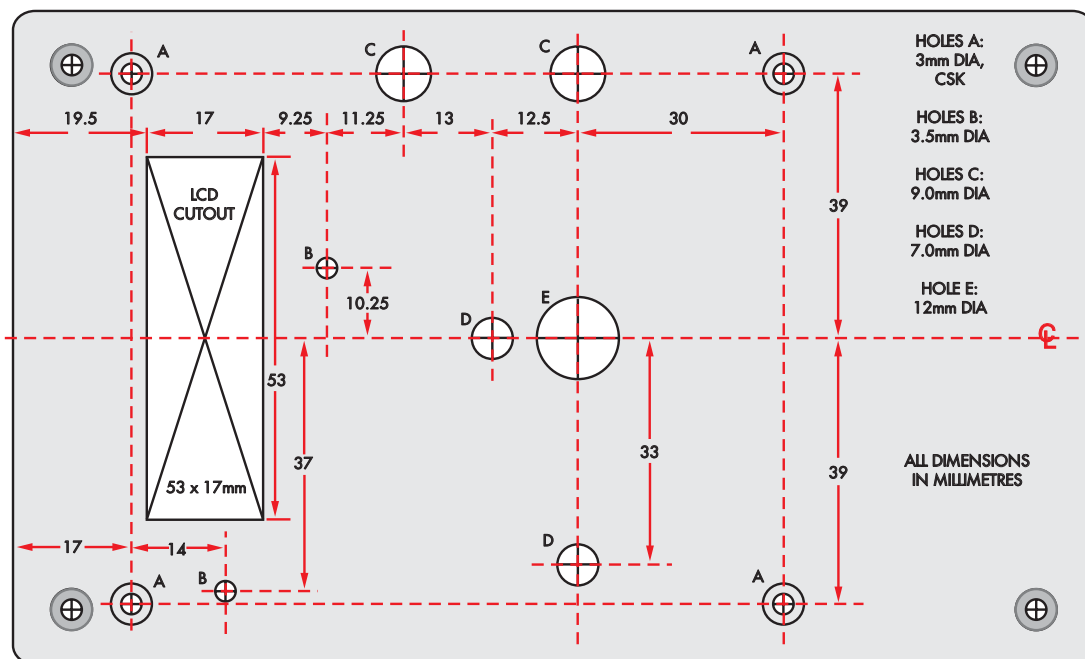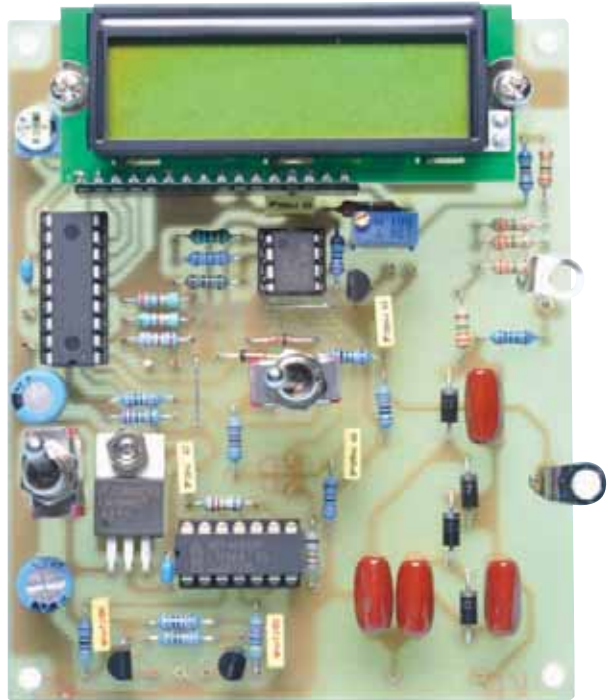Once this is fitted and soldered, you can fasten two 12mm long M3 tapped nylon spacers to the board in the module mounting positions (one at each end) using a 6mm M3 screw passing up through the board from underneath.



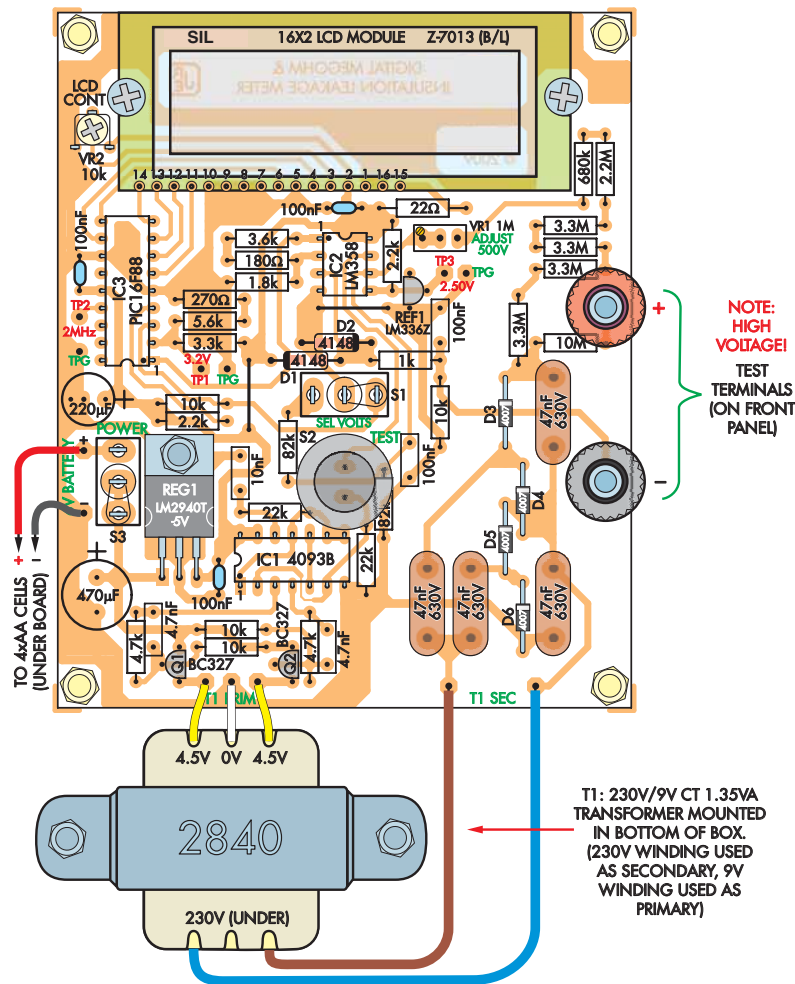

Then plug a 16-way length of SIL pin strip into the socket strip you have just fitted to the board. Make sure the longer ends of the pin strip pins are mating with the socket, leaving the shorter ends uppermost to mate with the holes in the LCD module.

Next, remove the LCD module from its protective bag, taking care to hold it between the two ends so you don't touch the board copper. Lower it carefully onto the main board so the holes along its lower front edge mate with the pins of the pin strip, allowing the module to rest on the tops of the two 12mm long nylon spacers. Then you can fit another 6mm M3 screw to each end of the module, passing through the slots in the module and mating with the spacers.

When the screws are tightened (not over tightened!) the module should be securely mounted in position.

The final step is to use a fine-tipped soldering iron to solder each of the 16 short pins of the pin strip to the copper

pads on the module, to complete its interconnections. Check that there are no shorts between pads.

After this is done, you can plug the three ICs into their respective sockets, making sure to orientate them all as shown in Fig.3.

Attach a 25mm long mounting spacer to the top of the board in each corner, using 6mm long M3 screws. Then the board assembly can be placed aside while you prepare the case and its lid.

Preparing the case

Two holes need to be drilled in the lower part of the case, to take the mounting screws for transformer T1. These should be 3mm in diameter, spaced 47mm apart and 20mm up from the end of the case, which will become the meter's lower end. The battery holder can be held securely in place using two strips of 'industrial' double-sided adhesive foam – see Fig.5 and photo.

PARTS LIST

- 1 PC board, code 818, available from the *EPE PCB Service*, size 84mm × 102mm
- 1 UB1-size plastic box, 157mm × 95mm × 53mm
- 1 LCD module, 2 lines × 16 chars, with LED back-lighting (SIL version)
- 1 power transformer, 9V CT secondary at 150mA or 1.35VA (eg 2840 type)
- 4 AA cell battery holder, flat type, with battery snap lead
- 2 mini SPDT toggle switch (S1, S3)
- 1 SPST pushbutton switch (S2)
- 2 binding post/banana jacks (1 red, 1 black)
- 2 4mm solder lugs
- 1 16-pin length of SIL socket strip
- 1 16-pin length of SIL pin strip
- 1 18-pin IC socket
- 1 14-pin IC socket
- 1 8-pin IC socket
- 4 25mm long M3 tapped metal spacers
- 2 12mm long M3 tapped nylon spacers
- 9 6mm long M3 pan-head screws
- 6 6mm long M3 machine screws, countersunk head
- 2 10mm long M3 machine screws, countersunk head
- 3 M3 nuts with star lockwashers
- 6 1mm diameter PC board terminal pins

Semiconductors

- 1 4093B quad Schmitt NAND gate (IC1)
- 1 LM358 dual op amp (IC2)
- 1 PIC16F88 programmed microcontroller (IC3)
- 1 LM2940T LDO +5V regulator (REG1)
- 1 LM336Z-2.5 +2.5V reference (REF1)
- 2 BC327 PNP transistors (Q1,Q2)
- 2 1N4148 signal diodes (D1,D2)
- 4 1N4007 1000V/1A diodes (D3-D6)


Capacitors

- 1 470mF 16V radial electrolytic
- 1 220mF 16V radial electrolytic
- 1 100nF MKT metallised polyester
- 1 100nF multilayer monolithic ceramic
- 4 47nF 630V metallised polyester
- 1 10nF MKT metallised polyester
- 2 4.7nF MKT metallised polyester

Resistors (0.25W 1% unless specified)

- | | | |
|---------------------------------------|---------|---------|
| 1 10MΩ | 1 680kΩ | 2 82kΩ |
| 2 22kΩ | 4 10kΩ | 1 5.6kΩ |
| 2 4.7kΩ | 1 3.6kΩ | 1 3.3kΩ |
| 2 2.2kΩ | 1 1.8kΩ | 1 1kΩ |
| 1 270Ω | 1 180Ω | |
| 4 3.3MΩ 5% carbon film 0.5W | | |
| 1 2.2MΩ 5% carbon film 0.5W | | |
| 1 22Ω 5% carbon film 0.5W | | |
| 1 1MΩ 25-turn trimpot, top adj. (VR1) | | |
| 1 10kΩ mini horizontal trimpot (VR2) | | |

Constructional Project

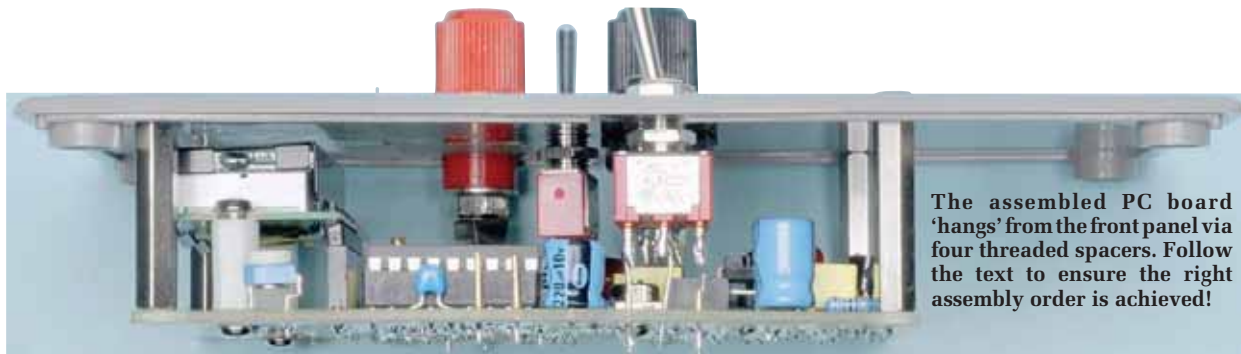

The lid needs to have a larger number of holes drilled, plus a rectangular cut-out near the upper end for viewing the LCD. The location and dimensions of all these holes are shown in the diagram of Fig.4. You can use a photocopy of it as a drilling template. The 12mm hole for S2 and the 9mm holes for the test terminals are easily made by drilling then first with a 7mm twist drill and then enlarging them to size carefully using a tapered reamer.

The easiest way to make the rectangular LCD viewing window is to drill a series of closely-spaced 3mm holes just inside the hole outline, and then cut between the holes using a sharp chisel or hobby knife. Then the sides of the hole can be smoothed using a medium file.

The artwork of Fig.6 can be used as the front panel label. This can be colour photocopied from the magazine. The resulting copy can be laminated and attached to the front of the lid (or covered with self-adhesive clear film) for protection against finger grease.

You might also like to attach a 60mm x 30mm rectangle of 1mm to 2mm thick clear plastic behind the LCD viewing window, to protect the LCD from dirt and physical damage. The 'window pane' can be attached to the rear of the lid using either adhesive tape or epoxy cement.

Once your lid/front panel is finished, you can mount switches S1 to S3 on it using the nuts and washers supplied with them. These can be followed by the binding post terminals. Tighten the binding post mounting nuts quite firmly, to make sure that they don't come loose with use. Then use each post's second nut to attach a 4mm solder lug to each, together with a 4mm lockwasher to make sure they don't work loose either.


Now you can turn the lid assembly over and solder 'extension wires' to the connection lugs of the three switches and to the solder lugs fitted to the rear of the binding posts. These wires should all be about 30mm long and cut from tinned copper wire (about 0.7mm diameter). Once all of the wires are attached, they should be dressed vertical to the lid/panel so they'll mate with the corresponding holes in the PC board, when the two are combined.

Next, mount transformer T1 at one end of the case, with its low voltage winding connections towards the top and the high voltage connections towards the bottom, as in Fig.5. Secure the transformer in position using two 10mm-long M3 machine screws with flat washers, star lockwashers and M3 nuts, tightening both firmly to make sure the transformer cannot work loose.

The 4-AA cell battery holder can also be mounted in the upper end of the case using double-sided adhesive foam, with its battery snap connections at the lower end.

Next, solder the bared ends of the battery clip lead wires to their connection pads on the PC board, just to the left of the position for power switch S3. The leads from transformer T1 can also be connected to the connection pads along the lower edge of the PC board, with the three low voltage winding leads connecting to the pads on the left and the two high voltage winding leads to the pads on the right, as shown in Fig.3.

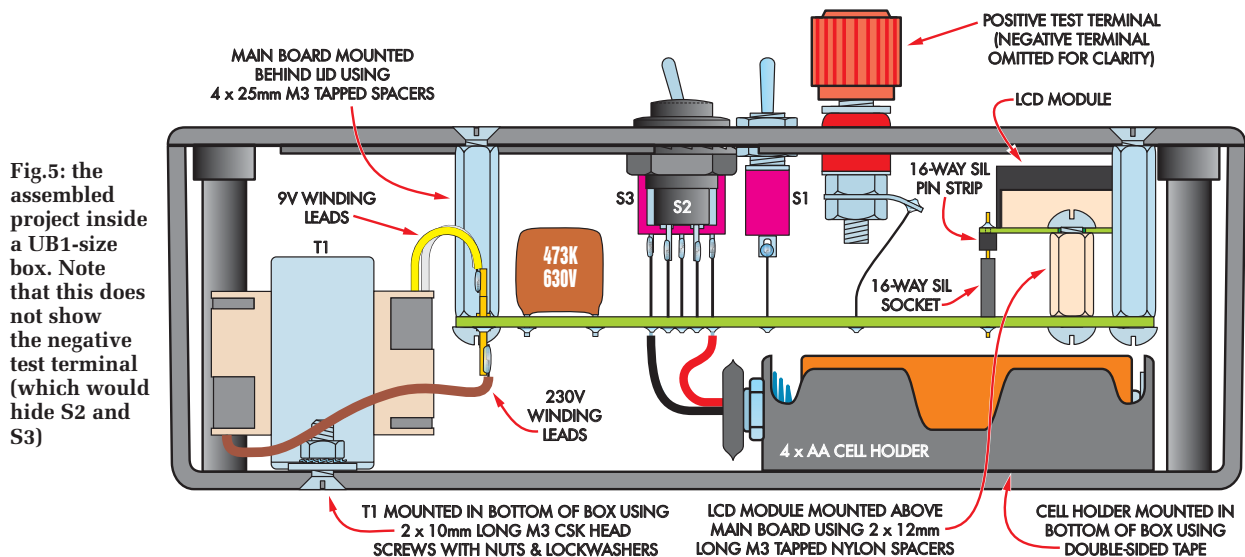Now you can attach the PC board assembly to the rear of the lid/front panel. You have to line up all of the extension wires from switches S1 to S3 and the two test terminals with their matching holes in the PC board, as you bring the lid and board together. Then you can secure





Here's how it all fits together inside a UB1 box. The power transformer and battery holder are the only components not mounted on the PC board

the two together using four 6mm long countersink head machine screws.

Next, turn the complete assembly over and solder each of the switch and terminal extension wires to their board pads. Fit four AA alkaline cells into the battery holder and your new Megohm/Insulation Meter is ready for its initial checkout.

Initial checkout

If you set switch S3 to its ON position, a reassuring glow should appear from the LCD display window – from the LCD module's back-lighting, and you should also see the meter's initial greeting 'screen'. You may need to adjust contrast trimpot VR2, until you get a clear and easily visible display. (VR2 is adjusted through the small hole just to the left of the LCD window.)

After a few seconds, the LCD should change to the meter's measurement 'screen', where it displays the current test voltage setting, together with the measured leakage current and resistance (as shown in the opening photograph).

At this stage, it will show a leakage current of $000\mu\text{A}$ and a resistance of $999\text{M}\Omega$, for two reasons: (1) because the test voltage isn't actually generated until you press the TEST button and (2) you haven't connected anything between the two test terminals at this stage, to draw any current.

Just to make sure though, try switching voltage selector switch S1 to the other position. You should find that the test voltage setting displayed on the top line of the LCD screen changes to match. If so, it will show that your Digital Megohm and Insulation Meter is working correctly.

This being the case, switch off the power and complete the final assembly by lowering the lid/PC board assembly into the case and securing the two together using the four small self-tapping screws supplied.

Setting the test voltages

The test voltage levels are set with trimpot VR1. This is adjusted via a small screwdriver through the small hole just below the LCD window. But how do we get the meter

to measure the test voltages itself? Simply by connecting a short piece of wire between the two test terminals, as a short circuit. This temporarily changes the meter into a 0-1000V voltmeter, to read the test voltage on the leakage current range.

So, to set the test voltages, fit the shorting wire between the test terminals and then switch S1 to the '1000V' position. Then switch the meter on, and once it is displaying the measurements screen press and hold down the TEST button (S2). The LCD should show a 'current' of close to $100\mu\text{A}$, corresponding to a test voltage of 1000V. If it indicates a figure either higher or lower than this, all you have to do is adjust trimpot VR1 with a small screwdriver until the reading changes to $100\mu\text{A}$ (=1000V).

To make sure that you have made the setting correctly, try switching voltage selector switch S1 to the '500V' position. You should find that the LCD reading changes to $50\mu\text{A}$ (=500V). If so, your meter is now fully set up.

Remove the short circuit between the test terminals and your meter is ready for use.

EPE


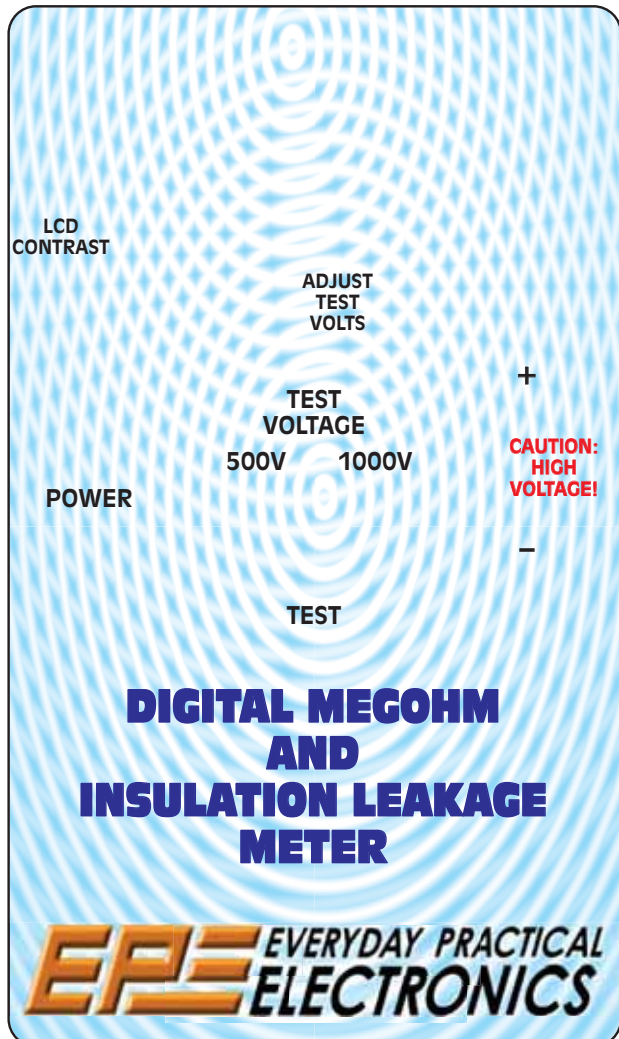


Fig.6: same-size artwork for the front panel. This does not have the hole positions shown, so all screws are hidden once it is glued in place

Integrated Circuits

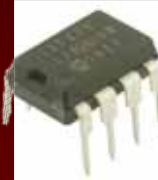

Microchip® PIC Microcontrollers

We stock a large range of popular Microchip® Microcontrollers at highly competitive prices, here is just a small selection of our range.

	Product Code	Price
Microchip PIC12F675-I/P Microcontroller	YC4-061	£0.98
Microchip PIC12F683-I/P Microcontroller	YC4-070	£1.07
Microchip PIC16F54-I/P Microcontroller	YD4-032	£0.68
Microchip PIC16F628A-I/P Microcontroller	YD4-061	£1.72
Microchip PIC18F690-I/P Microcontroller	YD4-109	£1.89
Microchip PIC16F84A-04/P Microcontroller	YD4-149	£3.89
Microchip PIC16F877A-I/P Microcontroller	YD4-175	£4.85
Microchip PIC18F252-I/SP Microcontroller	YE4-021	£5.27



Microchip® PIC Development Kits

From our range of the most popular development kits and programmers from Microchip®.

	Product Code	Price
Microchip PICkit 1 Flash Starter Kit	YA4-010	£29.99
Microchip PICkit 2 Flash Starter Kit	YA4-032	£42.99
Microchip PICkit 2 Programmer	YA3-025	£29.99
Microchip PICkit 3 Debug Express	YA3-046	£53.99
Microchip PICkit 3 Debugger/Programmer	YA4-051	£39.99
Microchip Low Pin Count USB Kit	YA3-068	£41.99
Microchip Low Pin Count USB + PICkit 2	YA4-077	£58.99



Atmel® Microcontrollers

Our range of Atmel® Microcontrollers are designed for high performance with high power efficiency in a small package.

ATtiny	Product Code	Price
Atmel ATTINY13-20PU	YF4-012	£1.39
Atmel ATTINY24-20PU	YF4-022	£1.85
Atmel ATTINY26-16PU	YF4-039	£1.98
Atmel ATTINY2313-20PU	YF4-043	£1.98

ATmega	Product Code	Price
Atmel ATMEGA48-20PU	YG4-014	£1.91
Atmel ATMEGA8-16PU	YG3-020	£2.52
Atmel ATMEGA8515-16PU	YG4-033	£2.96
Atmel ATMEGA16-16PU	YG4-047	£5.02
Atmel ATMEGA168-20PU	YG4-058	£3.23
Atmel ATMEGA32-16PU	YG4-064	£5.75
Atmel ATMEGA32L-8PU	YG4-075	£5.75



Logic ICs

We offer extensive ranges of standard logic in 4000, 74LS, 74HC and 74HCT formats.

	Prices From
4000 Series Logic	£0.18
74HC Series Logic	£0.14
74HCT Series Logic	£0.19
74LS Series Logic	£0.21

Switches & Relays



Push Button Switches

Extensive ranges of all different types of push button switches suitable for most applications.

	Prices From
Miniature Push Button Switches	£0.25
0.5A Square Push Switches	£0.46
1A Square Push Switches	£0.45
Ultra Miniature Push Button Switches	£0.44
Miniature Latching Push Switches	£0.71
Push Fit Button Switches	£0.98
Panel Mounting Push Switches	£1.09
Panel Mounting Latching Switches	£1.44
Low Profile Push Switches	£0.39
Latching Dome Push Switches	£0.56
Latching Push Switches with LEDs	£1.05
Circular Push-Pull Switches with LEDs	£1.40
Chrome Bezel Push Switches	£0.87



Toggle Switches

We offer ranges of switches for PCB and Chassis mounting in all sizes and contact configurations.

	Prices From
Standard Toggle Switches	£0.59
Miniature Toggle Switches	£0.60
Miniature Right Angle Toggle Switches	£0.88
Round LED Tipped Toggle Switches	£1.98
Metal Tumble Switches	£1.12

To purchase components for your
EPE Project
visit our dedicated page at...
spiratronics.com/epe

PCB, Hardware & Enclosures



PCB Prototyping Boards

We carry ranges of Circuit Boards ideal for experimenting, prototyping and building electronics projects.

	Prices From
Stripboard	£0.29
Plugblock Prototyping Board	£1.94
Matrix Board	£1.53



ABS Project Boxes

Listed are just a few of our wide range of enclosures suitable for housing all types of electronics projects.

	Dimensions (L x W x H mm)	Product Code	Price
Black ABS Box	75 x 50 x 25	HQ3-017	£1.43
Black ABS Box	110 x 56 x 20	HQ3-021	£1.98
Black ABS Box	100 x 75 x 40	HQ3-033	£2.12
Black ABS Box	150 x 100 x 55	HQ3-041	£4.17
ABS Project Case with LED Cut Out	87 x 59 x 31	HL3-017	£1.77
ABS Project Case with Aluminium Lid	83 x 53 x 35	HM3-013	£1.83

Resistors & Potentiometers



Resistors

We offer fixed resistors in Metal Film, Carbon Film and Wirewound formats for varying size, tolerance, accuracy and power rating trade off.

	Prices From
0.5W Carbon Film Resistors	£0.39 pack of 10
0.25W Metal Film Resistors	£0.39 pack of 10
0.6W Metal Film Resistors	£0.39 pack of 10
2W Metal Film Resistors	£0.10 each



Potentiometers

We have extensive ranges of both board-level and chassis mounting potentiometers on offer at everyday low prices.

	Prices From
16mm Potentiometers	£0.57
24mm Potentiometers	£0.84
Slide Potentiometers	£1.01
Carbon Preset Potentiometers	£0.12
Horizontal Enclosed Presets	£0.24
Vertical Enclosed Presets	£0.24
6mm Cermet Trimmer Potentiometers	£0.17
1/4" Multiturn Cermet Potentiometers	£0.98
3/4" Multiturn Cermet Potentiometers	£0.50

Sensors, Sounders & Motors



Sensors

We offer ranges of sensors from basic tip, tilt and vibration sensors through to application specific devices such as liquid and humidity sensors.

	Product Code	Price
Humidity Sensor	XQ2-019	£0.71
Horizontal Movement Sensor	XJ3-014	£0.91
Vertical Movement Sensor	XJ2-028	£0.91
Liquid Sensor	XM1-016	£3.38
Float Switch	XN1-013	£5.52
Horizontal Liquid Level Sensor	XP3-016	£8.49
PIR Module	XK1-018	£7.89

Cable & Wire



Equipment Wire

We offer ranges of differently coloured and configured cable suitable for most interconnection applications.

	Options	Price
1/0.6mm Single Core Equipment Wire	Choice of 11 Colours	£0.56 per 5 Metres
16/0.2mm Single Core Equipment Wire	Choice of 8 Colours	£0.65 per 5 Metres
Kynar Wrapping Wire	Choice of 8 Colours	£0.27 per Metre
Nickel Chromium (Nichrome) Wire	14SWG - 32SWG	From £0.35 per Metre



Ribbon Cable

Our range includes economically priced grey and coloured ribbon cable for multi-pole interconnection.

	Prices From (per metre)
Grey Ribbon Cable	£0.42
Rainbow Ribbon Cable	£1.01

Discrete Semiconductors

Diodes

We offer most popular ranges of signal & power diodes in addition to bridge rectifiers and other discrete semiconductors.

Prices From

Schottky Barrier Diodes	£0.07
Schottky Power Diodes	£0.19
500mW Zener Diodes	£0.26 pack of 5
1.3W Zener Diodes	£0.08
5W Zener Diodes	£0.28
1A Rectifier Diodes	£0.38 pack of 10
2A Rectifier Diodes	£0.60
3A Rectifier Diodes	£0.45
6A Rectifier Diodes	£0.41
1A Bridge Rectifiers	£0.21
1.5A Bridge Rectifiers	£0.27
4A Bridge Rectifiers	£0.35
6A Bridge Rectifiers	£0.52
35A Bridge Rectifiers	£1.27

Transistors

We offer large ranges of both NPN and PNP transistors in all power ranges.

Prices From

Low Power NPN	£0.05
Low Power PNP	£0.05
Medium Power NPN	£0.13
Medium Power PNP	£0.28
High Power NPN	£0.22
High Power PNP	£0.18
MOSFETs	£0.18
Programmable Unijunction Transistor	£0.24

Connectors

PCB Headers & Interconnects

From our range of products providing a solution to PCB interconnection needs.

Prices From

Single Row Headers	£0.06
Double Row Headers	£0.08
Right Angle Headers	£0.07
Single Row Header Sockets	£0.06
Jumper Links	£0.10

Optoelectronics

Standard Diffused LEDs

Our standard ranges of diffused LEDs offer excellent value for money for applications where a relatively low power indication is required.

Size Product Code Price (Pack of 5)

Red	3mm or 5mm	-	£0.34
Green	3mm or 5mm	-	£0.37
Yellow	3mm or 5mm	-	£0.37
Blue	5mm	LC2-046	£0.87
White	5mm	LC2-056	£0.87

LED Numeric Displays

Our range includes extensive options for digit height, digit colour, connection configuration and number of digits.

Prices From

7.6mm (0.3") Display	£0.54
9.9mm (0.39") Display	£0.70
10.2mm (0.4") Display	£0.42
14.2mm (0.56") Display	£0.42
14.2mm (0.56") Dual Display	£0.96
25.4mm (1") Display	£0.90

Multi-Colour LEDs

Ranges of bi-colour, tri-colour and multi-colour LEDs offered in various packages at low prices.

Prices From

Bi-Colour 3mm LEDs	£0.19
Bi-Colour 5mm LEDs	£0.19
High Brightness Tri-Colour 3mm LEDs	£0.44
Tri-Colour 5mm LEDs	£0.15
Tri-Colour 8mm LEDs	£0.25
Tri-Colour 10mm LEDs	£0.25
PCB Mounting Tri-Colour 5mm LEDs	£0.24
3mm Red/Blue Flashing LEDs	£0.38
RGB Full Colour LEDs	£0.41

High Brightness LEDs

Spiratronics offer LEDs in all sizes from 1.8mm to 20mm and in varying intensities, viewing angles and package types.

Prices From

Ultrabright 3mm LEDs	£0.13
Ultrabright 5mm LEDs	£0.13
Ultrabright 8mm LEDs	£0.14
High Intensity 10mm LEDs	£0.15
High Intensity 20mm LEDs	£0.90

FREE GIFT
with orders over £25

visit us at...
spiratronics.com
for full details

Tools, Storage & Service Aids

Tools

A selection of products from our tool range offering carefully selected items to support you in the construction of your project.

Product Code Price

IC Extraction Tool	TF2-018	£1.09
IC Extraction/Insertion Tool	TG3-017	£1.79
IC Straightener Tool	TH2-013	£3.79
Antex 18W Soldering Iron	TJ2-016	£17.99
Antex 25W Soldering Iron	TJ2-028	£17.99
Solder Tube	TK1-019	£3.79
Solder Reel (500g)	TL2-014	£16.85

Professional Digital Multimeter

A ruggedised 3½ digit digital multimeter offering unbelievable quality and thirty two range specification at an incredibly low price.

Product Code Price

Professional Digital Multimeter	CD3-011	£17.99
---------------------------------	---------	--------

Our service...

- Low cost, high quality products
- Same day dispatch on orders before 3pm
- Low, flat postage cost (£1.49 for UK) on all orders with no minimum order value



visit us at...
spiratronics.com
for our comprehensive range

Spiratronics

A Deluxe 3-channel UHF Rolling Code Remote Control

Part 2 – by John Clarke

Last month, we introduced our new high security remote control and got as far as completing both the receiver/relay driver and transmitter. This month we'll put it all together and get the two parts talking to each other – securely!

WE'RE ASSUMING that you've completed construction, including setting the transmitter and receiver identities, as detailed last month. You will also have given both PC boards a visual check and made sure that there are no solder bridges (except the deliberate ones in the transmitter identity!) or breaks, bad joins or errors.

Testing

With IC1 out of its socket, connect a 12V plugpack or other 12V supply via the power socket. Check that LED5 lights and that there is about 5V between pin 5 and pin 14 of the IC1 socket. The voltage could range from 4.85V to 5.15V.

If this is correct, switch off power and plug in IC1. Place the LK1 jumper link in the 'out' position and rotate VR1, VR2 and VR3 fully anticlockwise to set the momentary period at minimum.

Apply power and press switches S1, S2 and S3. This should activate RELAY1, RELAY2 and RELAY3 for about a quarter of a second each, with LED1, LED2 and LED3 lighting up during this period. If this test is OK, you can assume the circuit is working correctly. Now it's time to set the operation of the relays.

Momentary or toggle

Note that while we have made two of the relay 'NC' connections available, these may not be of much use in the momentary mode. However, they could be quite useful in the toggle mode.

Setting the relays for momentary or toggle mode is done in this



We presented construction details for the two PC boards last month. Here's what our completed project looks like. The panel on the receiver is actually an overhead projector transparency glued to the inside of the lid, so you can see the LEDs inside the case

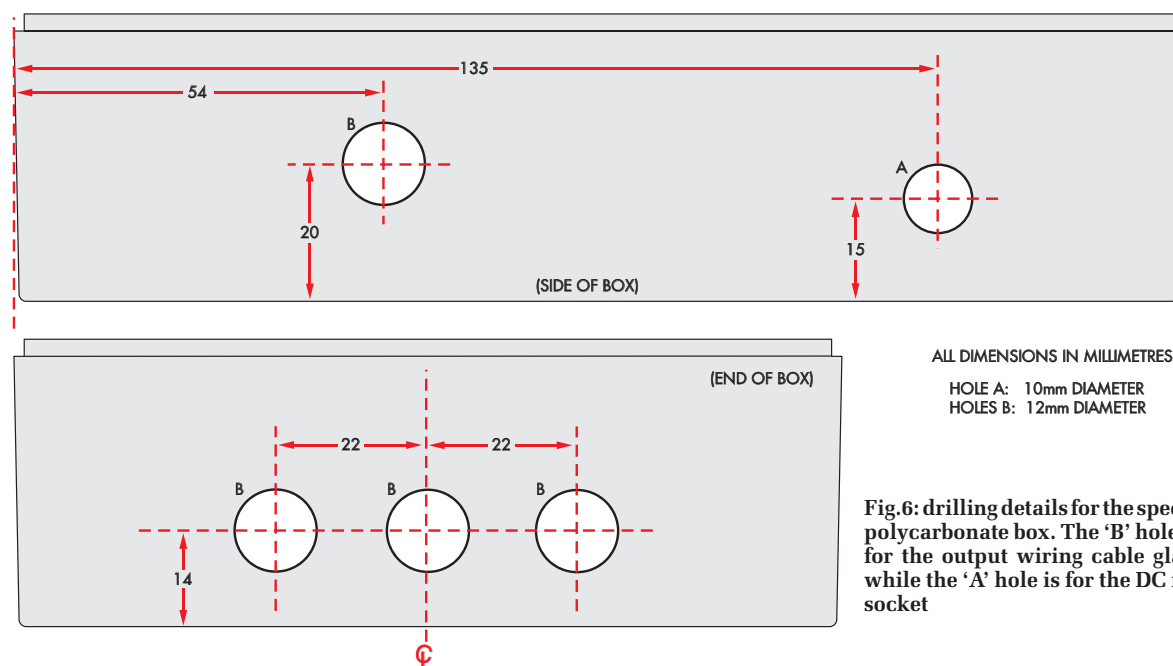


Fig.6: drilling details for the specified polycarbonate box. The 'B' holes are for the output wiring cable glands, while the 'A' hole is for the DC input socket

way. Place the LK1 jumper in the 'in' position. Set BCD1 switch to the number of the relay that you wish to change operation. Then press S2 momentarily. (Do not press S1 or you will lockout the transmitter with the identity number that is set on BCD1 instead). For example, if you want RELAY1 to be changed from momentary to toggle operation, set BCD1 to position 1. Then press S2. Now you can place the LK1 jumper in the 'out' position and by pressing S1 you will have RELAY1 operating in the toggle mode.

To revert to momentary mode, place LK1 in the 'in' position, set BCD1 to '1' and press S2 again. Placing LK1 in the out position and pressing S1 will show that RELAY1 now operates in momentary mode.

Momentary period

Momentary period for each of the relays is set with its associated trimpot (ie, RELAY 1 is set by VR1; RELAY2 by VR2 and RELAY3 by VR3). Periods are adjustable from 0.26s to 2s in 0.26s steps, then in 1s steps to 10s and in 15s steps to 4.4 minutes. Table 2 shows a sample of the settings available and the approximate voltage that is measured at the trimpot test points for various timeouts. The voltages can be measured between TP GND and the appropriate test point (TP1, 2 or 3) for VR1, VR2 and VR3 respectively.

If you want only short timeouts, it is easier to simply experiment with the position of the trimpot for the desired timeout. For longer timeouts, you will save time in finding the right setting for the trimpot by measuring the voltage and comparing this to the timeouts from Table. 2.

Note that the minimum period of 0.26s will be set for the first 10° to 20° of trimpot movement clockwise from its fully anticlockwise point. This is done so that it will be possible to finely set the increments of 0.26s at the lower end of travel. Trimpots tend to jump in value at their travel extremes, and having this dead band of operation moves

any changes in time settings into the more linear section of the trimpot.

At this stage, if the transmitter identity is '0', pressing the switches on the transmitter should activate the relays on the receiver. This is only if you have not used the randomise function on the transmitter. Also, the transmitter needs to be at least 1m from the receiver to work correctly – any closer may overload it. If you have activated the randomise function on the transmitter, then you will need to register the transmitter – see the registering section.

Randomising

Randomisation of the transmitter ensures that it uses a unique set of parameters to calculate the rolling code. This procedure is a vital step in ensuring security because the default parameters are the same for every transmitter.


You need to personalise the parameters to prevent another transmitter that has the same identity from possibly operating your receiver. If randomisation is not done, there is the risk that someone else's transmitter that also has not been randomised will operate your receiver.

To randomise a transmitter, simply connect the jumper shunt into the LK1 position. The transmit LED will flash at a four per second rate for the duration. Wait for a short period (say several seconds to a few minutes) then remove the jumper. To prevent losing the jumper, it can be stored in the 'keeper' position when finished.

Parameters are altered every 40μs, that is 25,000 times per second, so they will end up being different for each transmitter. The randomisation relies on the fact that it would be impossible to randomise two transmitters over exactly the same period by plugging and unplugging the jumper plug to within 40μs of the same period.

Add this to the fact that we do not specify a particular period to run the randomisation (as we leave this up to each individual person); a unique set of rolling code parameters is ensured.

Constructional Project

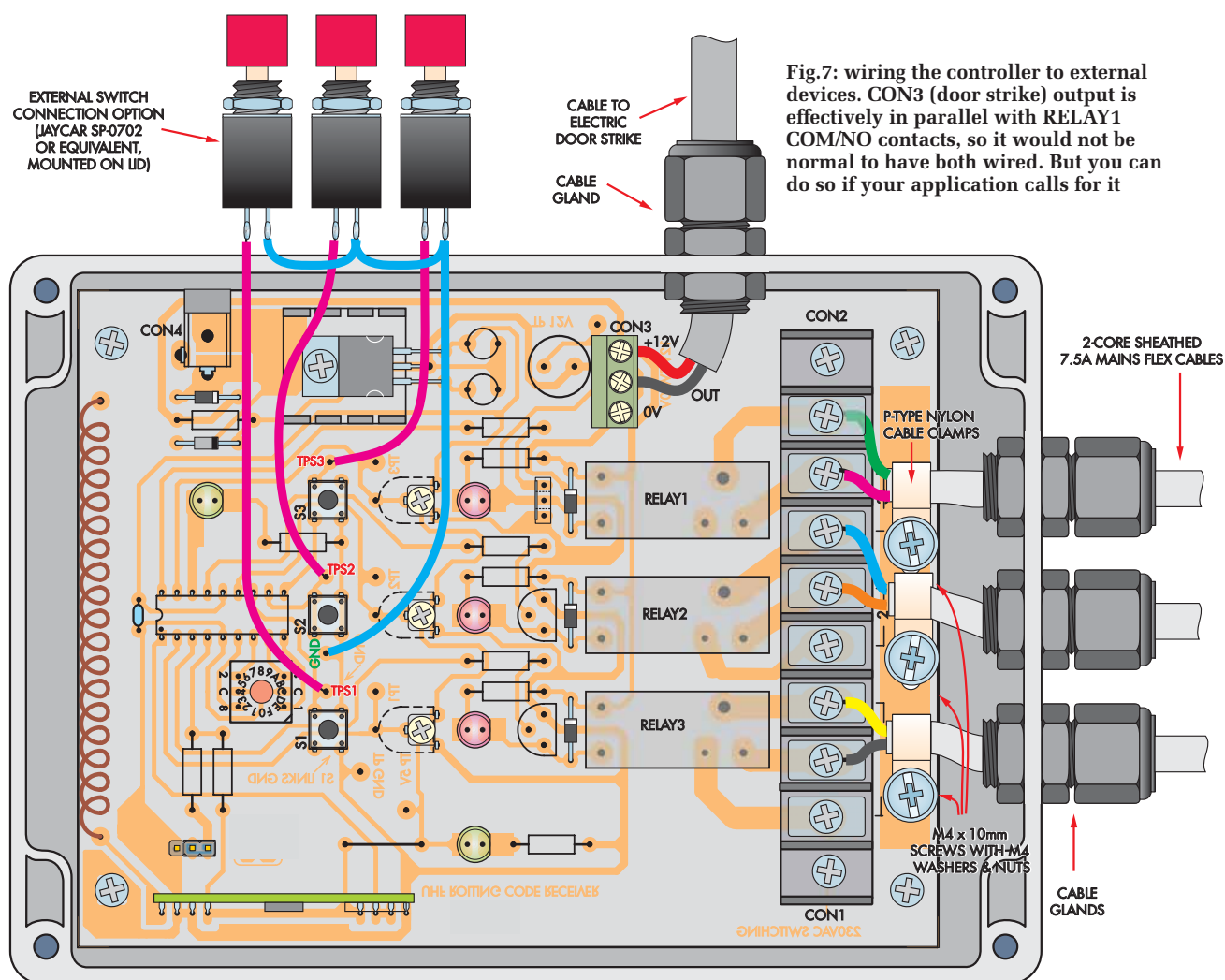

Registering

After randomisation, the transmitter needs to be registered with the receiver in order to work. Both transmitter and receiver must be readied for this. Place the transmitter jumper in the LK2 position and at the receiver, place the LK1 jumper in the 'in' position. Now press and hold S3 on the receiver and then momentarily press S3 on the transmitter (with the transmitter about 1m away from the receiver).

The acknowledge LED on the transmitter will flash twice and the receiver's acknowledge LED should then flash on and off at a one-second rate until S3 on the receiver is released. This one-second flashing is an indication that the registration process has been successful.

If the LED does not flash, then registration was unsuccessful, so try again. Release S3 on the transmitter and receiver, then press and hold S3 on the receiver again and momentarily press S3 on the transmitter.

If the registration process still fails, try re-randomising the parameters and then register again.

The randomisation and registering procedure must be done for each new transmitter. Note that registering a transmitter will prevent the use of a previously registered transmitter if it has the same identity. For this reason, transmitters need to have their own identity. A different identity transmitter

can be registered with the receiver without affecting the registration of the other transmitter.

Testing transmission


If registration was successful, the LK2 jumper can be removed from the transmitter and placed in the keeper position. Switch S3 on the receiver should by now be released. The receiver is now ready to respond to the transmitter on the second press of one of the transmitter switch buttons. Pressing a switch on the transmitter for the second time should activate the corresponding relay on the receiver. It should activate the relay on each successive press of a switch thereafter.

Lockout

Any transmitter that has been synchronised can be later locked out from operating the receiver. To do this, insert link LK1 on the receiver in its 'in' position. Then set BCD1 to the identity number of the transmitter you wish to lockout. Note again that the A, B, C, D, E and F positions on BCD1 are the 10, 11, 12, 13, 14 and 15 identities. Press S1 and the acknowledge LED will light once for one second. Then it will flash briefly for about 0.25s a number of flashes equal to the identity number.

For identity 0, only the one-second flash will not occur because the identity is zero and so does not briefly

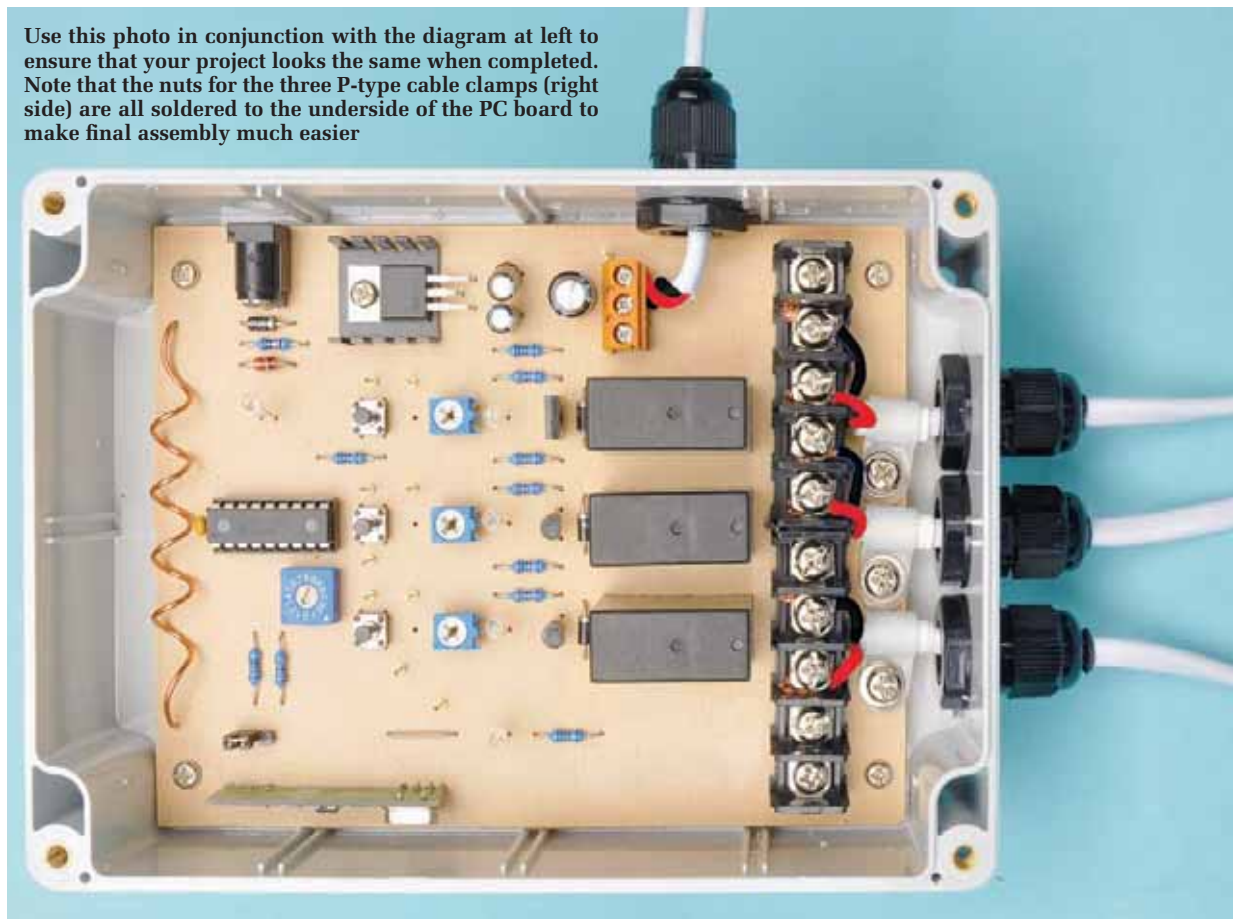Use this photo in conjunction with the diagram at left to ensure that your project looks the same when completed. Note that the nuts for the three P-type cable clamps (right side) are all soldered to the underside of the PC board to make final assembly much easier



flash. Put another way, for identity 0, the LED does flash but for zero times. After flashing the identity number, the LED will remain off for three seconds. If switch S1 is held pressed, the cycle of displaying a one-second flash and then the identity number will occur again. This cycle will occur only for three times, as S1 is kept held pressed. After this, if S1 is still held pressed, the LED will then stay lit. This 'stay lit' indication means that now all identities are locked out.

When all identities are locked out, re-registration will be necessary for each transmitter that is in use.

Transmitter case

Switch caps supplied with the 'keyfob' transmitter case are designed to fit over the switch actuators of S1 to S3. You may find that when the lid of the keyfob case is in place, the switches are already pressed. Note also that IC1 must be pressed fully into its socket so that S1 can be operated.

The top of each switch actuator may need to be shortened by a very small amount so the switch is not depressed when the lid is in place. Take care with filing down the actuator so you do not remove too much. If you do remove too much, the switch will not work, as the switch cap will touch the switch body before the actuator is pressed. To solve this, the bottom of the switch cap can be filed to prevent it touching the switch body.

A translucent light pipe diffuser is supplied with the case, and is inserted into the hole in the top of the lid. The rounded triangular wire for a keyring attachment is placed in the case lid at the battery end of the case. A self-tapping screw holds the lid secure at the battery end of the case.

To open the case, remove the self-tapping screw and take off the battery cover compartment by prising at the holes where the keyring attaches. The lower half of the case is removed by squeezing the sides of the top half of the case to release the catches from the base.

Receiver in its box

Using Fig.6 as a guide, mark out and drill the holes in the side of the box for the four cable glands and the power lead connector. At this stage, you can also drill the holes for the four cable glands, but don't put any wire in yet.

The PC board is secured in the box using the integral corner pillars. These accept M3 x 10mm screws.

While the three on-board switches will generally not be needed once setup is finished, some constructors may wish to fit external switches, so that the relays can be activated without the keyfob transmitter (ie, a 'local' mode). In fact, external switches can completely replace the on-board switches.

In this case, momentary push-to-close switches can be installed onto the lid or side of the case and wired as shown

Table 2: Momentary period settings

Momentary period settings for VR1, VR2 and VR3 with voltages as measured at TP1, TP2 and TP3 respectively.	TESTPOINT VOLTAGE (V)	TIMEOUT
Timeout periods are adjustable in 0.26s increments to 2s, then in 1s increments from 5 to 10s. Adjustments in 5s increments are made above 10s. Not all available timeout periods are shown in the table. You would need to interpolate the values for other timeouts. For example, to set for 2.5 minutes adjust the trimpot to between 2.79V (2 minutes) and 4V (3 minutes). A 3.4V setting should be close enough for 2.5 minutes timeout.	0 to 0.18	0.26s
	0.26.....	0.52s
	0.34.....	0.78s
	0.41.....	1.04s
	0.49.....	1.3s
	0.57.....	1.56s
	0.65.....	1.82s
	0.73.....	2.0s
	0.81.....	3s
	0.88.....	4s
	0.97.....	5s
	1.36.....	10s
	1.44.....	15s
	1.68.....	30s
	1.92.....	45s
2.15.....	60s	
2.47.....	90s	
2.79.....	2 minutes	
4	3 minutes	
5	4 minutes	

in Fig.7 to TPS1, TPS2, TPS3 and GND PC stakes. A suitable switch is the Javcar SP-0702.

If you decide not to install S1, S2 and S3 on the PC board because you are placing switches on the lid, note that the ground track on the PC board is connected via the lower two bridging terminals of switch S1. Removing S1 will mean you need to place a horizontal wire link between the lower two horizontal holes left after removing the switch. Switches S2 and S3 positions do not require any links. A note to this effect concerning S1 is located on the underside of the PC board.

Wiring into equipment

For an electric door strike, which is usually rated at less than 1A, you can use CON3 to directly drive the strike with 12V. The wires pass through a cable gland in the side of the box.

The relays are provided for switching 230V AC mains to power lights, door motors etc. The relays do not supply any power – they can simply be regarded as a switch. If controlling a light, for example, the pair of wires from each relay (common and NO (normal open)) are simply wired across the light switch. For two-way light switching, the common, NO and NC (normal closed) contacts would need to be used. These three contacts are available for outputs from Relay 1 and Relay 2.

If you want to control a garage door, you would wire across the pushbutton switch 'local' door control switch, Fig.8 shows how this is done. The pushbutton switch almost invariably controls a low-voltage circuit (hence you can use bell-push switches) so this can be run using light-duty figure-8 cable.

If using this mode, make sure the system is set for momentary operation – garage door controller local switches are almost invariably wired as push-to-open, push again to close. And some controllers might not like a long-term short across their local switch!

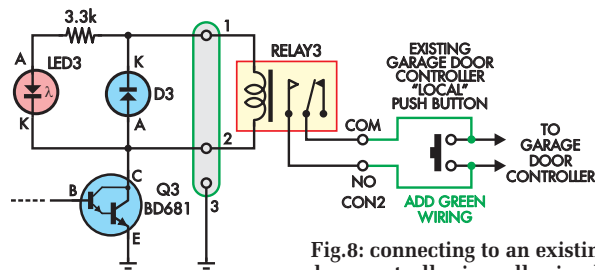


Fig.8: connecting to an existing garage door controller is really simple (and safe!) if your system has a 'local' pushbutton switch to open and close the door. This section of the circuit shows relay 3, but any of the three relays could be used – wire in the COM and NO terminals. Note that this would require the Rolling Code Remote Control to be used in 'momentary' mode

Switching mains

For switching 230V mains, the wire must be sheathed 2-core or 3-core mains flex (depending on what you are switching), rated at 7.5A 230V AC. Use 10A wire if switching more than 7.5A. The wire is passed through a cable gland in the box end and secured using a P-clamp that is attached to the PC board with an M4 \times 10mm screw washer and nut.

We soldered the M4 nuts to the underside of the PC board. This allows securing the P-clamps in position without accessing the underside of the PC board. If the 2-core wire is not held tightly enough in the P-clamp, enlarge the diameter of the wire by placing a short length of heat shrink tubing over the wire. Use a second layer of heatshrink tubing, if one layer is insufficient. The cable gland also helps secure the wire when tightened.

After wiring, replace the plastic cover over the CON1/CON2 terminal strip. It snaps into place when the PC board is mounted in the case (otherwise it slides in from the side).

Disable existing controllers?

While this controller should operate quite happily in conjunction (parallel) with an existing wireless garage door controller, it could become confusing to the operators. Because you can add up to 16 transmitter remotes, you're not likely to need the old unit anyway.

We suggest disabling the existing wireless receiver. The best way to do this would be to disconnect power to the receiver without disconnecting power to the controller itself. However, in many commercial garage door openers, the receiver and door control circuitry are combined so this might prove difficult.

Because of the variety of commercial garage door controllers, we cannot offer any real advice in this area – except to say that it might be as simple as removing the external (wire) antenna which most have fitted.

This should make the existing receiver ‘deaf’ enough so that nothing happens if an old transmitter button is pressed!

Reproduced by arrangement
with SILICON CHIP
magazine 2011.
www.siliconchip.com.au

Errata from Part 1 of this project (August 2011)

On page 35, discussing the BCD switch, should read:
Position 15 (or F) sets all switch outputs at 0V.

Frequently Asked Questions

Q. What happens if the transmitter is out of range and one of the transmit switches is pressed? Will the receiver still work when the transmitter is later brought within range and the button pressed again?

These questions are asked because the receiver was expecting a code that has already been sent and the transmitter has rolled over to a new code. So how does the system get around this problem?

A. The answer to this is that if the signal format is correct but the code is incorrect, the receiver then calculates the next code that it would expect and checks this against the received code. If the code is now correct, the receiver will operate.

If the code is still incorrect, the receiver calculates the next expected code and will do this up to 100 times. If none of these are correct, the receiver keeps its original code and it will not trigger. So the transmitter buttons can be pressed up to 100 times while out of the receiver's range without problems.

Q. How do you restore the transmitter operation?

A. The only way to trigger the receiver after this is to re-register the receiver with the transmitter. A different registered transmitter will still operate the receiver. That's because this transmitter has a different identity and a different code to the other transmitter.

Automatic Re-registration

Some rolling code transmitters systems offer automatic registration if the transmitter and receiver lose their synchronisation.

In these systems, the receiver includes a code 'look-ahead' feature, as described above, but the number of look-ahead codes is usually limited to fewer than 100. What happens is that if the code is not recognised after all the look-ahead calculations have been made, the receiver changes its synchronisation method.

Basically, the receiver requires two separate transmission codes before restoring correct operation. On the first transmission, it calculates the next code it should receive using this received code as the basis for calculation. If the second code sent by the transmitter is the same as the code that was calculated, the receiver operates.

The drawback of this latter scheme is somewhat less security, since, in theory, two successive transmission codes could be intercepted and recorded. These codes could then be re-transmitted in sequence to re-register and thus trigger the receiver.

Q. How does the receiver know which code to expect from the transmitter, since this changes each time?

A. The answer to this is that the transmitter and the receiver both use the same calculation to determine the next code. They also both use the same variables in the calculation and these variables tend to be unique values that no other transmitter uses.

For example, if the calculation for consecutive codes requires the original calculated code to be multiplied by 100 and the number 7 added to it, then both the

transmitter and receiver will use these numbers to perform the calculation. The values quoted for the multiplier and increment value are not as simple as 100 and 7, but are 24 bits and eight bits respectively in length. Without knowing both the multiplier and the increment value, it would be very difficult to predict the next code. This is particularly true because of the very large numbers involved.

The code length is 48 bits, with as many as 2.8×10^{14} combinations.

This reduces by a factor of 100 because of the look-ahead feature to a 1 in 2.8×10^{12} chance of striking the correct code – still impossibly long odds.

Code scrambling

A further complication with the transmitted code is that the code is not necessarily sent in sequence. There are also 32 possible scrambling variations that are applied to the code and the scramble changes each time that code is transmitted.

Q. What if the rolling code calculation results in two consecutive codes that are the same and the code is intercepted and re-transmitted to open the lock?

A. This is highly improbable and our rolling code transmitter has safeguards preventing the same code appearing twice in succession. For each code calculation, a comparison is made between the current and last code. If the code is the same, the code is recalculated after an increment of the code value to ensure successive code calculations diverge. It is this new code that is transmitted.

The receiver performs the same re-calculation so that the new code will be accepted.

A warning, though, is that, as with any encoded UHF encoded transmission, the signal can be intercepted and recorded. When played back it can be used to unlock a receiver. This is particularly true of fixed code systems where the same code is always used.

For rolling code systems, a capture of the transmitted code can be used to unlock the system if the code is captured when the transmitter is used out of range from the receiver. The captured code could then be used to unlock the receiver if it is transmitted before the genuine transmitter is used to unlock the receiver. The captured code will only work once because the receiver will change to its new code upon reception of the signal. The captured signal will also be nullified if the genuine transmitter is used to unlock the receiver.

Q. Does each transmitter use the same rolling code calculation and if so, wouldn't the receiver lose its synchronisation if several transmitters were used?

A. Each transmitter is treated independently to another and uses different rolling code and calculation parameters. So a receiver will not lose synchronisation with a particular transmitter, even if it is not generally used. Imbedded in the rolling code is the transmitter identity value from 0-15 and so the receiver knows which transmitter is sending the signal.

EPE

Edible Computing

TechnoTalk

Mark Nelson

Forget 'grey goo' — how about computers based on 'smart yogurt'? Or perhaps you'd like to get your own back on viruses to make them perform electronic assembly tasks? Mark reports the news stories that even his addled brain couldn't make up.

PRINCE Charles hit the headlines in 2003, when he expressed his views about nanotechnology. It appears he was misquoted, since afterwards he denied having used the expression 'grey goo' or stating that he believed that self-replicating robots, smaller than viruses, would one day multiply uncontrollably and devour our planet. 'Such beliefs,' he added, 'should be left where they belong, in the realms of science fiction.'

Molecular nanotechnology has always had a slightly edgy image, as the Wikipedia article on the subject explains: http://en.wikipedia.org/wiki/Grey_goo. Discussion of nanomachine technology dates back to 1986, when the term 'grey goo' was first coined, and it is still a favourite of futurologists. The only difference is that scientists are now demonstrating practical prototype devices.

Molecular computing

One of the first steps towards molecular computing was revealed last year, when scientists from Michigan Technological University in the USA demonstrated a novel computer composed not of silicon, but of organic molecules on a gold substrate. In fact, this different kind of computer is built out of DDQ, a hexagonal molecule made of nitrogen, oxygen, chlorine and carbon that self-assembles in two layers on a gold substrate. An important difference is that the DDQ molecule can switch among four conducting states – 0, 1, 2 and 3 – unlike familiar binary switches – 0 and 1 – as used by digital computers.

'Grey matter' was the inspiration for this proof-of-concept demonstration, in which evolving patterns on this molecular processor mimic patterns displayed by the human brain. Explained physicist Ranjit Pati, 'We have mimicked how neurons behave in the brain and the evolving neuron-like circuit network allows us to address many problems on the same grid, which gives the device intelligence.'

As well as intelligence, this approach to information processing also gives far greater speed. 'Modern computers are quite fast, capable of executing trillions of instructions a second, but they can't match the intelligent performance of our brain. Our neurons only fire about a thousand times per second. But I can see you, recognise you, talk with

you, and hear someone walking by in the hallway almost instantaneously, a Herculean task for even the fastest computer.'

Waiting for the right technology

Interestingly, the principles of this molecular computer were first proposed as far back as 1955 by the Hungarian-American quantum mechanics specialist John von Neumann. At that time, von Neumann was only able to demonstrate his 'cellular automaton' system for parallel computing on a piece of graph paper, moving black and white dots together according to simple rules.

It took another 55 years to realise this physically for the first time using molecular monolayers. It is, of course, only a conceptual breakthrough, and at a very rudimentary stage, but the possibilities of processing information so rapidly have remarkable potential.

According to Bandyopadhyay, robots could become much more intelligent and productive than today if his team's molecular computing approach is adopted. He explains: 'Current robots cannot cope with changing environments, and they will be unable to survive in more hostile environments than those they were programmed for. Their intelligence is very limited, even when compared to viruses and bacteria. With our hardware, robots can take many decisions at a time, which no computer can do. They can come up with new solutions an infinite number of times, which we can never expect from a normal robot.'

Smart yogurt

One of the most interesting proponents of new technology is futurologist Ian Pearson, who expressed his fascinating ideas on biological computing on a BBC *Radio 4* programme earlier this year. So, forget 'grey goo'; the new thing is 'smart yogurt' – linkable electronics in bacteria such as *E. coli*. I called this the new thing, but Pearson came up with the concept as long ago as 1997.

Five years ago he stated: 'You modify a real live bacterium – *E. coli* or something you find in yoghurt – so that it creates electronic circuits within its own cells. That's really good fun, because you've got electronic bacteria – a real live bacterium, which can replicate with electronics in it. The electronics have nothing to do with the bacteria,

they are just there, but they turn it into 'smart bacteria' because you can then connect those electronics together using infrared or bioluminescence and make completely scalable electronic circuits'.

'So you start off with one bacterium, which is essentially a module, and you link billions of these together and you've got something that makes your PC look pretty primitive. We'll have a 'smart yoghurt' by about 2025, we did the calculations, and we reckon that it's possible to make a yoghurt with roughly the same processing power as the entire European population.'

What else could you achieve with smart yogurt? On his blog, Pearson explains: 'You can do active skin, with 10 micron chips containing hundreds of thousands of transistors embedded among skin cells, using infra-red to communicate with each other. They will analyse blood passing in capillaries. They will monitor and record nerve signals associated with sensations, and allow them to be replayed at will'.

'We will embed chips in our corneas to raster scan lasers onto our retinas to create full 3-D high-res video overlays on what we see in the real world'.

Viruses welcome here

If you feel it's high time to redress the harm and misery wrought by viruses, you'll be pleased to learn that researchers at the Massachusetts Institute of Technology (MIT) have found a way of using genetically-modified viruses in a process that improves the efficiency of solar cells by nearly one-third. A report from MIT explained that significant improvements can be made to the power-conversion efficiency of solar cells by enlisting the services of tiny viruses to perform detailed assembly work at the microscopic level.

In this new development, researchers found that a genetically-engineered version of a virus called M13, which normally infects bacteria, can be used to control the arrangement of the nanotubes on a surface. It keeps the tubes separate so they can't short out the circuits, and separates the tubes so they don't clump. The two functions are carried out in succession by the same virus, whose activity is 'switched' from one function to the next by changing the acidity of its environment. Whatever next?



Here's a low-cost add-on for the Digital GPS Time Display published in our May and June 2011 issues. It senses the ambient light level, so that a modified program running in the display unit's PIC controller can adjust the LED brightness to a comfortable level – ranging from full brightness when the ambient light level is high, down to dim when the ambient light is very low.

SOON after the basic *6-Digit GPS Time Display* was published in the May 2011 issue, we received emails from readers who were disappointed that we hadn't provided the design with an 'autodim' facility. And they wanted to know if such a feature could be added in.

Unfortunately, trying to incorporate dimming on the existing clock PC board is quite difficult. The conventional way of doing it would be to use a transistor and LDR circuit to control the emitters of all six common-cathode

driver transistors, Q15 to Q20. We have used this scheme on quite a few past projects which had a PIC micro and 7-segment LED displays, but a quick look at the PC board pattern shows that it would be quite impractical.

This presented a real dilemma until we came up with an alternative scheme: use an LDR and transistor circuit to allow the PIC micro to directly monitor the ambient light level, and then change the duty cycle of the multiplexed drive to the 7-segment displays.

So we set out to develop the *Auto-dim Display Sensor* described here. The hardware was the easy bit, of course – the firmware mods took a bit longer.

How it works

The new hardware consists of just a few parts on a small PC board. This mounts on 10mm spacers in front of the display unit's main PC board, in place of the DB-9 connector (CON1) which was originally used to feed in the NMEA-0183 data stream from the GPS frequency reference.

Constructional Project


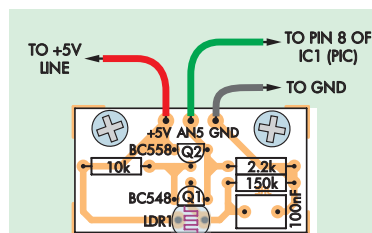


Fig.2: install the parts on the PC board as shown here. Take care not to get the two transistors mixed up.

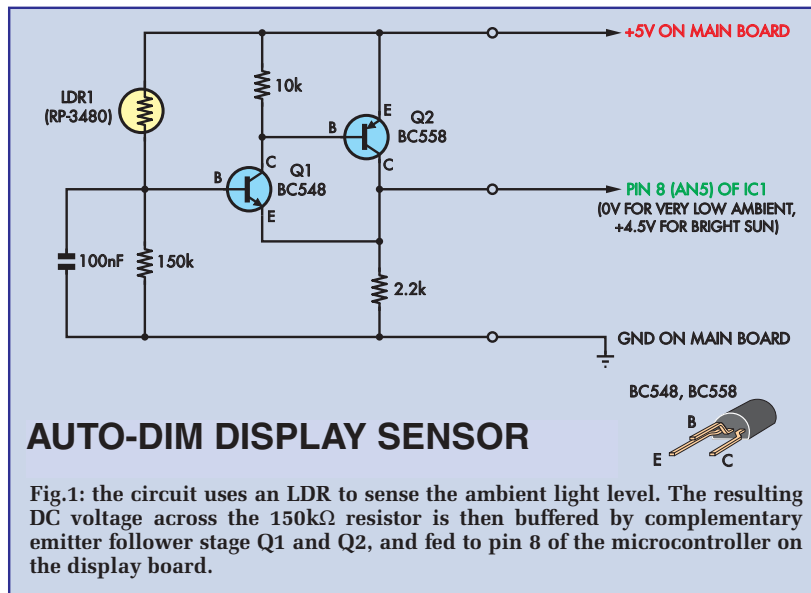

The DB-9 connector (CON1) is no longer needed if you're using the GPS receiver module described in the June 2011 issue.

Fig.1 shows the circuit details. The ambient light level is sensed by LDR1, a small light-dependent resistor (LDR) which varies its resistance between about 2MΩ in the 'dark' and a couple of hundred ohms in bright sunlight. This LDR is connected in series with a 150kΩ resistor across the +5V supply. As a result, resistance changes in the LDR result in corresponding DC voltage changes across the 150kΩ

resistor, the level varying from close to 0V when the ambient light level is very low, up to about +4.5V in bright sunlight.

Unity-gain buffer

The other components in the circuit, based on transistors Q1 and Q2, make up a near-unity gain impedance step-down buffer. This ensures that the light-dependent output voltage is made available at a much lower impedance level than 150kΩ.

In greater detail, transistors Q1 and Q2 form a complementary emitter follower, with a source resistance

much lower than the 2.2kΩ emitter/collector resistor. This makes it suitable for driving one of the analogue-to-digital converter (ADC) inputs of the display's PIC18F877A microcontroller (IC1). In this case, the sensor voltage is fed to the micro's AN5 ADC input.

That's really all there is to the hardware side of the add-on, apart from the 100nF capacitor across the 150kΩ resistor. This capacitor is used to filter the LDR's output voltage, to remove any modulation from the indoor ambient lighting level.

Modified firmware

The modified firmware for the PIC regularly monitors the voltage applied to the AN5 input (pin 8). It does this by directing the ADC module inside the PIC to measure this voltage. It then tests the measured voltage level and varies the on-off ratio of the display digit switching signals to vary the apparent display brightness, over six levels.

As a result, the apparent display brightness varies between virtually full brightness at high ambient light levels, down to about 17% of full brightness at very low ambient levels.

Building it


As mentioned earlier, the additional components are all mounted on a small PC board. This is coded 819 and measures just 36mm × 19mm. This board is available from the *EPE PCB Service*.

Fig.2 shows the parts layout on the PC board. The only polarised components are transistors Q1 and Q2, so make sure you fit these with the orientation shown. Also, be careful not to swap the two: **Q1 must be an NPN BC548, while Q2 is a PNP BC558.**

The LDR is not polarised and can be fitted either way around. Leave its leads about 15mm long so that they can be bent outwards from the PC board

Table 1: Resistor Colour Codes

	No.	Value	4-Band Code (1%)	5-Band Code (1%)
□	1	150kΩ	brown green yellow brown	brown green black orange brown
□	1	10kΩ	brown black orange brown	brown black black red brown
□	1	2.2kΩ	red red red brown	red red black brown brown

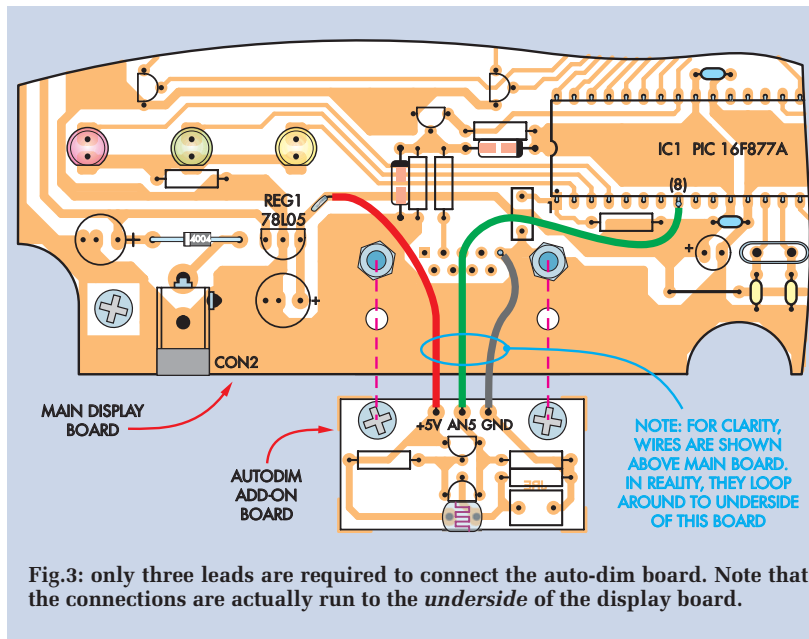

after it is fitted to the board. This allows the sensitive 'front face' of the LDR to be turned away from the main LED displays when the add-on board is mounted in position.

Note: if the LDR is able to pick up too much light from the displays themselves, the auto-dimming feature won't work. Instead, the displays will run at full brightness, regardless of the ambient light level.

Only three wires are required to connect the auto-dimming board to the main display board. Fig.3 shows the details.

The first step is to solder three 80mm lengths of light-duty hookup wire to the three external wiring points (ie, +5V, AN5 and GND). That done, attach two M3 × 10mm tapped spacers to the underside of the add-on board, using two M3 × 6mm machine screws.

Board mounting

The completed add-on assembly can now be mounted in the lower left-hand corner on the main display board. You will have to remove the display board from its case in order to do this. The add-on board is secured in place using two further M3 × 6mm screws, which pass up through the upper pair of 3mm holes that were originally provided to secure the DB-9 connector (CON1) – see photos.

Parts List

- 1 PC board, code 819 available from the *EPE PCB Service*
36mm × 19mm
- 2 M3 × 10mm tapped spacers
- 4 M3 × 6mm machine screws
- 1 light dependant resistor (LDR1)
- 3 80mm lengths of light-duty hookup wire

Semiconductors

- 1 BC548 *NPN* transistor (Q1)
- 1 BC558 *PNP* transistor (Q2)

Capacitors


- 1 100nF MKT metallised polyester

Resistors (0.25W 1%)

- 1 150kΩ 1 2.2kΩ
- 1 10kΩ

The three leads from the add-on board can now be fed to the rear of the main board and connected to the appropriate points underneath. As shown in Fig.3, the +5V lead goes to the +5V supply rail near the output pin of REG1, while the ground wire goes to the earth copper at what was originally pin 5 of CON1.

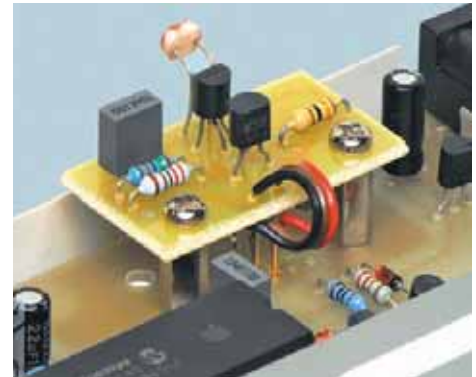The third centre wire (AN5) goes to pin 8 of the display's PIC16F877A micro (IC1). This pin was not used in the original 'non-dimming' version.



The auto-dim board is mounted on two M3 × 10mm tapped spacers. These are attached to the main board using the holes originally provided to secure the DB-9 connector (CON1).

Once these three connections have been made, you can slip the finished board assembly back into the enclosure and fasten it in place. All that now remains is to download the new version of the GPS Time Display firmware from the *EPE* website (www.epemag.com) and reprogram the PIC micro so that it knows how to monitor the LDR voltage and vary the display brightness accordingly.

Note that the add-on board by itself won't give you the auto-dimming function unless you use the revised firmware in your PIC.

The updated firmware now replaces the original program, whether or not you have the add-on board. **However, if you don't have the add-on board, you must now connect pin 8 of IC1 to the adjacent +5V supply rail via a 2.2kΩ resistor.**

This is necessary to give the PIC's AN5 input a *de facto* 'bright sun' input voltage level in the absence of the LDR sensor board.

That's it! With the add-on LDR sensor board and the modified firmware running inside the PIC, your GPS Time Display will now be able to adjust its brightness according to the ambient light level. **EPE**

Reproduced by arrangement
with SILICON CHIP
magazine 2011.
www.siliconchip.com.au

**EPE
EXCLUSIVE**

Win a Microchip Accessory Development Starter Kit For Android

EVERYDAY PRACTICAL ELECTRONICS is offering you the chance to win a **Microchip** Accessory Development Starter Kit for Android (DM240415), enabling accessory development for Google's Android platform. The Microchip PIC24F Accessory Development Start Kit for Android is a standalone board used for evaluating and developing electronic accessories for Google's Android operating system for smartphones and tablets.

Specifically, Android versions 2.3.4 and 3.1 and later include a new framework that allows apps to communicate directly with an accessory connected to a smartphone or tablet, via USB. The kits consist of a development board and a software library, available via free download from: www.microchip.com/get/522D, which enable the fast and easy development of Android smartphone and tablet accessories based on Microchip's large portfolio of 16-bit and 32-bit PIC microcontrollers.

This starter kit bundles five major components, including 16-bit PIC24F Development Board, PICkit 3 In-Circuit Debugger (PG164130), RJ-11 to ICSP Adapter (AC164110), 9V Power Supply (AC002014) and royalty-free, no-fee licensed software library.

Microchip's starter kits make it easy for designers to quickly design, develop and debug electronic accessories for this large and growing market. In addition to providing the schematics and gerber files for the development boards, the free software library includes a sample application protocol and an abstraction layer, which enables designers to focus on creating the application.

The development boards feature a USB connector, an on-board debugger, a programming user interface and standard Arduino connectors, for use with a host of third-party 'Shield' expansion daughter cards.

Example accessory applications include: automotive (car kits, audio, GPS); home (audio docks, remote controls, data backup); fitness/health (glucose meters, fitness equipment); and business (credit-card terminals, projectors).

HOW TO ENTER

For your chance to win a Microchip Accessory Development Starter Kit for Android, visit: www.microchip-comps.com/epe-android

CLOSING DATE

The closing date for this offer is 31 October 2011





Recycle It!




BY JULIAN EDGAR

www.julianedgar.com

Fun Projects From Salvaged Parts

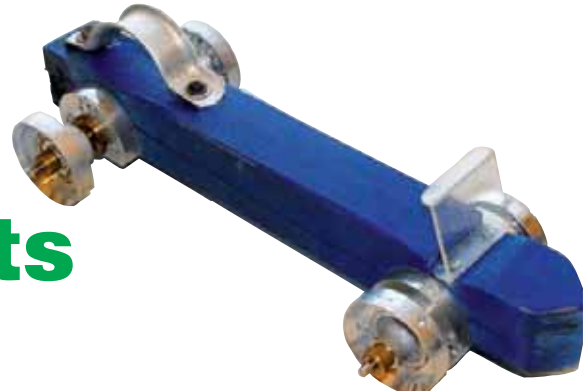IF YOU keep your eyes open, it's easy to salvage from other people's discards a whole range of interesting parts and devices. Here are six that I've recently been playing with.



Music player

THE other day, when pulling apart a PC, I spotted this stereo, amplified speaker system. It was slotted-into the rack under a disc drive. It is normally powered by the PC and comes complete with a 1/4-inch stereo plug on a cord. On the front is an 'on' LED and a volume control.

Having been after a lightweight music player to work with my iPhone, I wondered if it could be easily adapted to suit. Despite being powered from the 12V rail of the PC, I soon found that it was happy working down to 3V. I opened-up the box and found space for two AA cells and then I added an on/off switch (like the battery holder, a salvaged part).

The result is surprisingly good – certainly not hi-fi, but quite acceptable in quality and volume as a light-weight (280 grams!), portable music player that will work with any MP3 unit.



Unbreakable mirror



TALKING about light-weight items, have you checked-out the platters inside a PC hard disc drive? Current ones are glass or ceramic (not so useful), but older ones of the sort you can pick up for nothing are aluminium. The discs are very thin and about 95mm in diameter. They're coated in a material able to be magnetised and then highly polished. And it's this mirror polish that makes them interesting.

As someone who goes camping (normally via a pedal machine), I am amazed at how effective a hard drive platter is as a light-weight (just 15 grams!), indestructible mirror. A platter is perfect as a personal mirror and, more importantly, as an emergency signalling mirror. The hole through the middle even allows you to see exactly where the reflected light is going. Signal mirrors are generally regarded as having about a 15km range – that's an awful lot further than your shouting will be heard!


Unbreakable, ultra light-weight – and free!

Land speed record car toy

MY five year old son is fascinated by land speed record cars, and wanted to make his own. However, it had to be fast on carpet (not a criterion that applies to the full-size cars!).

This is the result of our construction – and it's relevant here because of the wheels and bearings. The 'body' of the toy is just a piece of shaped timber. The windscreen is made from a cut-down cassette deck door and the rear wing/spoiler/handle is half of an industrial clamp.

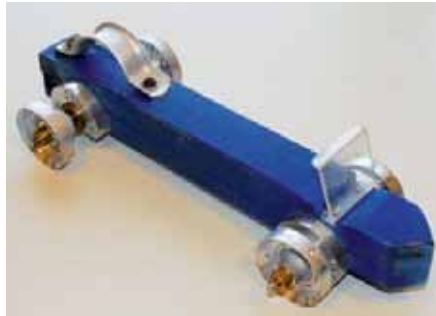All four wheels, bearings and mounts are made from video drums salvaged from VCRs. Because of slight differences in



construction of the video drums, all four wheel assemblies vary a little in appearance – but that doesn't matter.

On the carpet, the toy is fast and tracks beautifully – after all, each

wheel is equipped with a hardened steel axle and two precision sealed ball bearings! And, perhaps oddly enough, like this toy, many land speed record cars do actually use solid metal wheels.

It's also interesting that in this age of mass-produced and very cheap toys, this homebuilt car has continued to be treasured for months after it was first built, and in fact has even made a trip to school as part of a 'show and tell' session. 'What's it made from?' the other children asked Alexander. 'It's made from recycled stuff from the rubbish tip!' was his proud reply. In fact, all that was bought new was the paint.

Pressure switch



INSIDE any older washing machine you'll find a very sensitive pressure switch – good salvage material. But often, when you need a pressure switch, the washing machine items are both too large and too sensitive. But that's no problem, just pick up a spa bath at the local rubbish tip! Pardon? Well, you don't actually need to collect the whole bath – just some of its electricals.

Most spa baths use pneumatic switching to control their operation. A non-electrical pushbutton (basically, just a simple pneumatic plunger), is connected by plastic tubing to a pressure-operated microswitch. So, when you're sitting in the spa and press the button, you develop air pressure in the tube that triggers the remote microswitch. Pull out the electrical switch and you have a small, self-contained, momentary pressure switch, normally rated to mains voltages, that triggers at about 1psi.

You can, of course, use it in the same way as its maker intended – switching mains power when in dangerously wet conditions. Or you can use it as a pure pressure switch. For example, in car applications where the engine uses forced aspiration (that is, either a turbo or supercharger), the pressure switch can be used to trigger something when the engine is on boost. The 'something' could be as simple as a dashboard indicator, or as complex as an intercooler water spray.

Ultra high-pressure pump



YOU don't come across them often as thrown away items – but with their current popularity, that's sure to change. So what am I talking about? Those expensive home cappuccino machines, that's what!

The interesting thing about these machines is that they contain a high pressure water pump, for example rated at a maximum pressure of 15 bar (over 200psi!). The pump contains a coil, an internal piston and a one-way valve. When the coil is connected to mains AC current, the piston oscillates at mains frequency, producing a pulsating flow of water. If the outlet is restricted, the flow rapidly builds to a high pressure.

If you need a finely atomised water spray, one of these pumps and a good quality brass misting nozzle will produce an extraordinarily fine droplet size. So for humidifying or spray-water cooling, these pumps are amazing. Note that the pumps are designed for intermittent use, so if you are running one for longer than (say) a minute at a time, add fan cooling and monitor the pump's temperature.

Magic flasher

HERE'S a fascinating – but very simple – device to make. It uses the solenoid salvaged from a hair or beard trimmer, an LED (I used a 10mm high intensity LED) and one of the two powerful magnets from a microwave oven's magnetron. (If salvaging from a microwave oven, you need to be extremely careful of the high voltage capacitor that can give a lethal bite – don't delve inside microwaves unless you know exactly what you are doing.)

So what happens? Hang the magnet from a long piece of string or flexible wire, and then place it where there is space for the magnet to swing back and forth like a pendulum. Connect the solenoid directly to the LED and then locate the solenoid so that its pole piece is positioned directly beneath the hanging magnet. When the magnet swings past, it should clear the solenoid armature by only a millimetre or two.

Pull the magnet back and let it swing past the solenoid. Each time it whizzes past, the LED will give out a bright flash, especially effective in a semi-darkened room.

Of course, the electricity to light the LED is generated by the movement of the magnet past the solenoid coil – but to most people, it looks like magic. They wonder what makes the LED light as the magnet goes by. If you set the scene by saying some mumbo jumbo about the 'mysterious' process, people




will come up with all sorts of theories as to why the LED lights. They'll ask – but where are the batteries? And how does the coil 'know' the magnet is nearby? (One person said: 'There's a reed switch inside the coil!'.) Simple fun – and, of course, you can take the same idea and with a few more salvaged parts, make a hand-cranked high intensity LED flasher.


USB DrDAQ®

VERSATILE DATA ACQUISITION

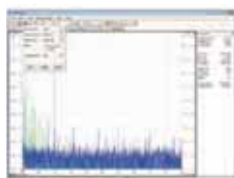- Use DrDAQ as a **Data logger**, an **oscilloscope**, and a **signal generator**
- **Built-in sensors** for light, sound and temperature
- **Measure pH** - just plug in any standard pH electrode
- Sockets for **external sensors**
- **Digital outputs** to control external devices
- **USB** connected and powered
- **Use up to 20 USB DrDAQs** on a single PC



Oscilloscope /
Spectrum Analyzer

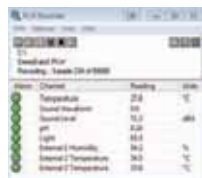

Multi-channel
data logger



Arbitrary waveform
generator



Write your
own software



USB DrDAQ: Making Data Logging Fun!
www.usbdrdaq.com/DD123


pico
Technology

TEACH-IN 2011

A BROAD-BASED INTRODUCTION TO ELECTRONICS

Part 11: Summing it all up

By Mike and Richard Tooley

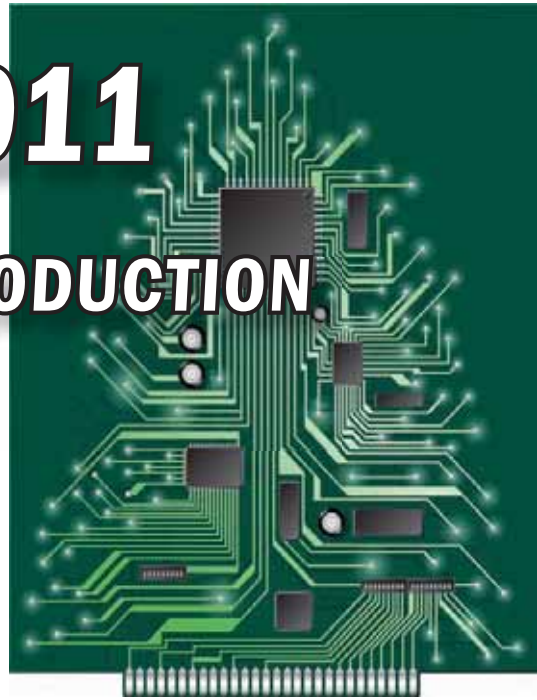

Our Teach-In series is designed to provide you with a broad-based introduction to electronics. We have attempted to provide coverage of three of the most important electronics units that are currently studied in many schools and colleges in the UK. These include Edexcel BTEC Level 2 awards, as well as electronics units of the new Diploma in Engineering (also at Level 2). The series will also provide the more experienced reader with an opportunity to 'brush up' on specific topics with which he or she may be less familiar.

Each part of our Teach-In series is organised under five main headings; Learn, Check, Build, Investigate and Amaze. Learn will teach you the theory, Check will help you to check your understanding, and Build will give you an opportunity to build and test simple electronic circuits. Investigate will provide you with a challenge which will allow you to further extend your learning, and finally, Amaze will show you the 'wow factor'!

IN THIS instalment of *Teach-In 2011*, we bring our series to a conclusion with a quick review of the previous ten parts, and include a comprehensive index that will help you to locate the key topics that we've introduced as the series has progressed. There's also a selection of questions and fun activities, including a crossword, that will help you to check your understanding.

For good measure, we've also included eight additional circuits for you to investigate using the Circuit Wizard software.

Learn

Looking back

We began our Teach-In series by looking at the signals that are used to convey information in electronic circuits. We discussed the units and quantities that we use when making measurements in electronic circuits, and how waveforms are used to show how the voltage and current in an electronic circuit vary with time. We also introduced batteries and power supplies that we use to provide power to electronic circuits.

Part 2 dealt with resistors, capacitors, timing circuits and Ohm's Law. We also found out what happens when a capacitor is charged or discharged.

Part 3 provided you with an introduction to diodes and power supplies. We investigated the voltage/current characteristics for two different types of diode, and showed how they could be used together with a transformer to produce a power supply. We also looked at light emitting diodes (LEDs) and Zener diodes.

Transistors were the subject of Part 4. We described the operation of *NPN* and *PNP* transistors, and explained how they are used to amplify current and operate as saturated switches.

An introduction to operational amplifiers (op amps) was the subject of Part 5. We showed how operational amplifiers can be connected in *inverting*, *non-inverting* and *differential* arrangements, as well as

showing how they could be used as comparators, where one voltage is compared with another.

Logic circuits were explained in Part 6. Here we met the symbols, truth tables and Boolean logic for each of the most common types of logic gate. We also introduced bistable devices, and showed how they could be used in binary counters. The highly versatile electronic timer (555/6) was introduced in Part 7.

These versatile circuits can be used to produce accurate time delays and repetitive pulse waveforms.

Analogue circuit applications, in the form of attenuators and filters, were described in Part 8. We explained the characteristics of low-pass, high-pass and band-pass filters and showed how these could be built using simple arrangements of resistors, capacitors and inductors. We also introduced some simple active

Crossword Check – How do you think you are doing?

The month's Check panels provides you with an opportunity to test your understanding of the previous ten parts of our *Teach-In 2011* series.

The first question tests your knowledge of some of the terms that are commonly used in electronics

11.1. Solve the crossword shown in Fig.11.1.

Clues across

- 5 Amplitude (4)
- 7 Instrument for measuring current (7)
- 8 Polarised capacitor (12)
- 10 Commonly used for logarithmic ratios (7)
- 15 Most positive connection of an *NPN* transistor (9)
- 18 Very common type of waveform (4)
- 19 Stores electric charge (9)
- 20 Unit of potential difference (4)
- 21 Instrument used to display waveforms (12)
- 22 P in PRF (5)
- 26 Most positive connection on a conducting diode (5)
- 27 $\times 0.000001$ (5)
- 29 Peak or maximum value (9)
- 30 Unit of frequency (5)

Clues down

- 1 Used to produce delays (5)
- 2 Diode voltage reference (5)
- 3 Present on the plates of a capacitor (6)
- 4 Time for one cycle (6)
- 6 Circuit that has no stable state (form of oscillator) (7)
- 9 Allows current to flow in one direction only (5)
- 11 C in CRT (7)
- 12 Input of a common-emitter amplifier (4)
- 13 Fast analogue-to-digital converter (5)

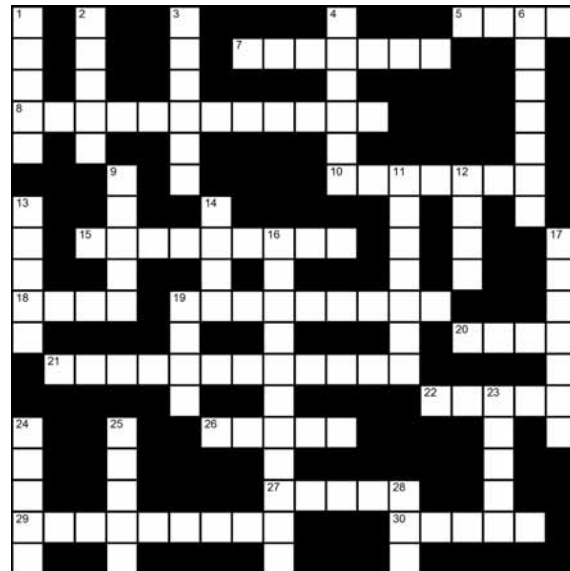


Fig.11.1. Common terms used in electronics

- 14 $\times 1,000,000$ (4)
- 16 Steps alternating voltage up or down (11)
- 17 Most positive connection of a *PNP* transistor (7)
- 19 Smallest indivisible part of a battery (4)
- 23 L in LED (5)
- 24 Unit of capacitance (5)
- 25 $\times 0.001$ (5)
- 28 Unit of resistance (3)

Crossword solution – page 53

filters based on op amps. For good measure, we explained how decibels are used to express gain or loss in electronic circuits.

In Part 9, we showed how an analogue signal can be converted to digital data, and *vice versa*. We described the process of quantisation and explained how the number of data bits affects the accuracy and resolution of a DAC and ADC.

Part 10 dealt with the practical aspects of constructing and testing electronic circuits. We introduced some basic items of test equipment in the form of *multimeters* and *oscilloscopes*, and showed how these could be used to measure voltage, current, frequency, time and waveform in an electronic circuit.

Check – How do you think you are doing?

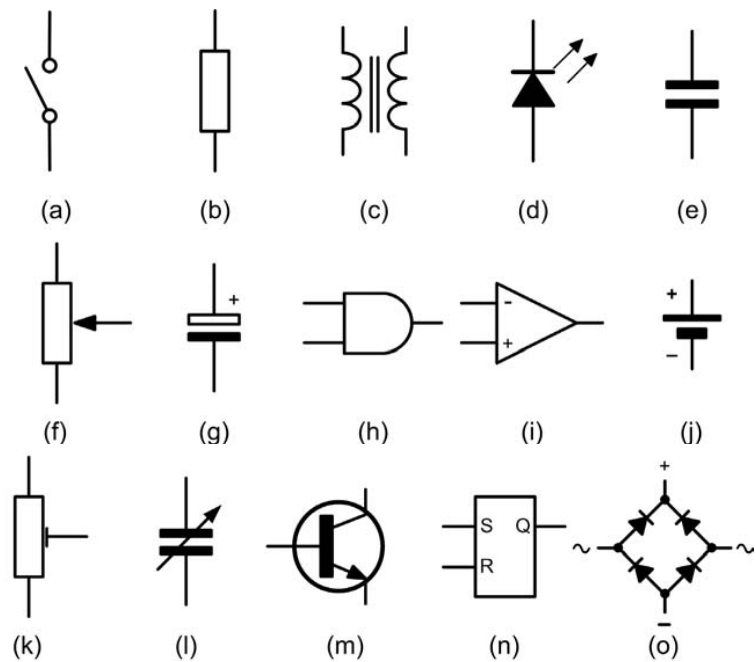


Fig.11.2 See Question 11.2

The next question tests your ability to recognise the symbols used in circuit diagrams:

11.2. Identify each of the symbols shown in Fig.11.2.

Question 11.3 and Question 11.4 test your ability to extract information from a waveform:


11.3. For the waveform shown in Fig.11.3(a):

- What type of waveform is shown?
- What is the frequency of the waveform?
- What is the periodic time of the waveform?
- What is the amplitude (peak value) of the waveform?


11.4. For the waveform shown in Fig.11.3(b):

- What type of waveform is shown?
- What is the pulse repetition frequency of the waveform?
- What is the periodic time of the waveform?
- What is the duty cycle of the waveform?
- What is the peak-peak value of the waveform?

Fig.11.3 (right). See Question 11.3 and Question 11.4

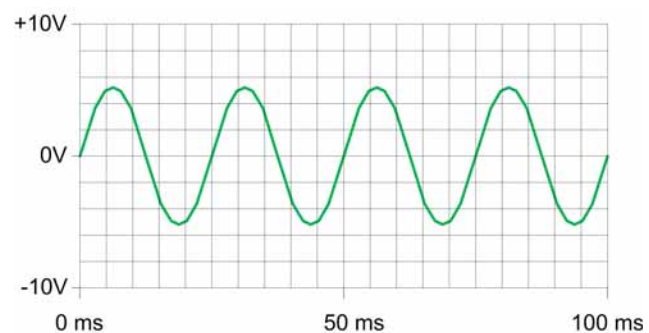

(a)

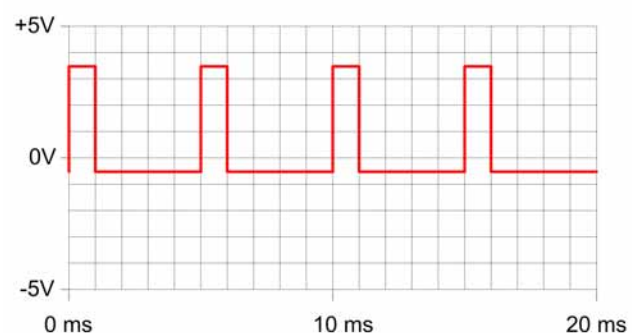

(b)

The next two questions test your knowledge of some of the units and quantities used in electronics:

Quantity	Unit	Abbreviation
Electric potential	volt	
	ampere	A
Electric power		W
Capacitance		F
Resistance	ohm	
Frequency		Hz
Bit rate		Bps

11.5. Complete the table of electrical quantities and units of measurement

Definition	Unit
The potential that appears between two points when a current of one ampere flows in a circuit having a resistance of one ohm	
The current that flows in an electrical conductor when electric charge is being transported at the rate of one coulomb per second	
	1 watt
The resistance of a circuit when a current of one ampere flowing in it produces a potential difference of one volt	
	1 hertz

11.6. Complete the table of definitions shown above

Question 11.7 tests your ability to convert multiples and sub-multiples to fundamental units:

- 11.7. Express:
- | | | |
|------------------|------------------|--------------------|
| (a) 250mV in V | (c) 68000Ω in kΩ | (f) 885Hz in kHz |
| (b) 0.15mA in μA | (d) 0.235W in mW | (g) 1500pF in nF |
| | (e) 0.22MΩ in kΩ | (h) 1.2kbps in bps |

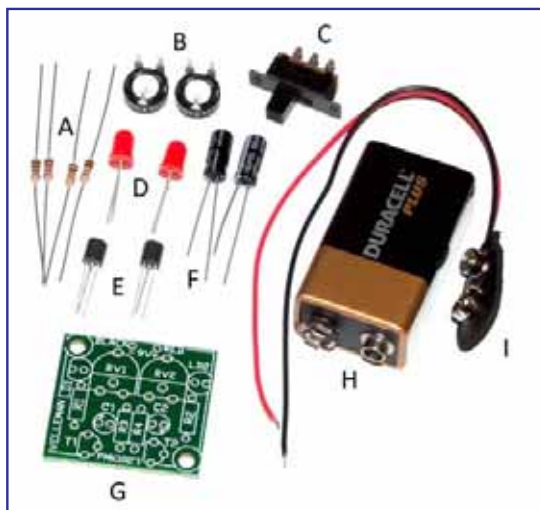


Fig.11.4. See question 11.8

The next question tests your ability to recognise some common electronic components:

11.8. Fig.11.4 shows a kit of parts needed to build a simple astable LED flasher. Identify the parts marked A to I.

Question 11.9 checks a basic understanding of basic digital logic:

11.9. Sketch logic circuits showing how:

- (a) a four-input AND gate can be built using three two-input AND gates
- (b) a four-input OR gate can be built using three two-input OR gates
- (c) a two-input AND gate can be built from two two-input NAND gates.
- (d) a two-input OR gate can be built from two two-input NOR gates.

Finally, Question 11.10 tests your ability to read and understand a simple electronic circuit diagram:

11.10. Fig.11.5 shows the circuit of a simple headphone amplifier in which all of the fixed resistors have a tolerance of ±5%.

- (a) What type of component is C2?
- (b) What type of component is TR3?
- (c) Which two components are connected to the base of TR1?
- (d) What colour code would be marked on R2?
- (e) Which component is adjustable?
- (f) What voltage will appear across C3 when S1 is closed?
- (g) If a current of 3mA flows in R3 what voltage will appear at the base of TR2?
- (h) Which component provides negative feedback?

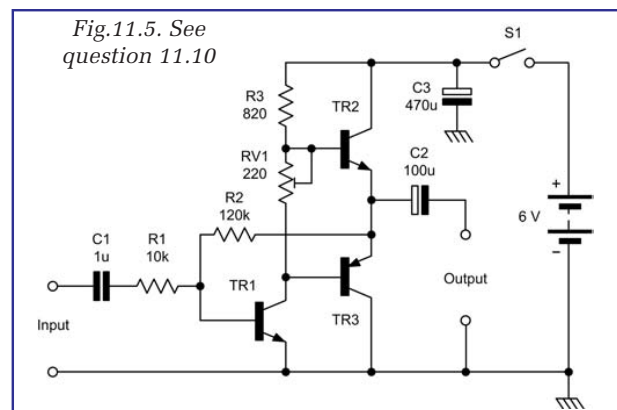


Fig.11.5. See question 11.10

The answers to these questions are shown on page 54

Build – The Circuit Wizard way

OVER the *Teach-In* series, our **Build** section has put theory into practice using Circuit Wizard to simulate a whole range of electronic circuits. We've shown how using simulation software is great for allowing you to really get to the bottom of how a circuit actually

operates, as well as being a crucial tool for electronic designers.

In this, the last edition we are giving you the opportunity to try out your 'wizard' skills with a selection of practical circuits that you can enter and investigate. For each circuit, we've included a brief description,

along with some suggestions for experimentation and a few questions to help test and extend your understanding of the underpinning theory. These circuits are a great starting point for your own projects and circuit designs.

COIN TOSS

Description

The circuit shown in Fig.11.6 uses a J-K flip-flop that is clocked at a very high speed. When switch SW1 is pressed, the flip-flop is clocked and alternates at 1kHz (that's one thousand times a second).

During this time, the LEDs will appear to flicker rapidly or may seem dimly lit. When the button is released, the flip-flop will remain in one state and hence one LED will remain lit to signify either 'heads' or 'tails'. The circuit is not truly random, but because the output is changing so quickly it would be hard to get a consistent output by timing the button press.

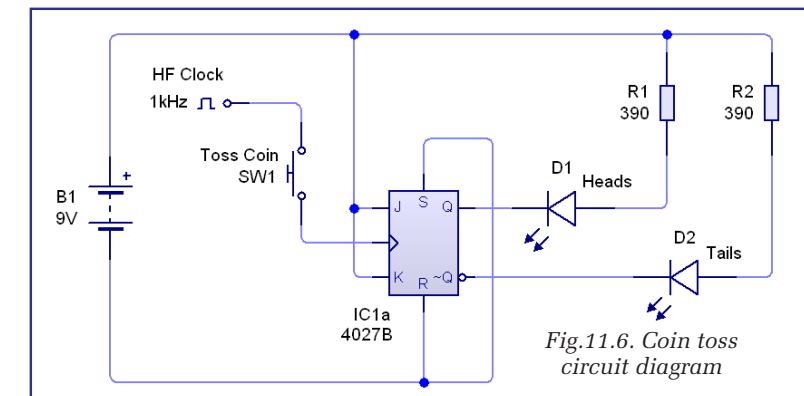


Fig.11.6. Coin toss circuit diagram

Investigate:

1. We've used the in-built clock device – try to create your own clock generator (perhaps using a 555 astable or a Schmitt oscillator circuit).
2. The coin toss circuit is not truly

random – how could we generate a real random selection?

3. How could we extend the circuit to give six outputs – ie, to create an electronic dice?

EGG TIMER

Description

The egg timer circuit shown in Fig.11.7 is a classic 555 bistable circuit. Switch SW1 selects between a soft-boiled (~3 min) and hard-boiled (~5 min) egg by changing the resistor through which capacitor C1 is charged. When the circuit is powered, the buzzer (BZ1) will sound until switch SW2 is pressed to start the timer. For this reason a practical version of this circuit should include a further toggle switch to connect/disconnect the power supply.

Investigate:

1. Monitor the charge on capacitor C1 by placing a probe on pin-6/7.
2. Use the theory that you learnt in Part 2 to calculate the time period for the circuit when timing both soft- and hard-boiled eggs (note that resistor R3 is in series with either R1 or R2 when you calculate the total resistance through which C1 is charged).
3. How would you alter the circuit to give a four-minute egg?

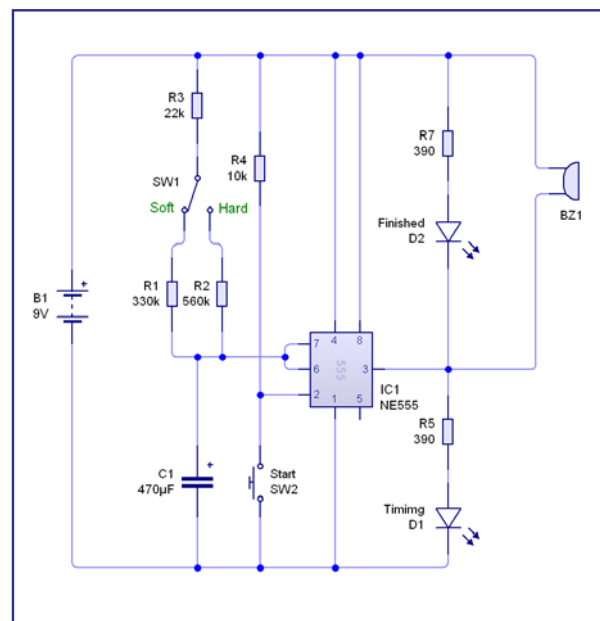


Fig.11.7. Egg timer circuit diagram

KNIGHT RIDER LIGHTS

Description

In Fig.11.8, a 4017 decade counter is used to produce a 'running lights' sequence illuminating each LED in turn. Each LED is connected to two outputs, so that as the 4017 counts up further, the LEDs are lit again in reverse order. This gives the effect of the LEDs running alternately forward/backwards.

Investigate:

1. The speed of the lights can be varied by 'adjusting' potentiometer VR1. Check that this works.

2. The 4017 is clocked by a simple Schmitt oscillator circuit (IC1a). Use the Internet and/or other resources to help you find out more about Schmitt devices and how they may be used to make a simple clock signal.

3. What is the purpose of diodes D1 to D8?

4. Why is only one series resistor (R10) required?

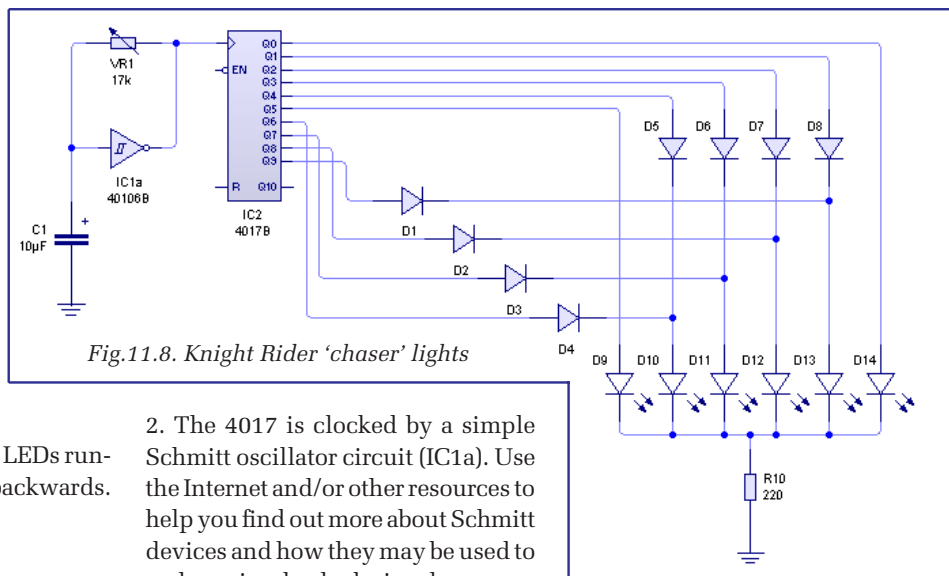


Fig.11.8. Knight Rider 'chaser' lights

INTRUDER ALARM

Description

The circuit shown in Fig.11.9 uses a thyristor (or silicon controlled rectifier (D1)). We've not met this particular device before, but it acts as a *latch* to hold the circuit in the 'on' state once pushswitch (push-to-break) SW1 is pressed.

The alarm will remain on until the circuit is disconnected from the battery (for example with keyswitch SW2), even if SW1 is released. Switch SW1 could be replaced with a normally closed (NC) pressure pad, a trip wire or a door contact in a real circuit.

Investigate:


1. Extend the circuit to include more than one trigger.

2. Use the Internet and/or other resources to find out how a thyristor works.

3. What would happen if (a) resistor R1 became open-circuit or (b) if

Fig.11.9. Circuit diagram for a simple intruder alarm

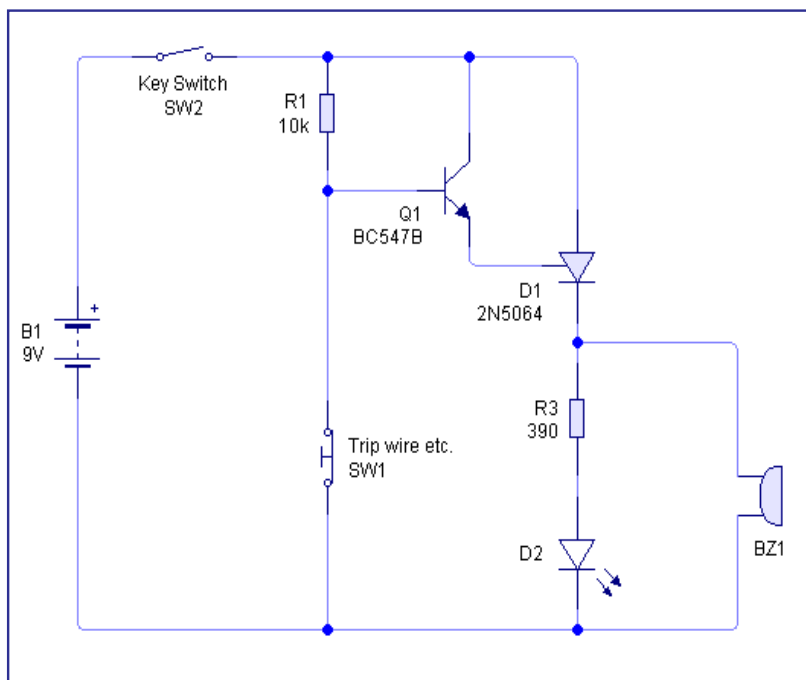transistor Q1 became short-circuit between collector and emitter?



For more information, links and other resources please check out our Teach-In website at:
www.tooley.co.uk/teach-in

Build – The Circuit Wizard way

PUSH-ON/PUSH-OFF CONTROL SWITCH

Description

In Fig.11.10, a J-K flip-flop is clocked on/off when pushswitch (push-to-make) SW1 is pressed. The Schmitt trigger inverter (IC2a) and capacitor C1 are used to debounce the clock input of the flip-flop. The output triggers transistor Q1, which in turn allows current to flow through the coil of the relay (RL1), and hence completes the mains voltage circuit and powers the lamp. In this way, the same pushbutton may be used to turn the light on and off.

Investigate:

1. What is switch 'bounce' and why do we need to reduce it?
2. What would happen if SW1 was not debounced properly?
3. What is the purpose of diode D1?

9V BATTERY TESTER

Description

The battery tester circuit (Fig.11.11) uses three consecutively higher breakdown voltage Zener diodes to control red, amber and green LEDs to indicate the battery voltage. We have used a variable power supply to simulate the voltage of the battery on test.

Investigate:

1. Why do resistors R1 to R3 need to be different values?
2. What would the effect be of changing the breakdown voltage of the Zener diodes?
3. How would you alter this circuit to test other battery voltages – eg, 5V, 12V etc.?

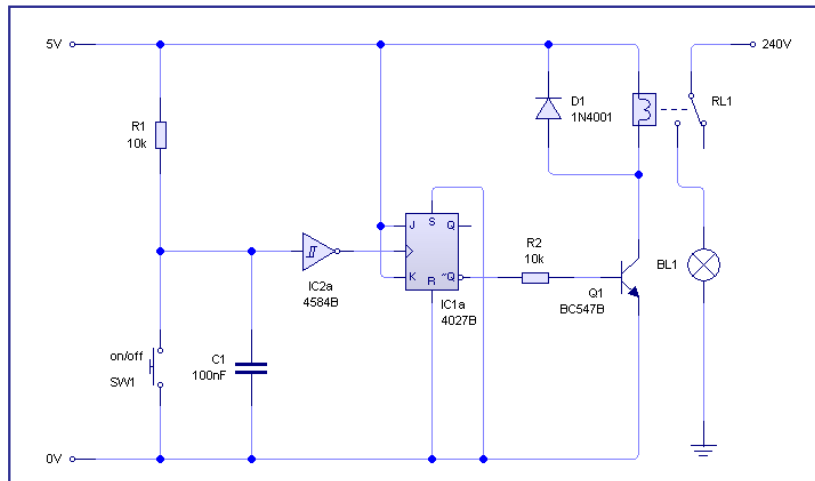


Fig.11.10. Circuit for a push-on/push-off control switch

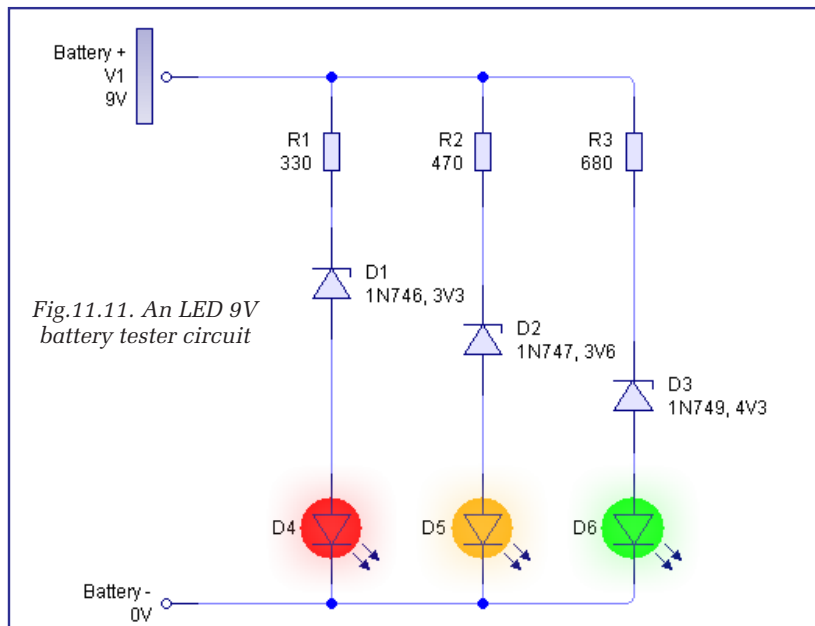


Fig.11.11. An LED 9V battery tester circuit

CIRCUIT WIZARD – featured in this Teach-In series

Circuit Wizard is a revolutionary new software system that combines circuit design, PCB design, simulation and CAD/CAM manufacture in one complete package. Two versions are available, Standard and Professional.

By integrating the entire design process, Circuit Wizard provides you with all the tools necessary to produce an electronics project from start to finish – even including on-screen testing of the PCB prior to construction!

- * Circuit diagram design with component library (500 components Standard, 1500 components Professional)
- * PCB Layout
- * Virtual instruments (4 Standard, 7 Professional)
- * Interactive PCB layout simulation
- * On-screen animation
- * Automatic PCB routing
- * Gerber export

This is the software used in our Teach-In 2011 series. Standard £61.25 inc. VAT Professional £91.90 inc. VAT. See Direct Book Service – pages 75-77 in this issue

METRONOME

Description

A 555 timer is used in Fig.11.12 in an astable configuration. The frequency of the output is controlled by adjusting variable 'resistor' VR1, which varies the speed at which capacitor C1 is charged/discharged. As the output (pin 3) changes from 0V to 9V, LEDs D1 and D2 are lit alternately. Note that Circuit Wizard will not simulate the 'tick' that you would hear from the speaker as the output changes in the real circuit.

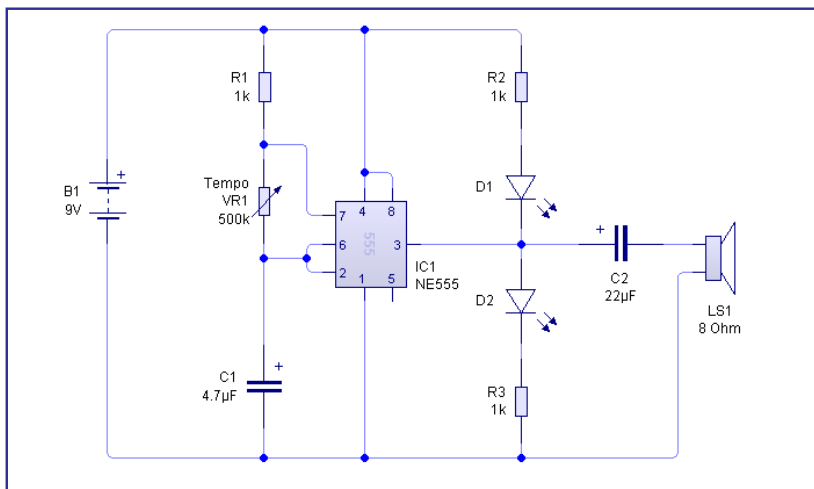


Fig.11.12. Metronome circuit using a 555 timer IC

Investigate:

1. What is the purpose of capacitor C2?
2. How could you add an additional range of tempo that would be (a) ten times slower or (b) ten times faster than the original rate? What single component would need to be changed?

TEMPERATURE-CONTROLLED FAN

Description

A simple potential divider-driven sensor circuit is shown in Fig.11.13. As the temperature changes, the resistance of the thermistor (R1) changes accordingly. This affects the voltage at the base of the transistor. Once this voltage is sufficient, the transistor will allow current to flow through the coil of the relay down to ground (0V), thus completing the fan circuit. Varying VR1 will adjust the point at which the fan is activated.


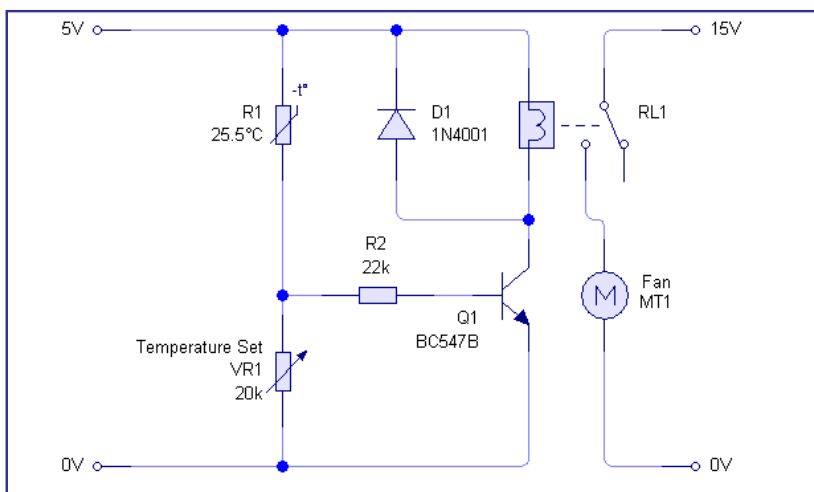


Fig.11.13 (above).
Temperature-controlled fan circuit

Investigate:

1. How could you improve this circuit by using an operational amplifier?
2. What would happen if the thermistor went open-circuit?
3. What does diode D1 do? Use the Internet and/or other resources to find out.

Fig.11.14 (right).
Answer to
Question 11.1

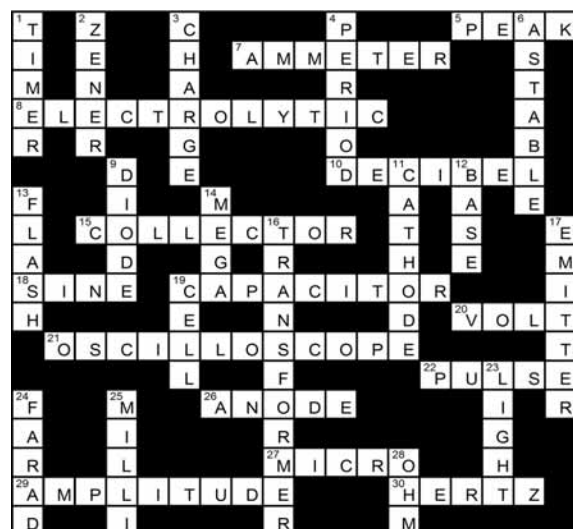

Answers to Check questions

11.1. See Fig.11.14

11.2. (a) switch (SPST)

(b) resistor (fixed)

(c) transformer (iron cored)

(d) light emitting diode (LED)

(e) capacitor (fixed, non-electrolytic)

(f) variable potentiometer

(g) electrolytic capacitor

(h) AND gate

(i) operational amplifier

(j) cell (or battery)

(k) preset potentiometer

(l) variable capacitor

(m) NPN bipolar junction transistor (BJT)

(n) R-S bistable (or flip-flop)

(o) bridge rectifier

11.3. (a) sinewave

(b) 40Hz

(c) 25ms

(d) 5V.

11.4. (a) pulse (repetitive)

(b) 5ms

(c) 200Hz

(d) 20%

(e) 3.5V

11.5. V; electric current; watt; farad;
 Ω ; hertz; bits per second

11.6. one volt; one amp; a power of one watt is equivalent to one joule of energy being used every second; one ohm; a signal has a frequency of one hertz if one complete cycle occurs every second

11.7. (a) 0.25V

(b) 150 μ A

(c) 68k Ω

(d) 235mW

(e) 220k Ω

(f) 0.885kHz

(g) 1.5nF

(h) 1200bps.

11.8. (a) resistors (4)

(b) preset potentiometers (2)

(c) slide switch (DPDT)

(d) light emitting diodes (2)

(e) transistors (2)

(f) electrolytic capacitors (2)

(g) printed circuit board

(h) battery (9V PP3 type)

(i) battery connector.

11.9. See Fig. 11.15

11.10. (a) electrolytic capacitor

(b) PNP transistor

(c) R1 and R2

(d) brown, red, yellow, gold

(e) RV1

(f) 6V

(g) 3.54V

(h) R2.

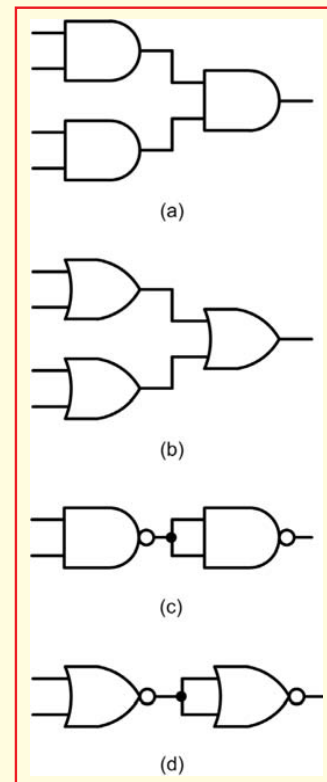


Fig.11.15. Answer to Question 11.9

Round-up

Over the last ten parts of our *Teach-In 2011* series, we've attempted to cover the core electronics syllabus taught in many schools and colleges in the UK. We've introduced each of the main topics studied at Level 2 (equivalent to GCSE) as well as a few that bridge the gap into further studies at Level 3 (equivalent to A-level).

'Build' provides you with eight additional circuits to build and investigate using the Circuit Wizard

software. All of these circuits can be modified and extended and we've suggested how this can be done and things that you might want to try. As mentioned previously in our series, you can learn a great deal by experimentation.

Finally, we tried to keep the mathematics to a level that is sufficient to understand and apply the underpinning theory (for example, to calculate the values required to achieve a particular time constant in a *C-R* circuit). If you are intending

to progress to higher level courses in electronics, you will require further study of mathematics at Level 3, but please don't let this put you off – the most important thing is to develop a 'feel' for how electronic circuits behave and the best way to do this is to do it the 'practical way'.

Good luck with your studies of electronics and don't forget that 'sums + circuits = understanding'!

Mike and Richard Tooley

TEACH-IN 2011 = *Topic Index*

555 timer	4-53, 7-44, 7-45	Cut-off frequency	5-52, 8-51, 8-49
556 timer	7-46, 7-53	D-type bistable	6-48, 6-50
741 operational amplifier	5-48	DAC	1-51, 9-47, 9-49
ADC	1-51, 9-49, 9-51	DIL package	6-50
AND logic	6-45, 6-47	Darlington transistor	4-48
Acceptor circuit	8-49	Decade counter	6-54
Accuracy	9-49	Decay	2-55
Active filter	8-50	Decibels	8-50
Ampere	1-51, 2-51	Depletion mode MOSFET	4-48
Amplitude	1-53	Dielectric	2-53
Analogue meter	10-43	Differential amplifier	5-52
Analogue signal	1-51, 9-47	Digital logic	6-44
Analogue-to-digital conversion	1-51, 9-46, 9-49	Digital meter	10-43
Anode	3-48	Digital signal	9-47
Astable oscillator	4-55	Digital-to-analogue conversion	9-47
Astable pulse generator	7-48	Digital-to-analogue converter	1-51
Attenuators	8-46	Diode characteristics	3-49, 3-51
Automatic light switch	5-56	Diodes	3-48, 3-52
Automatic routing	10-49	Discharge	2-54
BJT	4-46, 4-47, 4-48, 4-49	Dual timer	7-52
Balanced attenuator	8-47	Dual-in-line	6-50
Band-gap reference	9-49	Dual-slope ADC	9-51
Band-pass filter	8-47, 8-48, 8-57	Duty cycle	1-54
Band-stop filter	8-47, 8-48	Electric charge	2-54
Bandwidth	5-51, 8-50	Electrolytic capacitor	2-53
Base	4-46	Emitter	4-46
Batteries	1-54	Energy storage	2-54
Bias	3-48, 4-50	Enhancement-mode MOSFET	4-48
Binary	6-49, 9-46	Equivalent circuit	5-50
Binary-weighted DAC	9-48, 9-52	Exclusive-NOR logic	6-46, 6-47
Bipolar junction transistor	4-46, 4-47	Exclusive-OR logic	6-46, 6-47
Bistable	6-48	Exponential decay	2-55
Bits per second	1-51	Exponential growth	2-55
Block schematic	1-55	FET	4-46, 4-47
Boolean logic	6-46	Feedback	4-51
Bridge rectifier	3-50	Field effect transistor	4-46, 4-47
Buffer	6-46	Filters	8-47, 8-51
C-R circuits	2-54	Fixed resistor	2-51
C-R high-pass filter	8-48	Flash ADC	9-50
C-R low-pass filter	8-48	Follower	5-52, 5-53
CLEAR input	6-48, 6-49	Forward bias	3-48
CMOS	6-50	Frequency	1-53
CRT	10-44	Frequency response	5-51, 5-52
Capacitors	2-53, 2-57, 2-58	Full-wave rectifier	3-50
Cathode	3-48	Gain	4-53, 5-50, 5-51
Cathode ray tube	10-44	Gain-bandwidth product	5-51
Cells	1-54	Gates	6-45
Characteristic impedance	8-50	Germanium	3-49
Charge	2-54	Giga	1-52
Circuit Wizard	1-56, 10-48	Graticule	10-44
Collector	4-46	Growth	2-55
Collector load	4-50	Half-wave rectifier	3-50
Colour code	2-52	Hertz	1-51
Combinational logic	6-47	High-frequency cut-off	5-52
Common base	4-48	High-frequency roll-off	5-52
Common collector	4-48	High-pass filter	8-47, 8-48, 8-51, 8-50, 8-56
Common emitter	4-48	Input resistance	5-50
Common-emitter amplifier	4-49, 4-51	Integrated circuits	5-48
Comparator	5-53, 5-55	Intruder alarm	6-53
Complex waveform	1-52	Inversion	6-46
Counter	7-52	Inverter	6-46, 6-47
Current	1-51	Inverting amplifier	5-52, 5-54
Current gain	4-49, 4-53, 5-50, 8-50	Inverting input	5-49
Current measurement	10-43, 10-44	J-K bistable	6-48, 6-49
		JFET	4-48

Kilo	1-52	Pulse repetition frequency	1-53, 7-48
Kitchen timer	7-50	Pulse waveform	1-52, 1-53
L-C band-pass filter	8-49	Q-factor	8-50
L-C band-stop filter	8-49	Quantisation	9-46, 9-47
LDR	2-51	R-2R ladder DAC	9-48
LED	3-50, 3-51, 3-55	RESET input	6-48
LED flasher	7-51	Ramp waveform	1-52
Light-dependent resistor	2-51	Ramp-type ADC	9-50, 9-51
Light-emitting diode	3-50	Rats nest	10-51
Light-emitting diodes	3-51	Rectifier	3-50
Load	4-48, 4-50	Rectifier diode	3-49, 3-50
Logic	6-44, 6-47	Rejector circuit	8-49
Logic 0	6-44	Resistor colour code	2-52
Logic 1	6-44	Resistors	2-51
Logic gates	6-45, 6-46, 6-52	Resolution	9-49
Low-frequency cut-off	5-52	Resonance	8-49
Low-frequency roll-off	5-52	Reverse bias	3-48
Low-pass filter	8-47, 8-48, 8-51, 8-50, 8-55	Ripple counter	6-53
MOSFET	4-48	Roll-off	5-52
MSB	9-46	SET input	6-48
Matching	8-50	Sallen and Key filter	8-50
Mega	1-52	Saturated switch	4-52
Micro	1-52	Sawtooth waveform	1-52
Mid-band	5-52	Schematic diagram	1-55
Milli	1-52	Second-order filter	8-56
Monostable pulse generator	7-46	Semiconductor	3-48
Most significant bit	9-46	Signal diode	3-50
Motor control circuit	4-53	Signal diodes	3-49
Multimeters	10-42, 10-43	Signals	1-51, 1-50
Multiples	1-52	Silicon	3-49
Music	1-52	Simulation	1-56
N-type material	3-48, 4-46	Sinking	7-45
NAND logic	6-46, 6-47	Sourcing	7-45
NOT logic	6-46	Speech	1-52
NPN transistor	4-46, 4-47	Square wave generator	7-49
Nano	1-52	Sub-multiples	1-52
Negative feedback	4-51, 5-51	Successive approx. ADC	9-50
Non-inverting amplifier	5-52	T-network	8-47
Non-inverting input	5-49	TTL	6-50
OR logic	6-45, 6-46, 6-47	Temp.-sensitive resistor	2-51
Off state	6-44	Termination	8-50
Off time	1-53	Thermistor	2-51
Ohm	1-51, 2-51	Time constant	2-55
Ohm's Law	2-50, 2-56	Timer circuit	7-47
On state	6-44	Timing diagram	6-48, 6-49
On time	1-53, 7-46	Tolerance	2-51
Operating point	4-50	Transfer characteristic	4-49
Operational amplifier	5-48, 5-49	Transformers	3-50
Oscillator	4-55, 5-56	Transistor amplifier	4-54
Oscilloscope	10-44, 10-45	Transistor switch	4-51
Output resistance	5-50	Transistors	4-46
P-type material	3-48, 4-46	Triangle waveform	1-52
PCB	10-48	Trigger input	7-48
PNP transistor	4-46, 4-47	Unbalanced attenuator	8-47
PRESET input	6-48, 6-49	Valves	5-57
Parallel plate capacitor	2-53	Variable capacitor	2-53
Periodic time	1-53	Variable resistor	2-51
Phase shift	5-49	Virtual instrument	10-45
Photodiode	3-50	Virtual test	10-49
Pi-network	8-47	Volt	1-51, 2-51
Polarising voltage	2-53	Voltage follower	5-52, 5-53
Potentiometer	2-51	Voltage gain	5-50, 5-51, 8-50
Power gain	5-50, 8-50	Voltage measurement	10-43, 10-44
Power supplies	1-54	Watt	1-51
Pre-set resistor	2-51	Waveform measurement	10-45
Printed circuit board	10-48	Waveforms	1-52, 1-58
Pulse generator	7-46, 7-48	Zener diode	3-50, 3-51, 3-54
Pulse period	1-53		

Attending to noise and stability

CHAT ZONE contributor 741 posted the following question about using op amp amplifiers with gains of less than unity (that is attenuator circuits).

Is there any reason not to use a fractional gain inverting amplifier? Here is an example [See Fig.1], $V_o = -V_{in}/3$.?

If you build the circuit in Fig.1 there is a reasonable chance that it will work. However, it may prove to be unstable, depending on the op amp used and the gain setting. Furthermore, there are potential issues with noise and offsets.

Although 741 is interested in an inverting circuit, it is instructive to consider both basic op amp amplifier configurations – the inverting (Fig.2) and non-inverting amplifiers (Fig.3). We will need to use the properties of both circuits to analyse the inverting amplifier, as we will see later.

The expressions for closed-loop gain (circuit gain with feedback), A_{CL} , of the two amplifier configurations, are, with reference to Fig.2 and Fig.3: $-R_2/R_1$ for the inverting and $(1+R_2/R_1)$ for the non-inverting. These show that only the inverting circuit could be used directly as an attenuator. The '1' in the non-inverting gain equation ensures its gain cannot be less than one, irrespective of any practicalities as to what resistor values might be usable in a real circuit.

Feedback block

When analysing circuits and systems with feedback, it is common to abstract the design to a feedback block diagram. These are shown in Fig.4 and Fig.5 for the inverting and non inverting amplifiers respectively. We looked at this topic in depth in the April and May *Circuit Surgery*

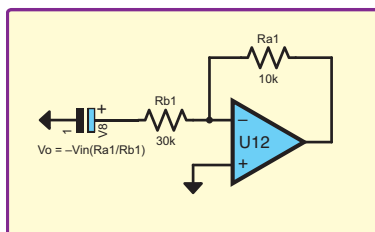


Fig.1. Copy of 741's first example circuit

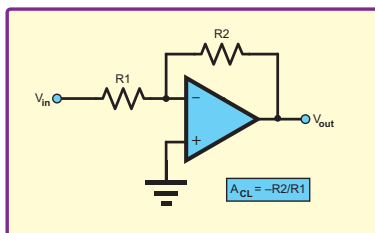


Fig.2. Op amp inverting amplifier

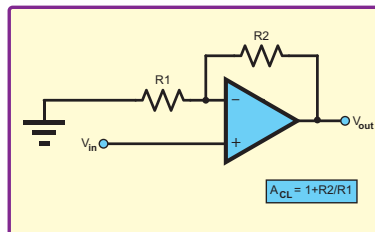


Fig.3. Op amp non-inverting amplifier

articles, so will not go into so much detail here. If you do not have the earlier issues an online search for 'negative feedback gain' should help.

In the feedback diagrams, A is the open-loop gain of the op amp and β is the feedback fraction – the proportion of the output which is fed back. α in the inverting circuit structure is also a scaling factor. In the May issue, we showed that $\alpha = 1-\beta$. Analysis of the

feedback structures provides us with generalised expressions for closed-loop gain (gain of the whole circuit) in terms of A , β and α .

$$\text{Inverting} \quad A_{CL} = \frac{\alpha A}{(1 + \beta A)}$$

$$\text{Non-inverting} \quad A_{CL} = \frac{A}{(1 + \beta A)}$$

We showed how to obtain these equations in detail in the April and May articles.

Of particular importance when considering these two equations is that A is typically very large (typically hundreds of thousands or millions for op amps) and β is typically a moderate fraction (say in the range hundredths to unity). Thus βA is typically much larger than 1 so $(1 + \beta A)$ is more or less the same values as βA . If we remove the 1 from the equations we can simplify them by cancelling out the A , leaving:

$$\text{Inverting} \quad A_{CL} = \alpha \frac{1}{\beta}$$

$$\text{Non-inverting} \quad A_{CL} = \frac{1}{\beta}$$

Inspection of the circuits in Fig.2 and Fig.3 reveals that the feedback is provided by the potential divider formed by the two resistors. Using the formula for a potential divider, we find that for both circuits:

$$\beta = \frac{R1}{(R1 + R2)}$$

From this, and given that $\alpha = 1-\beta$, we can easily derive the closed loop gain equations in terms of the resistor values. The fact that the β is the same for both configurations, but the closed-loop gains are different is of importance.

Noise gain

The value $1/\beta$ is called the **noise gain** of the circuit and is relevant to the amount of noise and offset we see at the

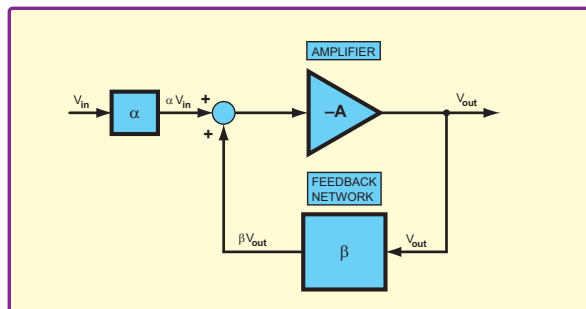


Fig.4. Feedback structure for the inverting amplifier (Fig.2)

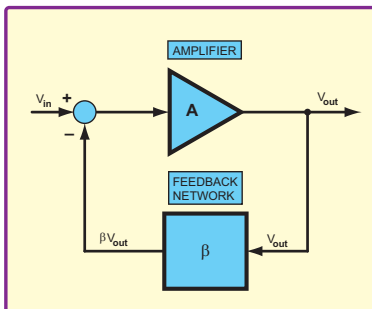


Fig.5. Feedback structure for the non-inverting amplifier (Fig.3)

output of both op amp amplifier configurations. We discussed noise in detail in last month's *Circuit Surgery*, so will not go into a lot of detail about how to perform noise analysis here. The noise voltage produced by an op amp, as stated on the datasheet, is input-referred to the non-inverting input. The noise voltage, v_{N^*} , stated (typically in nV/√Hz) can be viewed as a voltage source connected to a noiseless op amp, as shown in Fig.6.

To perform a noise analysis of the two op amp amplifiers in Fig.2 and Fig.3, we replace the op amps with the noise model shown in Fig.6. We also ground the input signal, as this is not included in the analysis (we assume it is noise free and so equal to 0V). This is shown in Fig.7 and Fig.8

It should be obvious that the two noise analysis circuits are identical, despite the fact that the original circuits were different. In both cases, as far as the noise voltage source is concerned, the circuit acts as a non-inverting amplifier with a gain of $1/\beta$, or $1 + R_2/R_1$ in terms of the component values.

The previous discussion leads us to the, perhaps surprising, conclusion that the gain by which noise is amplified is not necessarily the same as the closed-loop signal gain of the circuit. In both cases, the noise gain is $1/\beta$, which is why this term is referred to as noise gain.

For the inverting amplifier, the open-loop gain is $-R_2/R_1$ and the noise gain is $1 + R_2/R_1$. For large gains, this will not make much difference, for example if the inverting circuit gain is 200 the noise gain will be very similar at 201.

For small gains, however, the difference is more significant. If $R_2/R_1 = 0.3$, as in 741's fractional gain example, the circuit gain is -0.33 and the noise gain is four times larger at 1.33 .

Current input noise

So far, we have only considered the op amp's voltage noise; there is also current input noise (which is generally less significant) and noise from the resistors to consider. If the non-inverting input noise current flows through any impedances (it does not in our circuits) then the resulting voltage would be amplified by the noise gain. Noise in R_1 is amplified by the circuit voltage gain, not the noise gain.

Offset voltages are treated in a similar way to noise. The op amp's input offset voltage (another datasheet parameter) is represented like Fig.6, but with the input offset voltage instead of v_{N^*} and an offset-free amplifier. It follows that input voltage offsets are amplified by the noise gain and that, like noise, this may be significant in inverting amplifiers with low closed-loop gains.

Application of feedback to an amplifier may result in instability. This unwanted oscillation is very undesirable, so we need an understanding of how this might occur in order to design to prevent it. As we have seen, both standard basic op amp amplifier circuits use negative feedback and so may suffer from stability problems in certain circumstances.

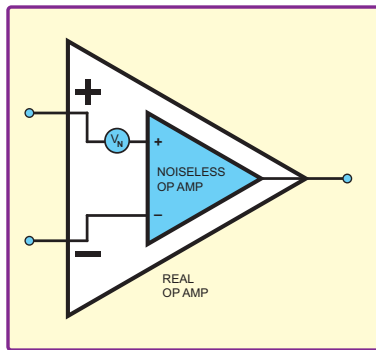


Fig.6. Representing the noise produced by an op amp

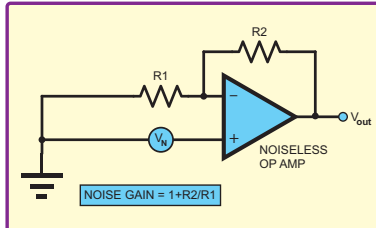


Fig.7. Op amp noise analysis for an inverting amplifier based on Fig.2. and Fig.6. Note this is the same as Fig.8.

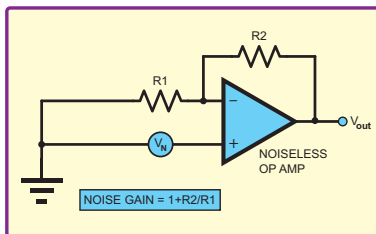


Fig.8. Op amp noise analysis for a non-inverting amplifier based on Fig.3. and Fig.6. Note this is the same as Fig.7.

Instability

Consider the closed-loop gain equation for the non-inverting configuration stated earlier:

$$A_{CL} = A / (1 + \beta A).$$

If the value of $(1 + \beta A)$ approaches zero, then closed-loop gain will approach infinity. This results in instability; specifically the circuit oscillates. The condition for which $(1 + \beta A) = 0$ is $\beta A = -1$. Since A and β have magnitude and phase shift it is often more useful to express the condition for instability as: $|\beta A| = 1$ and the phase shift due to βA is $\pm 180^\circ$. The vertical lines around $|\beta A|$ mean 'absolute value of' – that is the value of βA without regard to the sign.

Looking at the closed-loop equation for the inverting amplifier we see that the equation 'blows up' when $(1 + \beta A) = 0$ in exactly the same way as the non-inverting case. For a given op amp (and hence value of A) it is β that will determine the stability of the circuit. Thus, we can conclude that it is noise gain ($1/\beta$), rather than closed-loop circuit gain, which fundamentally influences the stability of both types of op amp amplifier.

Phase shift

It is the phase shift in the amplifier circuit which is responsible for instability, so it worth looking at this in more detail. The output of an amplifier does not respond infinitely quickly to changes at its input, so any signal fed back from the output to the input will be offset in time with respect to the original input.

Consider a simple case in which there is a fixed delay from input to output of a circuit whatever the input signal does (things are usually more complicated than this). Say, for example, this delay was $0.1\mu s$. If the input frequency was 100Hz this time would be 0.001% of the signal's cycle time and could probably be considered insignificant.

However, at 2.5MHz the $0.1\mu s$ delay is a quarter of the signal's cycle time of $0.4\mu s$. This would usually be expressed by saying that the circuit had a phase shift of 90° at 2.5MHz (one complete cycle of the waveform is 360°). At 5MHz $0.1\mu s$ is half the cycle time of the signal. This is a significant point because a phase shift of 180° is equivalent to multiplying the signal by -1 .

Consider the total phase shift through the amplifier and feedback network as we increase the input signal frequency. Once this reaches 180° we have effectively inverted our feedback signal – what was negative feedback has become positive feedback. Positive feedback is what you need to make an oscillator, so our amplifier may become unstable.

The reason that all amplifiers do not become oscillators is because as frequency and hence phase shift increase the gain decreases. By the time the phase shift has reached 180° the gain has hopefully decreased below the point at which oscillation can be sustained (it is less than unity).

Phase and gain margins

If we are building an amplifier we must avoid oscillation and it is useful to know how far away our circuit is from potential instability. This can be measured in a couple of related ways – phase margin and gain margin.

As $|\beta A|$ approaches 1, the phase shift is less than 180° . The difference between the phase at this point and 180° is the *phase margin*.

As the phase shift of βA approaches $\pm 180^\circ$ $|\beta A|$ may be less than 1. This difference can be expressed as the *gain margin* (usually in dB).

Gain margin and phase margin are illustrated in Fig.9, which shows the variation of $|\beta A|$ and phase shift of βA with signal frequency. Note that a gain of 1 is 0dB and that the phase shift is negative because the output lags behind the input signal in time.

The larger the feedback fraction β the more 'difficult' it is to fulfil the gain and phase margin stability criteria because the feedback signal is stronger and less likely to get down to unity by the time the phase shift gets to 180° . Thus a circuit configuration could, for example, be stable with $\beta=0.5$, but not with $\beta=1.0$. It is not just the designed components which affect

stability – things like circuit load and stray capacitance can have a significant impact on the variation of $|\beta A|$ and the phase shift of βA with signal frequency.

The decrease in gain with frequency for an op amp is not arbitrary, it is part of the design of the op amp. Introducing circuitry to modify how gain and phase shift change with frequency in such a way as to ensure stability is known as **compensation**. Most op amp ICs are compensated to guarantee stability down to unity gain, but not all are. If an op amp is only guaranteed stable down to, say, a gain of 5 then it will not be stable in the circuit in Fig.1.

The fact that noise gain and circuit gain are different gives us some potential to trade off noise/offset and stability. We can make the noise gain higher for stability, while keeping the low circuit gain (attenuation). An example is shown in Fig.10. The gain for the signal is $-R_2/R_1$ as before because as far as the inverting circuit is concerned R_3 is like an input to a summing amplifier with zero signal applied. When we analyse the circuit in Fig.10 as a non-inverting amplifier working on the noise we use the parallel combination of R_1 and R_3 rather than

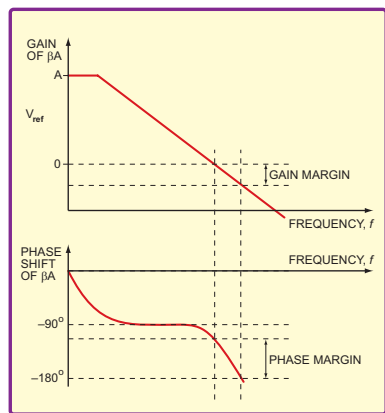


Fig.9. Variation of a $|\beta A|$ and phase shift of βA with signal frequency illustrating gain margin and phase margin

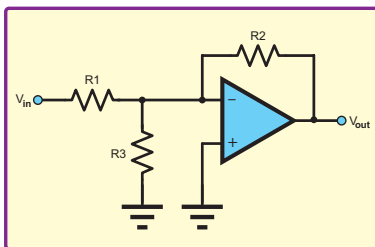


Fig.10. Adding a resistor to adjust the noise gain for stability

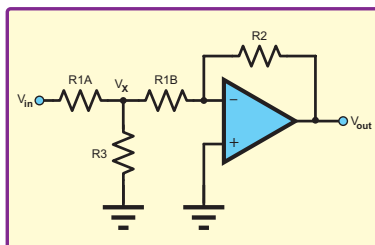


Fig.11. Stable inverting attenuator

just R_1 in the gain calculation (call this R_p) so the noise gain is $1+R_2/R_p$.

Using the same values as Fig.1 and adding $R_3=5k\Omega$ would give a noise gain of 3.3, which may be more stable than 1.3. The circuit gain is still 0.33.

Fig.11 shows another op amp attenuator, this is like Fig.10, but with R_3 connected in the middle of a split R_1 . Calculation of resistor values for this circuit is more complex, but is simplified if we use normalised values and then scale up to the required resistance values later. For this reason we set $R_{1A} = R_{1B} = 1$ and $R_2 = 2$.

We can think of the circuit in Fig.11 as an inverting amplifier amplifying the voltage, V_x , at the R_1/R_3 junction. The gain of this amplifier is 2 by virtue of the normalised values we have already set. The voltage V_x is given the action of the potential divider formed by R_1 and R_3 on the input voltage. More specifically, this potential divider is formed by R_{1A} and the parallel combination of R_{1B} and R_3 (call this parallel value R_p). The total

gain of the circuit, G , is therefore the inverting amplifier gain (2) times the potential divider factor, so we have:

$$G = \frac{2R_p}{(R_3 + R_p)}$$

The value of R_p is as follows (noting that $R_{1B} = 1$):

$$R_p = \frac{R_3}{(R_3 + 1)}$$

We substitute this value of R_p into the equation for G and obtain an expression which just contains G and R_3 . After a bit of algebraic manipulation to rearrange and simplify things, we can get a formula to set R_3 based on the gain we want.

$$R_3 = \frac{G}{(2 - 2G)}$$

For example, for a gain of one third (as in Fig.1) we get $R_3 = 0.25$. If we choose $R_{1A} = R_{1B} = 10k\Omega$, the other values scale proportionally, so $R_2 = 20k\Omega$ and $R_3 = 2.5k\Omega$. If the source driving V_{in} has significant output impedance this should be taken into account when selecting resistor values (eg, by reducing R_{1A} accordingly).

There is a useful article from Bruce Carter of Texas Instruments which discusses the attenuator circuit in Fig.11 in more depth, and also looks at a fully differential version. According to the article, there is an online utility (called RESISTOR-CALC) on TI's website which will calculate resistor values for this circuit, but at the time of writing it did not seem to be functioning.

Reference

Bruce Carter, 'Op amp attenuators', *Texas Instruments Analogue Applications Journal*, Fourth Quarter, 2003, pages 28 to 30. <http://focus.ti.com/lit/an/slyt051/slyt051.p>

Radio Bygones

The Leading Magazine For Vintage Radio Enthusiasts

Radio Bygones includes articles on restoration and repair, history, circuit techniques, personalities, reminiscences and just plain nostalgia – you'll find them all. Plus, features on museums and private collections.

It is mostly about valves, of course, but solid-state – whether of the coherer and spark-gap variety or early transistors – also has a place.

From the days of Maxwell, Hertz, Lodge and Marconi to what was the state-of-the-art just a few short years ago.

There is also a selection of free readers' For Sale and Wanted adverts in every issue.

The magazine is published six times a year, and is only available by postal subscription.

Subscription Prices: UK £25.00, Europe £27.00, Rest Of The World £32.00 (one year).

It is not available in newsagents.

Radio Bygones is published by Wimborne publishing, 113 Lynwood Drive, Merley, Wimborne, Dorset, BH21 1UU. Tel: 01202 880299.

To take a subscription or request a sample copy (cost £5.00 to UK) then please do not hesitate to contact us.

Radio Bygones

August/September 2011
Issue No. 132


ISSN 0956-974X

The Lasky Skyrover Mark II Receiver



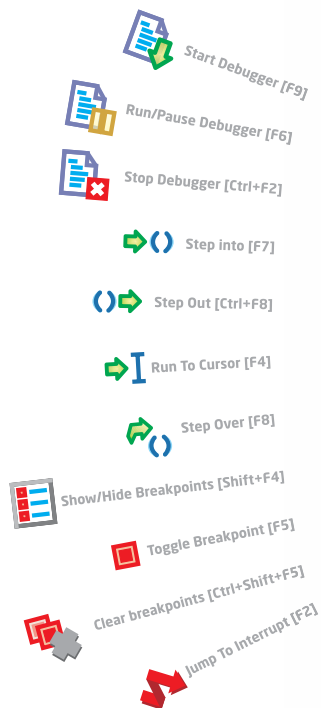Search And Rescue Radios
The Complex Development Of L, M & S
Microwave Cavity Resonators – A Tale Of Spies,
Bugs And Lizards





www.radiobygones.com



mikroProg™ \$99

programmer and In-Circuit Debugger

One programmer to rule them all.

 <p>One programmer for 574 devices</p> <p>All PICs covered</p> <p>PIC10, PIC12, PIC16, PIC18, dsPIC30/33, PIC24 and PIC32, we have it all covered. You'll never need another programmer!</p>	 <p>In-Circuit Debugger Supported</p> <p>Fast mikroICD™ debugger</p> <p>Debug your code and monitor code execution on the chip itself. mikroICD™ technology brings the power of hardware debugging to your favorite mikroE compiler.</p>
 <p>Single firmware takes care of it all</p> <p>Supporting new chips is easy</p> <p>Adding new chips is easy. Just download the latest mikroProg Suite Software, and new devices will be available using the same hardware and the same firmware inside!</p>	 <p>Support in 9 mikroE compilers</p> <p>Compiler Compatibility</p> <p>mikroProg™ is supported with mikroC, mikroBasic and mikroPascal compilers for PIC, dsPIC and PIC32.</p>



Max's Cool Beans

By Max The Magnificent

Acting mentor

Recently, I've been hearing from young engineers who have started their first jobs, but are finding themselves out of their depth with nowhere to turn. The way things used to work when I began my career was that each newcomer was assigned to an older, more experienced engineer who acted as a mentor. If you were lucky – and I was – you got someone who delighted in teaching you the tricks of the trade.

After graduating with a BSc in control engineering in the summer of 1980, my first position ('Look mum, a real job!') was with International Computers Limited (ICL) in Manchester, England. At that time, ICL made honking big mainframe computers, and I was hired as a member of one of their central processing unit (CPU) design teams.

It didn't take me long to discover that little of what I'd studied at college had much bearing on my new job. I also quickly realised that tasks that had appeared easy in the classroom were somewhat trickier when you had to do them in earnest. Fortunately, ICL had a really good policy whereby junior engineers like me were partnered with more experienced team leaders. I was lucky in this regard to be assigned a mentor called Dave Potts, who taught me far more than I'm sure he ever realised.

As one example, my first task at ICL was to design a 128-bit barrel shifter/rotator; that is, a unit that could shift or rotate the contents of the 128-bit data bus by any amount from 1 to 128 bits in a single clock cycle. The idea was to design a special silicon chip and to then use eight of these chips to implement the shifter/rotator, where each chip would handle a 16-bit chunk of the data bus. All of the chips were to be functionally identical in order to keep the project within budget.

As an aside, I should point out that we were designing gate-level schematics using pencil and paper; also, the chips in question each contained only around 2,000 equivalent logic gates (these devices were considered to be pretty much state-of-the-art at the time).

Initially, my task didn't appear to be particularly arduous. The only tricky details involved working out what data I needed to 'stuff' into the 'ends' of the shifter/rotator. In the case of a logical shift right, for example, you shift the appropriate number of logic 0 values into the left-hand side of the shifter. By comparison, in the case of an arithmetic shift right, you shift in copies of the original sign bit. As I recall, part of my solution was to employ a couple of the pins on each of the chips to act as a device ID. These pins could be hardwired to logic 0 and 1 values on the circuit board, thereby informing each chip as to its position in the chain.

When I'd completed the first part of the exercise, Dave deigned to inform me that he'd neglected one slight detail, which was that – in addition to being able to process all 128 bits from the data bus – the shifter/rotator also had to be capable of working with only the least-significant 64 bits or the least-significant 32 bits.

So my task had just become a little trickier, but it still wasn't all that bad and a few days later I returned with my latest offering. 'Ah, Ha!' said Dave, 'Now we're getting there, but in addition to working with binary values, this device also has to be able to handle 128, 64, or 32-bit binary-coded decimal (BCD) data.'

Dave then proceeded to explain the concepts behind BCD in general, along with what shifting/rotating this form of data entailed. For example, since each BCD digit occupies four bits, it was only possible to perform shifts in four-bit (one nibble) increments. Also, when performing an arithmetic shift right, I had to shift an appropriate number of copies of the sign nibble into the left-hand side of the shifter.

And so it went. Every time I finished working on a problem, another feature would be added to my portion of the project. In reality, of course, the main specification already contained all of these details, but if I'd been presented with the full requirements on my first day, my brains would have leaked out of my ears and I would have been reduced to a gibbering wreck.

Endless patience

The great thing was that Dave was endlessly patient and he was always available to answer questions and to offer suggestions as to different ways to do things and cunning logic tricks one might employ. Looking back with hindsight (the one exact science) I realise just how lucky I was. If I had simply been presented with the full-up specification for the shifter/rotator on the first day, I wouldn't have known where to start. The result could well have been to ruin my self-confidence and to leave me feeling like a failure, which would almost certainly have negatively affected the rest of my career. By comparison, the way Dave broke things down into sub-projects, only ever giving me tasks I could handle (even if I had to think about them for a while) really built up both my knowledge and my confidence.

Any ideas?

The problem is that very few companies seem to use any form of mentoring these days. Instead, they take the attitude that when a student leaves college he or she should be ready to hit the ground running. In my experience, this is rarely the case. Of course, there are various online training resources available for continuing education, but there's nothing as good as having access to someone more experienced with whom you can ask questions and bounce ideas around.

How about you? Have you had experiences of this sort of thing – either as a mentor or as a new engineer who had (or did not have) a mentor? And what would you suggest that newcomers to the industry do in the absence of a mentoring program? Please write in to the *EPE* letters page and share your insights with the rest of us.

Until next time, have a good one!



Practically Speaking

Robert Penfold looks at the Techniques of Actually Doing it!

IF YOU are not careful, locating and buying all the components for a project can be a very time consuming business. Going about things in a totally disorganised fashion could result in more time being spent obtaining the components than actually assembling them! It is probably fair to say that the size and complexity of electronic projects has reduced somewhat over the years, and the days when a 'mega' project had to be carefully assembled over a period of weeks or even months are probably behind us.

Even so, many projects require a fair number of components, and obtaining a full set of them is potentially a time-consuming business. It is worth putting in some time and effort into getting to know the strengths and weaknesses of the various component suppliers. Where there are printed catalogues available it is a good idea to obtain them and to spend some time studying their contents.

Information superhighway

As with much else in the retail world, the sale of electronic components is now largely via online ordering rather than over-the-counter or using traditional mail or telephone ordering. While it is not essential to have an Internet connection in order to pursue the hobby of electronic project construction, being without one is likely to be a significant hindrance.

In addition to providing access to online electronic component catalogues, the Internet makes available a huge amount of data and other information from the websites of the semiconductor manufacturers. In fact, there is a massive amount of information available on a wide range of components, from simple passive types such as resistors and capacitors to the highly specialised devices such as gas sensors. Last, and certainly not least, there is the *EPE* website and Alan Winstanley's highly regarded guide to soldering (www.epemag.wimborne.co.uk/solderfaq.htm).

Whether you rely on a conventional catalogue, the online variety, or a mixture of the two, it is a good idea to study them carefully. Apart from learning the types of component available from each source, component

catalogues often have a great deal of information that is helpful to beginners.

There will often be some connection data for semiconductors, physical dimensions and mounting details for switches, relays, and so on. In the case of online catalogues, there will be links to the manufacturers' data sheet for many of the components, and for practically all of the semiconductors.

Mail order

Postage and packing charges can add significantly to the cost of building a project, but this just has to be accepted as a fact of project building life. In order to minimise this additional cost it obviously makes sense to obtain all the components from a single source, but in many cases it is likely that there will be no single supplier that has everything required.

Many projects have one or two highly specialised components such as sensors and complex integrated circuits, and these might have to be obtained from a different source to the other parts. If the project is based on a custom printed circuit board (PCB) it will have to be obtained separately, unless you make your own. Initially, it is advisable to use ready-made boards.

It helps if you plan ahead by purchasing the components for two or three projects at a time so that the number of orders is minimised. The suppliers that deal mainly with hobbyists either have no minimum order value, or if there is one it will be set at a relatively low level. The large professional suppliers of electronic components have an amazing range on offer, and will accept orders from non-professional customers. These days they are very important sources of supply, but there will typically be a minimum order value of about £20 for non-account customers.

Again, planning ahead can be useful here, and can help to bring an otherwise inadequate order value above the minimum order threshold, in addition to keeping down postage costs. It also helps to bear in mind that these large professional suppliers offer more than just electronic components. If you need some hacksaw blades, or a new hacksaw for that matter, there will probably be several to choose from.

Stock market

There is a risk of delays occurring when you finally start construction and discover that a commonplace but crucial component has been overlooked or is broken. Delays can also occur if one or more of the parts are out of stock at the retailer. Improvements in logistics mean that delays of this type tend to be relatively rare and short these days, but they can still be very frustrating.

I would guess that every electronic project builder decides sooner or later that it is worth having a stock of the more everyday components. This removes the need to buy every single component for a project, right down to the last nut and bolt. The expensive and more specialist items still have to be purchased in the normal way, but all or most of the more mundane components are taken from a stock of such items. This makes ordering the components much quicker and can help to avoid frustrating 'out of stock' delays.



Fig.1. Although small resistors such as these are available in a large range of values, producing a large stock of them does not have to cost very much

The obvious problem when building up a stock of components is to decide which ones to buy. There is no point in buying components that will not be used for many years, or never at all. It is probably best not to stock any expensive components at all. Doing so would greatly increase the cost of the stock, and there would be no guarantee that any of the highly priced components would ever be used. Even a few remaining unused would represent a substantial waste of money.

Building up a stock of inexpensive components is a different matter. However, even with these it makes sense to concentrate on components that are used very frequently. Resistors are the obvious starting point, as they are the cheapest electronic components and are probably used in larger numbers than any other type of electronic part.

Even with resistors you have to take a down-to-earth approach since there is no point in building up a stock of the more expensive and rarely used types. This mainly means close tolerance (1%) or high wattage types.

Most projects use carbon film resistors having a power rating of about 0.25 to 0.5 watts and a 5% tolerance rating (Fig.1). These are very cheap, require little storage space, and it does not cost a fortune to buy several hundred of them.

This is just as well, since resistors come in a very wide range of values, many of which are used a great deal. Obtaining several of each value therefore means buying at least a few hundred resistors. Some resistor values crop up much more often than others, so it is advisable to buy more of the popular values and less of the ones that are used infrequently.

It tends to be the middle values from about 1k Ω to 100k Ω that are used the most. Values above 1M Ω and below 100 Ω are used very infrequently. Probably the most popular values of all are 1k Ω , 4k7, 10k Ω , 47k Ω , and 100k Ω , with the closest values to these (820 Ω , 1k2, 3k9, etc.) being used very much less. The extra values in the E24 series (1.1, 1.3, 1.6, etc.) are not used a great deal in projects, and it is not worth stocking them.

Under development

The resistor development packs offered by some suppliers represent the easiest way of obtaining a large stock of resistors. Few offer a full range of values, and they typically cover all the normal E12 range of values from 10 Ω to 1M Ω . Presumably, because the very high and low values are little used in modern circuits they are not usually included, but it is helpful if a few of these are obtained separately. The resistor kits currently on offer do not seem to vary the quantities to suit the typical usage of each one, so it can



Fig.2. In order to be really useful a stock of components must be well organised so that the required parts can be located quickly. Inexpensive miniature chests of drawers are idea for storing components in an organised fashion

be useful to buy extra supplies of the most popular values. An advantage of buying a large resistor pack is that the price per resistor can be relatively low, and in some cases is well under one pence per resistor.

The advice often given by magazines in the past, was to build up a stock of resistors by obtaining two or three times as many as you actually needed. For example, if a project needed three 10k Ω resistors you would actually order six or nine of them. The big advantage of this method is that there is no 'up front' cost, and you should barely notice the increase in the cost of each components order. The drawback is that it can take quite a while to build up a really useful stock of resistors.

There is another advantage to this method, which is its built-in weighting. Without having to put any thought or effort into it, you will buy larger quantities of the popular values, and fewer of those that are little-used. The quantities needed in the past will not necessarily reflect your future needs with a high degree of accuracy, but in practice, it likely to be more accurate than any other method.

Of course, the same method can be applied to other components, but it should only be applied to the cheaper and more frequently used components. It cannot usefully be applied to any components that cost more than 'peanuts' or are in any way out of the ordinary.

High capacity

Building up a useful stock of capacitors is likely to be more difficult than producing a stockpile of resistors. As with resistors, a huge range of values

is involved, but with capacitors there is also a variety of different types in common use. With mid-range values of around 10nF there could well be ten or twenty different types to choose from. I suppose this is simply a reflection of the fact that nothing approaching the perfect capacitor has yet been developed.

Circuit designers, therefore, have to select a type of capacitor that has suitable characteristics for each application. One application might require capacitors that are designed to work efficiently at high frequencies, while in another circuit it may be high stability and accuracy that is required. Some applications are undemanding and will work well enough with any capacitor of the correct value, but substituting a capacitor from stock where one of a different type is called for will not necessarily have the desired result.

These days, most capacitors are of the printed circuit mounting (PCM) variety, and have pins rather than long leadout wires. A capacitor of a given type can be available with two or more pin separations. While it is not impossible to use a component having the wrong pin spacing, it does not always work well and is best avoided. A further complication is that some capacitors are still available in axial versions. This is the type that has a leadout wire at each end of a tubular body, like normal resistors.

Producing a comprehensive stock of capacitors is not really a worthwhile proposition, it would require a huge number of relatively expensive components. The over-buying method can be used with capacitors, but it should be restricted to the cheapest



Fig.3. Most storage drawers have provision for adding labels that make it easier to find the required components

types. Over-buying with something like a very high value component or a precision type would probably be a waste of money. However, it can be worthwhile producing a stock of the more common capacitors, but it is necessary to buy them very selectively.

Probably due to their very wide tolerances, electrolytic capacitors are only generally available in the E6 range of values. They are only used to a great extent in what could be termed the E3 range (1, 2.2, 4.7, and their decades), so it is probably best to only bother with these values. The axial types seem to be used very little these days, so it is probably best to concentrate on the printed circuit mounting type. Values from $1\mu\text{F}$ to about $100\mu\text{F}$ are used a great deal, so a few of each value from this range should prove useful.

Components having a maximum working voltage of about 50V to 100V should be chosen for values up to $10\mu\text{F}$, but a lower voltage rating of about 16V to 25V will suffice for the higher values.

In modern electronics there seems to be relatively little need for high quality capacitors having low values, and very low values are not used much at all. It is still worthwhile having some inexpensive ceramic or ceramic plate capacitors in the E6 range from about 10pF to 1nF. Capacitors from 1nF to about 470nF are mostly of the plastic foil variety (polyester, Mylar, polycarbonate, etc.), and in general it does not matter which type is used. As explained previously, the main problem is the physical differences. Having a few of each value in the E12 range with several different lead pitches would be very useful, but could be expensive.

As with resistors, it is possible to obtain development packs, but these usually have a selection of one type of capacitor rather than a broad range of values and types. In order to produce a

good stock of capacitors it is necessary to have at least three or four different types. On the plus side, development packs usually represent a very cheap way of buying capacitors.

There are a few other components that it is worth buying for stock. Some general purpose silicon diodes such as the 1N4148 or 1N914 are well worth having, as are some small rectifier diodes, such as the 1N4007. Some of the more simple switches, such as the miniature toggle types are likely to be useful, as are PP3 battery clips and a large reel of solder.

It is certainly a good idea to have the popular items of hardware in stock, such as nuts, bolts, spacers, and stand-offs. Some of these are only available in largish quantities, so you will probably end up with a stock of them as a natural part of the buying process.

Storage

Having obtained a large stock of components it is essential to store them sensibly. Simply placing everything into one or two large boxes will make it difficult to find any given component. The more things are compartmentalised, the quicker and easier it will be to find the component you require. It is not difficult to make or improvise your own storage system using biscuit tins and the like. Alternatively, miniature chests of plastic or plastic and metal storage drawers (Fig.2) can be obtained from DIY superstores and elsewhere at quite low prices.

The least expensive types are adequate for an application such as this, where mainly very light bits and pieces will be stored. Organise things sensibly with (say) all the resistors from 10Ω to 82Ω in one drawer, those from 100Ω to 820Ω in another, and so on. Label each drawer so that you can quickly locate the one that contains the part you are looking for (Fig.3).

MIACTM

Now you are in control



The MIAC rugged PICmicro microcontroller is an industrial grade controller which can be used to control a wide range of different electronic systems: for mains switching, motor control, sensor monitoring and much more.

Free Flowcode 3 with every MIAC



- ▶ Rugged PIC 18F4455
- ▶ Programmable from USB - download software provided
- ▶ Compatible with third party PICmicro, BASIC and C compilers
- ▶ Includes free Flowcode 3 graphical programming software (no upgrade rights)
- ▶ 8 digital or analogue inputs
- ▶ 4 relay outputs - 8A
- ▶ 4 motor outputs with speed control - 12V, 500mA
- ▶ 4 line 16 character display
- ▶ Control keypad
- ▶ Fully networkable via built in CAN bus
- ▶ Lab View and Visual Basic compatible - DLL supplied
- ▶ In-Circuit Debug over USB with FlowKit


MATRIX

www.matrixmultimedia.com

101: C on PIC16F818

**FUN PROJECTS
WITH MY CCS COMPILER**

\$149

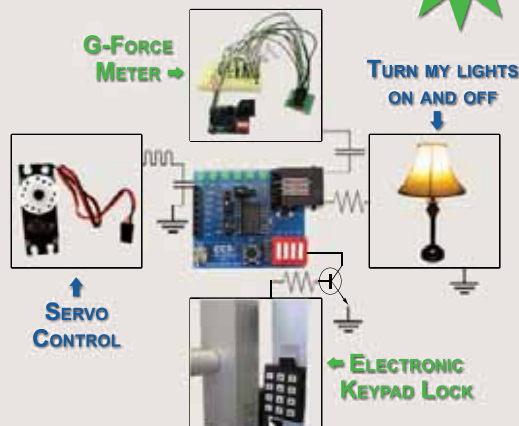

**EVERYTHING YOU NEED TO START A
PROJECT WITH C AND PIC®MCU**

You GET: + + +

WWW.CCSINFO.COM/EDPE

PHONE: 262-522-6500 x35 • SALES@CCSINFO.COM

PIC®MCU and dPIC®DSC are registered trademarks of Microchip Technology, Inc.



**CRICKLEWOOD
ELECTRONICS**
Established 1981



Frustrated with your supplier?
Visit our component packed
website for a vast range of
parts - old and new,
many unavailable elsewhere!
www.cricklewoodelectronics.com

1000's OF PRICES REDUCED!

Alternatively phone us on
020 8452 0161 with your
requirements.



**Visit our Shop, Call or Buy online at:
www.cricklewoodelectronics.com**

020 8452 0161 Visit our shop at:
40-42 Cricklewood Broadway
London NW2 3ET

SHERWOOD ELECTRONICS

Buy 10 x £1 Special Packs and choose another one FREE

SP1	15 x 5mm Red Leds	SP131	2 x TL071 Op-amps
SP2	12 x 5mm Green Leds	SP133	20 x 1N4004 diodes
SP3	12 x 5mm Yellow Leds	SP134	15 x 1N4007 diodes
SP5	20 x 5mm 1 part Led clips	SP135	5 x Miniature slide switches
SP6	15 x 3mm Red Leds	SP136	3 x BFY50 transistors
SP7	12 x 3mm Green Leds	SP137	4 x W005 1.5A bridge rectifiers
SP8	10 x 3mm Yellow Leds	SP138	20 x 2.2/63V radial elect caps
SP9	20 x 3mm 1 part Led clips	SP142	2 x Cmos 4017
SP10	100 x 1N4148 diodes	SP143	5 Pairs min. croc. clips (Red+Blk)
SP11	30 x 1N4001 diodes	SP144	5 Pairs min. croc. clips (assorted colours)
SP12	30 x 1N4002 diodes	SP146	10 x 2N3704 transistors
SP16	20 x BC182B transistors	SP151	4 x 8mm Red Leds
SP20	20 x BC184B transistors	SP152	4 x 8mm Green Leds
SP23	20 x BC549B transistors	SP153	4 x 8mm Yellow Leds
SP24	4 x Cmos 4001	SP154	15 x BC548B transistors
SP25	4 x 555 timers	SP160	10 x 2N3904 transistors
SP26	4 x 741 Op-amps	SP161	10 x 2N3906 transistors
SP28	4 x Cmos 4011	SP164	2 x C106D thyristors
SP29	3 x Cmos 4013	SP165	2 x LF351 Op-amps
SP33	4 x Cmos 4081	SP166	20 x 1N4003 diodes
SP34	20 x 1N914 diodes	SP167	5 x BC107 transistors
SP36	25 x 10/25V radial elect caps	SP168	5 x BC108 transistors
SP37	12 x 100/35V radial elect caps	SP172	3 x Standard slide switches
SP38	15 x 47/25V radial elect caps	SP173	10 x 220/25V radial elect caps
SP39	10 x 470/16V radial elect caps	SP174	20 x 22/25V radial elect caps
SP40	15 x BC237 transistors	SP175	20 x 1/63V radial elect caps
SP41	20 x Mixed transistors	SP177	10 x 1A 20mm quick blow fuses
SP42	200 x Mixed 0.25W CF resistors	SP178	10 x 2A 20mm quick blow fuses
SP47	5 x Min. PB switches	SP181	5 x Phono plugs - assorted colours
SP49	4 x 4 metres stranded core wire	SP182	20 x 4.7/63V radial elect caps
SP102	20 x 8 pin DIL sockets	SP183	20 x BC547B transistors
SP103	15 x 14 pin DIL sockets	SP186	8 x 1M horizontal trim pots
SP104	15 x 16 pin DIL sockets	SP189	4 x 4 metres solid core wire
SP109	15 x BC557B transistors	SP192	3 x Cmos 4066
SP112	4 x Cmos 4093	SP195	3 x 10mm Yellow Leds
SP115	3 x 10mm Red Leds	SP197	6 x 20 pin DIL sockets
SP116	3 x 10mm Green Leds	SP198	10 x 24 pin DIL sockets
SP118	2 x Cmos 4047	SP199	4 x 2.5mm mono jack plugs
SP124	20 x Assorted ceramic disc caps	SP200	4 x 2.5mm mono jack sockets
SP130	100 x Mixed 0.5W CF resistors		

RESISTOR PACKS - C.Film

RP3	5 each value - total 365 - 0.25W	£3.55
RP7	10 each value - total 730 - 0.25W	£4.85
RP10	1000 popular values - 0.25W	£6.90
RP4	5 each value - total 305 - 0.5W	£4.45
RP8	10 each value - total 610 - 0.5W	£7.20
RP11	1000 popular values - 0.5W	£9.75

Catalogue available £1 inc. P&P
or **FREE** with first order.

P&P £2.25 per order. NO VAT
Cheques and Postal Orders to:

**Sherwood Electronics,
10 NEWSTEAD STREET,
MANSFIELD, NOTTS.
NG19 6JJ**

Technobots

Electronic & Mechanical Components

With over 5,100 products available to order online, Technobots
provides one of the widest range of components for the
electronics and engineering enthusiast



Education Accounts
Welcome

www.technobotsonline.com

Shop callers welcome: Technobots Ltd, 60 Rumbridge Street,
Totton, Hampshire SO40 9DS Tel: 023 8086 4891

Ingenuity Unlimited

Readers' Circuits

Our regular round-up of readers' own circuits

WIN A PICO PC-BASED OSCILLOSCOPE WORTH £799

- 200MHz Analogue Bandwidth Dual Channel Storage Oscilloscope
- Spectrum Analyser • Frequency Meter • Multimeter • USB Interface.

If you have a novel circuit idea which would be of use to other readers then a Pico Technology PC-based oscilloscope could be yours. After every 20 published IU circuits, Pico Technology will be awarding a PicoScope 3206 digital storage oscilloscope for the best IU submission. In addition a PicoScope 2105 Handheld 'Scope worth £199 will be presented to the runner up.

We pay between £10 and £50 for all material published, depending on length and technical merit. We're looking for novel applications and circuit designs, not simply mechanical, electrical or software ideas. Ideas must be the reader's own work and **must not have been published or submitted for publication elsewhere.**

The circuits shown have NOT been proven by us. **Ingenuity Unlimited** is open to ALL abilities, but items for consideration in this column should be typed or word-processed, with a brief circuit description (between 100 and 500 words maximum) and include a full circuit diagram showing all component values. **Please draw all circuit schematics as clearly as possible.** Send your circuit ideas to: Ingenuity Unlimited, Wimborne Publishing Ltd., 113 Lynwood Drive, Merley, Wimborne, Dorset BH21 1UU. Email: editorial@epemag.wimborne.co.uk. **Your ideas could earn you some cash and a prize!**



Low-Battery Indicator – Go/No-go

HAVE encountered many low-battery indicators which flicker under transient conditions, as though they are unable to 'decide' if the battery is flat or not.

The circuit diagram for a relatively simple low-battery indicator is shown in Fig.1. The voltage of the battery, reduced to a suitable level by a resistor network, is compared with a reference voltage derived from the regulated output, such that the output of the first comparator goes low when the battery voltage is less than 7.25V. (Hence the circuit in its present form is unsuitable for use with NiCad or NiMH batteries, which don't offer a

high enough voltage, even when fully charged).

This output triggers a second comparator, which has so much feedback applied (between pins 5 and 7) that it effectively becomes a latching device, similar to an unusually sensitive thyristor. Correct operation may be verified by momentarily grounding the test point (TP1) at pin 5 of IC1b. The feedback resistance may be decreased in the unlikely case that good performance is not achieved using the components shown.

A low output lights the 'Low Bat' LED, and simultaneously diverts current away from the 'Power' LED,

which is thus extinguished. If a more traditional red-green combination is preferred, a 1N4148 diode needs to be put in series with the green LED. The idea being to create as big a difference in forward voltage between the two LEDs as practicable. It is perhaps unfortunate that 'tri-colour' LEDs don't seem to be widely available in a common-anode configuration.

A fairly large capacitor at pin 6 of IC1b prevents false triggering when power is initially applied; the capacitance may be increased if required. Total current consumption is about 20mA. High load currents may require a heatsink for the 7805.

S G Mitchell,
Lurgan, Co. Armagh

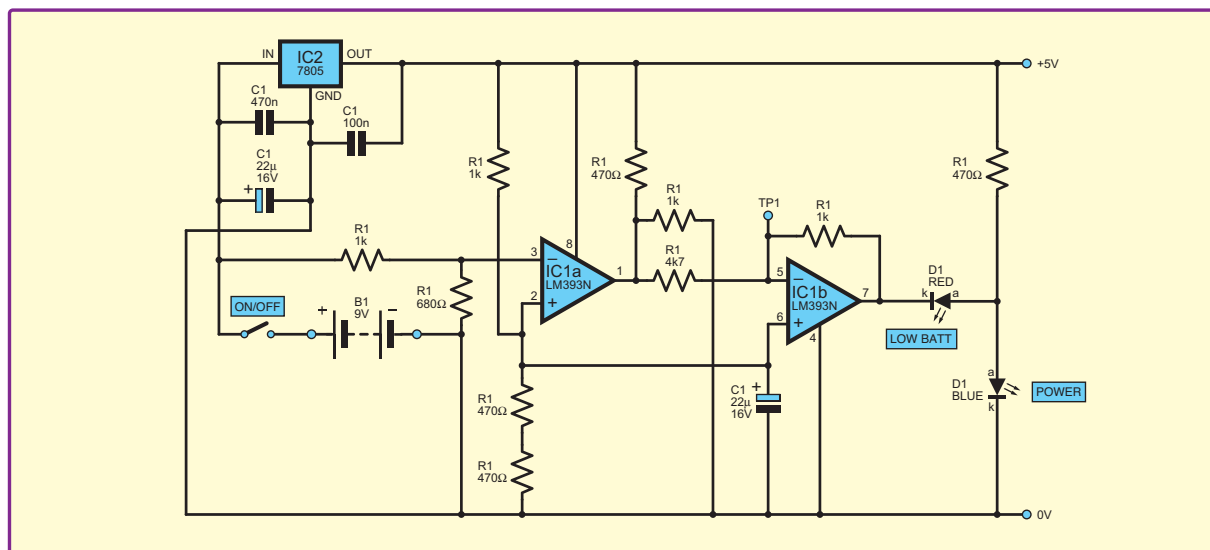


Fig.1. Circuit diagram for a low-battery indicator

EPE IS PLEASED TO BE ABLE TO OFFER YOU THESE

ELECTRONICS CD-ROMS




Flowcode 4 is one of the World's most advanced graphical programming languages for microcontrollers. The great advantage of Flowcode is that it allows those with little experience to create complex electronic systems in minutes.

Flowcode's graphical development interface allows engineers to construct a complete electronic system on-screen, develop a program based on standard flow charts, simulate the system and then produce hex code for PICmicro® microcontrollers, AVR microcontrollers, ARM microcontrollers, dsPIC and PIC24 microcontrollers.



Design

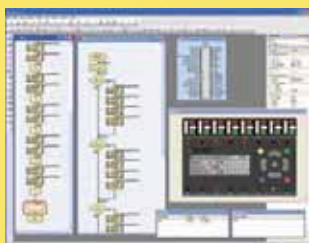Flowcode contains standard flow chart icons and electronic components that allow you to create a virtual electronic system on screen. Drag icons and components onto the screen to create a program, then click on them to set properties and actions.



Simulate

Once your system is designed you can use Flowcode to simulate it in action. Design your system on screen, test the system's functionality by clicking on switches or altering sensor or input values, and see how your program reacts to the changes in the electronic system.



Download

When you are happy with your design click one button to send the program directly to your microcontroller based target. Targets include a wide range of microcontroller programmers, upstream E-blocks boards, the Formula Flowcode robot, the MIAC industrial controller, or your own system based on ECIO technology.



FlowKit

The FlowKit can be connected to hardware systems to provide a real time debug facility where it is possible to step through the Flowcode program on the PC and step through the program in the hardware at the same time. The FlowKit can be connected to your own hardware to provide In-Circuit Debug to your finished designs.

PRICES

Prices for each of the CD-ROMs above are: (Order form on third page)

(UK and EU customers add VAT to 'plus VAT' prices)

Hobbyist/Student	£45.95	inc VAT
Professional (Schools/HE/FE/Industry)	£149	plus VAT
Professional and Flowkit bundle	£175	plus VAT

PICmicro TUTORIALS AND PROGRAMMING


HARDWARE

VERSION 3 PICmicro MCU development board

Suitable for use with the three software packages listed below.

This flexible development board allows students to learn both how to program PICmicro microcontrollers as well as program a range of 8, 18, 28 and 40-pin devices from the 12, 16 and 18 series PICmicro ranges. For experienced programmers all programming software is included in the PPP utility that comes with the development board. For those who want to learn, choose one or all of the packages below to use with the Development Board.

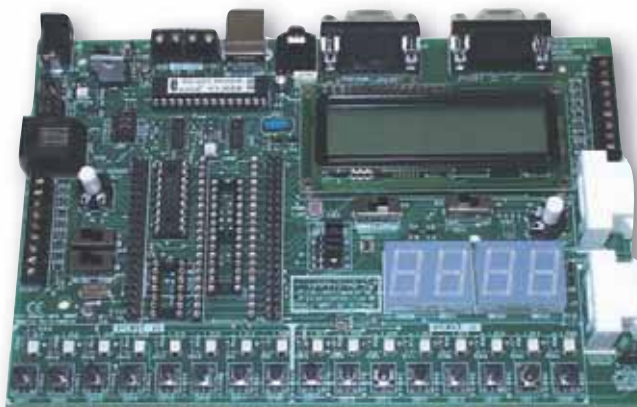- Makes it easier to develop PICmicro projects
- Supports low cost Flash-programmable PICmicro devices
- Fully featured integrated displays – 16 individual LEDs, quad 7-segment display and alphanumeric LCD display
- Supports PICmicro microcontrollers with A/D converters
- Fully protected expansion bus for project work
- USB programmable
- Can be powered by USB (no power supply required)



£161 including VAT and postage, supplied with USB cable and programming software

SOFTWARE

ASSEMBLY FOR PICmicro V3

(Formerly PICTutor)

Assembly for PICmicro microcontrollers V3.0 (previously known as PICTutor) by John Becker contains a complete course in programming the PIC16F84 PICmicro microcontroller from Arizona Microchip. It starts with fundamental concepts and extends up to complex programs including watchdog timers, interrupts and sleep modes.

The CD makes use of the latest simulation techniques which provide a superb tool for learning: the Virtual PICmicro microcontroller, this is a simulation tool that allows users to write and execute MPASM assembler code for the PIC16F84 microcontroller on-screen. Using this you can actually see what happens inside the PICmicro MCU as each instruction is executed, which enhances understanding.

- Comprehensive instruction through 45 tutorial sections
- Includes Vlab, a Virtual PICmicro microcontroller: a fully functioning simulator
- Tests, exercises and projects covering a wide range of PICmicro MCU applications
- Includes MPLAB assembler
- Visual representation of a PICmicro showing architecture and functions
- Expert system for code entry helps first time users
- Shows data flow and fetch execute cycle and has challenges (washing machine, lift, crossroads etc.)
- Imports MPASM files.



'C' FOR 16 Series PICmicro Version 4

The C for PICmicro microcontrollers CD-ROM is designed for students and professionals who need to learn how to program embedded microcontrollers in C. The CD-ROM contains a course as well as all the software tools needed to create Hex code for a wide range of PICmicro devices – including a full C compiler for a wide range of PICmicro devices.

Although the course focuses on the use of the PICmicro microcontrollers, this CD-ROM will provide a good grounding in C programming for any microcontroller.

- Complete course in C as well as C programming for PICmicro microcontrollers
- Highly interactive course
- Virtual C PICmicro improves understanding
- Includes a C compiler for a wide range of PICmicro devices
- Includes full Integrated Development Environment
- Includes MPLAB software
- Compatible with most PICmicro programmers
- Includes a compiler for all the PICmicro devices.



Minimum system requirements for these items: Pentium PC running, 2000, ME, XP; CD-ROM drive; 64MB RAM; 10MB hard disk space.
Flowcode will run on XP or later operating systems

FLOWCODE FOR PICmicro V4

Flowcode is a very high level language programming system based on flowcharts. Flowcode allows you to design and simulate complex systems in a matter of minutes. A powerful language that uses macros to facilitate the control of devices like 7-segment displays, motor controllers and LCDs. The use of macros allows you to control these devices without getting bogged down in understanding the programming. When used in conjunction with the Version 3 development board this provides a seamless solution that allows you to program chips in minutes.

- Requires no programming experience
- Allows complex PICmicro applications to be designed quickly
- Uses international standard flow chart symbols
- Full on-screen simulation allows debugging and speeds up the development process.
- Facilitates learning via a full suite of demonstration tutorials
- Produces ASM code for a range of 18, 28 and 40-pin devices
- 16-bit arithmetic strings and string manipulation
- Pulse width modulation
- I2C.

New features of Version 4 include panel creator, in circuit debug, virtual networks, C code customisation, floating point and new components. The Hobbyist/Student version is limited to 4K of code (8K on 18F devices)



PRICES

Prices for each of the CD-ROMs above are:
(Order form on next page)

(UK and EU customers add VAT to 'plus VAT' prices)

Hobbyist/Student	£45.95	inc VAT
Professional (Schools/HE/FE/Industry)	£99	plus VAT
Professional 10 user (Network Licence)	£350	plus VAT
Site Licence	£699	plus VAT
Flowcode Professional (Schools/HE/FE/Industry)	£149	plus VAT
Flowcode 10 user (Network Licence)	£399	plus VAT
Flowcode Site Licence	£799	plus VAT


CIRCUIT WIZARD

Circuit Wizard is a revolutionary new software system that combines circuit design, PCB design, simulation and CAD/CAM manufacture in one complete package.

Two versions are available, Standard or Professional.

By integrating the entire design process, Circuit Wizard provides you with all the tools necessary to produce an electronics project from start to finish – even including on-screen testing of the PCB prior to construction!

- * Circuit diagram design with component library (500 components Standard, 1500 components Professional)
- * Virtual instruments (4 Standard, 7 Professional)
- * On-screen animation
- * Interactive circuit diagram simulation
- * True analogue/digital simulation
- * Simulation of component destruction
- * PCB Layout
- * Interactive PCB layout simulation
- * Automatic PCB routing
- * Gerber export
- * Multi-level zoom (25% to 1000%)
- * Multiple undo and redo
- * Copy and paste to other software
- * Multiple document support

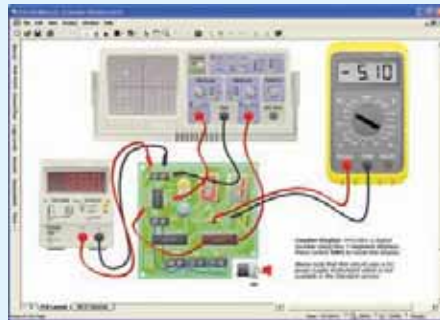


This is the software used in our *Teach-In 2011* series.
Standard **£61.25** inc. VAT
Professional **£91.90** inc. VAT

Minimum system requirements for these CD-ROMs: Pentium PC, CD-ROM drive, 32MB RAM, 10MB hard disk space. Windows 2000/ME/XP, mouse, sound card, web browser.

EPE PIC RESOURCES V2

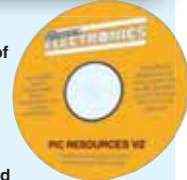Version 2 includes the EPE PIC Tutorial V2 series of Supplements (EPE April, May, June 2003)



The CD-ROM contains the following Tutorial-related software and texts:

- EPE PIC Tutorial V2 complete series of articles plus demonstration software, John Becker, April, May, June '03
- PIC Toolkit Mk3 (TK3 hardware construction details), John Becker, Oct '01
- PIC Toolkit TK3 for Windows (software details), John Becker, Nov '01

Plus 18 useful texts to help you get the most out of your PIC programming.

Price **£14.75** inc. VAT

ELECTRONIC COMPONENTS PHOTOS

A high quality selection of over 200 jpg images of electronic components.



This selection of high resolution photos can be used to enhance projects and presentations or to help with training and educational material. They are royalty free for use in commercial or personal printed projects, and can also be used royalty free in books, catalogues, magazine articles as well as worldwide web pages (subject to restrictions – see licence for full details).

Now contains Irfan View image software for Windows, with quick-start notes included.

Price **£19.95** inc. VAT

Please send me: CD-ROM ORDER FORM



- ☐ Assembly for PICmicro V3
- ☐ 'C' for 16 Series PICmicro V4
- ☐ Flowcode for PICmicro
- ☐ Flowcode for AVR
- ☐ Flowcode for ARM
- ☐ Flowcode for dsPIC & PIC24

Version required:

- ☐ Hobbyist/Student
- ☐ Professional
- ☐ Professional 10 user
- ☐ Professional + Flowkit
- ☐ Site licence

Note: The software on each version is the same, only the licence for use varies.

☐ PICmicro Development Board V3 (hardware)

- ☐ Circuit Wizard – Standard
- ☐ Circuit Wizard – Professional
- ☐ EPE PIC Resources V2
- ☐ Electronic Components Photos

Full name:

Address:

..... Post code: Tel. No:

Signature:

☐ I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £

☐ Please charge my Visa/Mastercard/Maestro: £

Valid From: Card expiry date:

Card No: Maestro Issue No.

Card Security Code (The last 3 digits on or just under the signature strip)

ORDERING ALL PRICES INCLUDE UK POSTAGE

Student/Single User/Standard/Hobbyist Version price includes postage to most countries in the world
EU residents outside the UK add £5 for airmail postage per order

Professional, Multiple User and Site License Versions – overseas readers add £5 to the basic price of each order for airmail postage (**do not add VAT** unless you live in an EU (European Union) country, then add VAT at 20% or provide your official VAT registration number).

Send your order to:
Direct Book Service
Wimborne Publishing Ltd
113 Lynwood Drive, Merley, Wimborne,
Dorset BH21 1UU

To order by phone ring
01202 880299. Fax: 01202 843233

Goods are normally sent within seven days

E-mail: orders@wimborne.co.uk

Online shop:

www.epemag.com

Net Work

Alan Winstanley



Quick off the mark

FOR centuries, human beings have sought easier ways of exchanging information with their fellow mortals. Fortunately, we have come a long way since we hid paper strips inside Chinese fortune cookies, which is why in the late 1990s one of the early PDAs – the delectable Handspring Visor Deluxe – included an infra-red port enabling owners to ‘beam’ their business cards wirelessly to other users. I’m not sure that the idea caught on, but in an era when mobile phones were still quite primitive (they too had IR ports), beaming a contact address from one PDA to another was a neat thing to do. Handspring’s Palm Graffiti handwriting recognition was well ahead of the game too.

My column last month covered QR (Quick Response) 2D barcodes, which are a small grid of pixels containing information such as a piece of text, an email address, a discount voucher code or a website URL. They can be scanned by a suitably-equipped mobile phone, webcam or 2D software and they are a slick way of ‘beaming’ snippets of data. More technical details can be found at the inventor’s website, www.denso-wave.com/qrcode/index-e.html.

As well as appearing in magazine advertisements, QR codes will increasingly be seen on billboards, posters, T-shirts and wristbands, and mobile phone users will be seen taking snapshots of QR codes and stopping in the street to goggle at the results. At least one *EPE* advertiser is already using them in their artwork – simply snap the barcode with a QR-capable mobile phone, and the phone’s web browser opens at the advertiser’s home page.

Windows PC users can have fun with QR codes by using the Quickmark software I highlighted last month (www.quickmark.com.tw – free for personal use, registration required). Quickmark can use your webcam to scan larger-sized printed codes, and to test it I used the *EPE* advertisement for PoScope, which includes a small QR code (P.17, July 2011 *EPE*). My webcam could not focus or resolve sufficiently to scan the tiny code, but I did print it onto a larger sheet and Quickmark responded impressively well to a fuzzy facsimile, opening my browser at the PoScope website instantly.

The software can also be dragged across your desktop like a ‘loupe’ to decode any QR codes that you see on-screen. You can try it for yourself by viewing the *EPE Chat Zone* forum where I ran a thread composed entirely of QR codes at <http://tinyurl.com/3cgcx33>.

Quickmark will generate bespoke QR graphics as a BMP, GIF, JPG or PNG (be sure to choose ‘QR code’ as the code type), for embedding in your own artwork. A phone number, URL, SMS, email address or small text message can all be encoded this way, and a code

containing a Google Maps link can be scanned directly onto a mobile, given customers personalised navigation instructions via their mobile browser.

Another resource to browse around is the QR applications specialists BeQrious (www.beqrious.com) where some forward-thinking applications of QR codes are explained. You can also build your own codes online (including a small logo at the centre) courtesy of their free online generator.

As I mentioned last month, a competing technology is Near Field Communications (NFC), which enables payments to be made or information to be transmitted wirelessly to some mobile phones. Details are at: www.nfc-forum.org and you will undoubtedly see the NFC ‘N’ logo appearing in the High Street in a few years.

Keep taking the tablets

For surfing the web, emailing or using a webcam, a mobile phone has its limitations, especially for regular use at home, on holiday or in the office. Back in *Net Work* August 2008, I introduced the Asus Eee PC netbook, which heralded a new wave of shrunken laptops capable of running Linux or Windows. Netbooks are still popular because they are very compact, stylish and unthreatening to use, and they boast a conventional-style QWERTY keyboard. Some have a built-in webcam enabling Skype to be used, but they don’t have an internal DVD drive.

If a netbook or laptop aren’t for you, then the market is awash with new ‘tablet’ computers. These sleek and seamless devices are entirely self-contained and offer everything needed to work and play online. Tablets invariably use a 7in. or 10in. touchscreen, which hard-bitten QWERTY typists may not find so productive, in which case a Bluetooth keyboard can be used – check availability.

The choice of operating system is a major headache because it controls the choice of applications (apps) that you might want to buy later down the line. Tablet and smartphone reviewers regularly comment about the variable quality of apps, or the lack of compatibility with their chosen OS. Undoubtedly, Apple offers the widest choice of quality apps by far.

Tablet fanatics have been busily devising new apps for their beloved tablets, and I commend to you the beautifully-worked USB Typewriter (<http://www.usbtypewriter.com/>) which hooks an iPad to an old mechanical typewriter, displaying the text onscreen as a sheet of ‘paper’. The Ion iCADE adds a retro Atari arcade game front-end to an iPad (<http://www.ionaudio.com/products/details/icafe>), and you can buy oscilloscope and test gear apps, music training apps and much more through iTunes, all using the iPad as a display screen.



Quickmark QR Reader can decode QR codes on-screen, using it as a ‘loupe’

While Apple offers the trend-setting iPad 2 running Apple's iOS, some familiar PC brands have joined in the fray with Windows 7 and Google Android-based devices. (Android is Google's own OS, using Linux at its core.) For example, the Acer Iconia W500 is a Windows 7 device with a 10.1in. screen costing about £435 (\$700); the similar, but cheaper Acer A500 runs Android instead.

Meantime, Research in Motion – best known for the Blackberry smartphone – has launched its new Playbook tablet, which claims a key advantage over the iPad: it runs Flash natively, which allows multimedia and animated websites to be displayed, while Apple users need a mobile browser such as Skyfire to view Flash files. Unfortunately, the Playbook won't currently work with Blackberry's own email service without using some very messy workarounds.

Elsewhere, Motorola's interesting Xoom is a new 10.1in. HD tablet also running Android Honeycomb. The



HP's Touchpad tablet is part of the new wave of tablet devices and it runs under WebOS. A Bluetooth QWERTY keyboard is available

Xoom offers an HDMI port, a Bluetooth QWERTY keyboard and speaker dock as extras. See www.motorola.com/XOOM for more details. Samsung offers the Galaxy Tab 10, a 10.1in. Android tablet with Flash support and full HD playback that claims to be the lightest and thinnest large screen tablet available (www.samsung.com/GalaxyTab).

As if Windows 7, Apple iOS, Android and Blackberry operating systems aren't enough, HP has arrived on the tablet scene with its WebOS-powered HP Touchpad (www.palm.com/touchpad). It was Handspring, you might recall, which used the Palm OS on the Visor Deluxe PDA that I mentioned right at the beginning. Handspring was absorbed into Palm and in turn, HP purchased Palm in 2010. Happily, the Palm OS has evolved into the mobile WebOS used in the Touchpad. The multi-tasking HP Touchpad handles Flash files and the 9.7in. 32GB version should be available by the time you read this. Prices from £399 to £479.

Chrome-plated

In recent weeks, I have been plagued by computer updates slowing down my computer boot-up times, partly thanks to a string of Adobe Reader and Adobe Flash emergency updates. Sometimes it seemed like Windows constantly needed patching too. Imagine a netbook-style device with no application software to worry about at all! The Google OS-based Chromebook (www.google.co.uk/chromebook) is designed for always-on web usage, and it uses Wi-Fi (or optionally 3G) to connect directly to the web within eight seconds, it is claimed. The online apps are hosted in the cloud, not on the local hard drive, and they are updated automatically without user intervention.

Chromebook users simply connect to the net to access their email and documents, and they don't have to worry about constantly patching their computer. Any product updates and fixes are downloaded and applied silently. The Chromebook 'dumb terminal' approach may be a good idea in theory, but early reviews are very mixed indeed, and it is unclear how practical the Chromebook will turn out to be, due to its complete dependence on the net. A 12.1in. Chromebook from Samsung has appeared, and Acer will be next to launch its own Chromebook.

Tablets and Chromebooks promise much for the Internet user, but, exciting as they are, one gains a dizzy feeling of a technological *déjà-vu* about the emerging market. The tablet form-factor is now here to stay, but at present, I have a tangible sense of disappointment



The Google Chromebook is an always-on web device that relies on finding an Internet connection

caused by the reportedly lacklustre performance of many tablets, or missing core features that have been criticised by reviewers across the board. There are practical shortcomings in this segment of the market, and a very close scrutiny of spec. sheets and user reviews is necessary before purchasing.

Next month, I'll look at another challenge to tablets – e-readers, wafer-thin displays that let you download e-books from the web and read them on the go. In the meantime, you can email me at: alan@epemag.demon.co.uk or write to the editor for possible inclusion in *Readout* at: editorial@wimborne.co.uk.



Laser

Why tolerate when you can automate?



X10 Home Automation



KAT5 AV transmission and IR control system



Barix Ethernet based MP3, communications and control systems



C-Bus Shop
C-Bus and C-Bus Wireless

www.cb-us-shop.com

www.laser.com

Integrators, Installers, Trade and Retail customers welcome

Laser Business Systems Ltd
Tel: +44 (0) 20 8441 9788
Fax: +44 (0) 20 8449 0430
Email: info@laser.com
16 Garthland Drive, EN5 3BB

NEW

Electronics Teach-In 3

FREE
CD-ROM

The three sections of this book cover a very wide range of subjects that will interest everyone involved in electronics, from hobbyists and students to professionals. The first 80-odd pages of Teach-In 3 are dedicated to *Circuit Surgery*, the regular *EPE* clinic dealing with readers' queries on various circuit design and application problems – everything from voltage regulation to using SPICE circuit simulation software.

The second section – *Practically Speaking* – covers the practical aspects of electronics construction. Again, a whole range of subjects, from soldering to avoiding problems with static electricity and identifying components, are covered.

Finally, our collection of *Ingenuity Unlimited* circuits provides over 40 different circuit designs submitted by the readers of *EPE*.

The free cover-mounted CD-ROM is the complete *Electronics Teach-In 1* book, which provides a broad-based introduction to electronics in PDF form, plus interactive quizzes to test your knowledge, TINA circuit simulation software (a limited version – plus a specially written TINA Tutorial), together with simulations of the circuits in the Teach-In 1 series, plus Flowcode (a limited version) a high level programming system for PIC microcontrollers based on flowcharts.

The Teach-In 1 series covers everything from Electric Current through to Microprocessors and Microcontrollers and each part includes demonstration circuits to build on breadboards or to simulate on your PC. There is also a MW/LW Radio project in the series.

The contents of the book and Free CD-ROM have been reprinted from past issues of *EPE*.

160 pages+CD-ROM Order code ET3 £8.50

ROBOTICS

INTRODUCING ROBOTICS WITH LEGO MINDSTORMS Robert Penfold

Shows the reader how to build a variety of increasingly sophisticated computer controlled robots using the brilliant Lego Mindstorms Robotic Invention System (RIS). Initially covers fundamental building techniques and mechanics needed to construct strong and efficient robots using the various "click-together" components supplied in the basic RIS kit. Then explains in simple terms how the "brain" of the robot may be programmed on screen using a PC and "zapped" to the robot over an infra-red link. Also, shows how a more sophisticated Windows programming language such as Visual BASIC may be used to control the robots.

Detailed building and programming instructions provided, including numerous step-by-step photographs.

288 pages - large format Order code BP901 £14.99

MORE ADVANCED ROBOTICS WITH LEGO MINDSTORMS – Robert Penfold

Shows the reader how to extend the capabilities of the brilliant Lego Mindstorms Robotic Invention System (RIS) by using Lego's own accessories and some simple home constructed units. You will be able to build robots that can provide you with 'waiter service' when you clap your hands, perform tricks, 'see' and avoid objects by using 'bats radar', or accurately follow a line marked on the floor. Learn to use additional types of sensors including rotation, light, temperature, sound and ultrasonic and also explore the possibilities provided by using an additional (third) motor. For the less experienced, RCX code programs accompany most of the featured robots. However, the more adventurous reader is also shown how to write programs using Microsoft's VisualBASIC running with the ActiveX control (Spirit, OCX) that is provided with the RIS kit.

Detailed building instructions are provided for the featured robots, including numerous step-by-step photographs. The designs include rover vehicles, a virtual pet, a robot arm, an 'intelligent' sweet dispenser and a colour conscious robot that will try to grab objects of a specific colour.

198 pages Order code BP902 £14.99

ANDROIDS, ROBOTS AND ANIMATRONS Second Edition – John Iovine

Build your own working robot or android using both off-the-shelf and workshop constructed materials and devices. Computer control gives these robots and androids two types of artificial intelligence (an expert system and a neural network). A lifelike android hand can be built and programmed to function doing repetitive tasks. A fully animated robot or android can also be built and programmed to perform a wide variety of functions.

The contents include an Overview of State-of-the-Art Robots; Robotic Locomotion; Motors and Power Controllers; All Types of Sensors; Tilt; Bump; Road and Wall Detection; Light; Speech and Sound Recognition; Robotic Intelligence (Expert Type) Using a Single-Board Computer Programmed in BASIC; Robotic Intelligence (Neutral Type) Using Simple Neural Networks (Insect Intelligence); Making a Lifelike Android Hand; A Computer-Controlled Robotic Insect Programmed in BASIC; Telepresence Robots With Actual Arcade and Virtual Reality Applications; A Computer-Controlled Robotic Arm; Animated Robots and Androids; Real-World Robotic Applications.

224 pages Order code MGH1 £16.99

DIRECT BOOK SERVICE

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the last book page.

FOR A FURTHER SELECTION OF BOOKS SEE THE NEXT TWO ISSUES OF *EPE*

All prices include UK postage

RADIO

BASIC RADIO PRINCIPLES AND TECHNOLOGY Ian Poole

Radio technology is becoming increasingly important in today's high technology society. There are the traditional uses of radio which include broadcasting and point to point radio as well as the new technologies of satellites and cellular phones. All of these developments mean there is a growing need for radio engineers at all levels.

Assuming a basic knowledge of electronics, this book provides an easy to understand grounding in the topic.

Chapters in the book: Radio Today, Yesterday, and Tomorrow; Radio Waves and Propagation; Capacitors, Inductors, and Filters; Modulation; Receivers; Transmitters; Antenna Systems; Broadcasting; Satellites; Personal Communications; Appendix – Basic Calculations.

263 pages Order code NE30 £28.99

PROJECTS FOR RADIO AMATEURS AND S.W.L.S. R. A. Penfold

This book describes a number of electronic circuits, most of which are quite simple, which can be used to enhance the performance of most short wave radio systems.

The circuits covered include: An aerial tuning unit; A simple active aerial; An add-on b.f.o. for portable sets;

A wavetrapp to combat signals on spurious responses; An audio notch filter; A parametric equaliser; C.W. and S.S.B. audio filters; Simple noise limiters; A speech processor; A volume expander.

Other useful circuits include a crystal oscillator, and RTTY/C.W. tone decoder, and a RTTY serial to parallel converter. A full range of interesting and useful circuits for short wave enthusiasts.

92 pages Order code BP304 £4.45

AN INTRODUCTION TO AMATEUR RADIO I. D. Poole

Amateur radio is a unique and fascinating hobby which has attracted thousands of people since it began at the turn of the last century. This book gives the newcomer a comprehensive and easy to understand guide through the subject so that the reader can gain the most from the hobby. It then remains an essential reference volume to be used time and again. Topics covered include the basic aspects of the hobby, such as operating procedures, jargon and setting up a station. Technical topics covered include propagation, receivers, transmitters and aerials etc.

150 pages Order code BP257 £5.49

COMPUTERS AND COMPUTING

ELECTRONICS TEACH-IN 2 CD-ROM USING PIC MICROCONTROLLERS A PRACTICAL INTRODUCTION

This *Teach-In* series of articles was originally published in *EPE* in 2008 and, following demand from readers, has now been collected together in the *Electronics Teach-In 2* CD-ROM.

The series is aimed at those using PIC microcontrollers for the first time. Each part of the series includes breadboard layouts to aid understanding and a simple programmer project is provided.

Also included are 29 *PIC N' Mix* articles, also republished from *EPE*. These provide a host of practical programming and interfacing information, mainly for those that have already got to grips with using PIC microcontrollers.

An extra four part beginners guide to using the C programming language for PIC microcontrollers is also included.

The CD-ROM also contains all of the software for the *Teach-In 2* series and *PIC N' Mix* articles, plus a range of items from Microchip – the manufacturers of the PIC microcontrollers. The material has been compiled by Wimborne Publishing Ltd. with the assistance of Microchip Technology Inc.

The Microchip items are: MPLAB Integrated Development Environment V8.20; Microchip Advance Parts Selector V2.32; Treelink; Motor Control Solutions; 16-bit Embedded Solutions; 16-bit Tool Solutions; Human Interface Solutions; 8-bit PIC Microcontrollers; PIC24 Microcontrollers; PIC32 Microcontroller Family with USB On-The-Go; dsPIC Digital Signal Controllers.

CD-ROM Order code ET12 CD-ROM £9.50

CD-ROM

BUILD YOUR OWN PC – Fourth Edition Morris Rosenthal

More and more people are building their own PCs. They get more value for their money, they create exactly the machine they want, and the work is highly satisfying and actually fun. That is, if they have a unique beginner's guide like this one, which visually demonstrates how to construct a computer from start to finish.

Through 150 crisp photographs and clear but minimal text, readers will confidently absorb the concepts of computer building. The extra-big format makes it easy to see what's going on in the pictures. The author goes 'under the hood' and shows step-by-step how to create a Pentium 4 computer or an Athlon 64 or Athlon 64FX, covering: What first-time builders need to know; How to select and purchase parts; How to assemble the PC; How to install Windows XP. The few existing books on this subject, although outdated, are in steady demand. This one delivers the expertise and new technology that fledgling computer builders are looking for.

224 pages - large format Order code MGH2 £16.99

PROGRAMMING 16-BIT PIC MICROCONTROLLERS IN C – LEARNING TO FLY THE PIC24 Lucio Di Jasio (Application Segments Manager, Microchip, USA)

A Microchip insider tells all. Focuses on examples and exercises that show how to solve common, real-world design problems quickly. Includes handy checklists to help readers perform the most common programming and debugging tasks. FREE CD-ROM includes source code in C, the Microchip C30 compiler, and MPLAB SIM software, so that readers gain practical, hands-on programming experience.

Until recently, PICs didn't have the speed and memory necessary for use in designs such as video- and audio-enabled devices. All that changed with the introduction of the 16-bit PIC family, the PIC24. This new guide teaches readers everything they need to know about the architecture of these chips, how to program them, how to test them and how to debug them. Lucio's common-sense, practical, hands-on approach starts out with basic functions and guides the reader step-by-step through even the most sophisticated programming scenarios.

Experienced PIC users and newcomers alike will benefit from the text's many thorough examples, which demonstrate how to nimbly side-step common obstacles and take full advantage of all the 16-bit features.

496 pages +CD-ROM Order code NE45 £38.00



NEW FULL COLOUR COMPUTING BOOKS

WINDOWS 7 – TWEAKS, TIPS AND TRICKS Andrew Edney

This book will guide you through many of the exciting new features of Windows 7. Microsoft's latest and greatest operating system. It will provide you with useful hints, tips and warnings about possible difficulties and pitfalls. This book should enable you to get much more out of Windows 7 and, hopefully, discover a few things that you may not have realised were there.

Among the topics covered are: A brief overview of the various versions of Windows 7. How to install and use Upgrade Advisor, which checks to see if your computer meets the minimum requirements to run Windows 7 and that your software and drivers are supported by Windows 7. How to use Windows Easy Transfer to migrate your data and settings from your Vista or XP machine to your new Windows 7 computer. Exploring Windows 7 so that you will become familiar with many of its new features and then see how they contrast with those of earlier versions of Windows. How to connect to a network and create and use Home Groups to easily share your pictures, videos, documents, etc., with the minimum of hassle. Why Windows Live Essentials is so useful and how to download and install it. A brief introduction to Windows Media Center. The use of Action Center, which reports security and maintenance incidents. Windows Memory Diagnostic to detect the fairly common problem of faulty memory and Troubleshooting tools.

120 pages **Order code BP708** £8.49

HOW TO BUILD A COMPUTER MADE EASY R.A. Penfold

Building your own computer is a much easier than most people realise and can probably be undertaken by anyone who is reasonably practical. However, some knowledge and experience of using a PC would be beneficial. This book will guide you through the entire process. It is written in a simple and straightforward way with the explanations clearly illustrated with numerous colour photographs.

The book is divided into three sections: *Overview and preparation* – Covers understanding the fundamentals and choosing the most suitable component parts for your computer, together with a review of the basic assembly. *Assembly* – Explains in detail how to fit the component parts into their correct positions in the computer's casing, then how to connect these parts together by plugging the cables into the appropriate sockets. No soldering should be required and the only tools that you are likely to need are screwdrivers, small spanners and a pair of pliers.

BIOS and operating system – This final section details the setting up of the BIOS and the installation of the Windows operating system, which should then enable all the parts of your computer to work together correctly. You will then be ready to install your files and any application software you may require.

The great advantage of building your own computer is that you can 'tailor' it exactly to your own requirements. Also, you will learn a tremendous amount about the structure and internal workings of a PC, which will prove to be invaluable should problems ever arise.

120 pages **Order code BP707** £8.49

AN INTRODUCTION TO eBay FOR THE OLDER GENERATION Cherry Nixon

eBay is an online auction site that enables you to buy and sell practically anything from the comfort of your own home. eBay offers easy access to the global market at an amazingly low cost and will enable you to turn your clutter into cash.

This book is an introduction to eBay.co.uk and has been specifically written for the over 50s who have little knowledge of computing. The book will, of course, also apply equally to all other age groups. The book contains ideas for getting organised for long term safe and successful trading. You will learn how to search out and buy every conceivable type of thing. The book also shows you how to create auctions and add perfect pictures. There is advice on how to avoid the pitfalls that can befall the inexperienced.

Cherry Nixon is probably the most experienced teacher of eBay trading in the UK and from her vast experience has developed a particular understanding of the issues and difficulties normally encountered by individuals.

So, if you are new to computers and the internet and think of a mouse as a rodent, then this is the book for you!

120 pages **Order code BP709** £8.49

GETTING STARTED IN COMPUTING FOR THE OLDER GENERATION Jim Gatenby

You can learn to use a computer at any age and this book will help you achieve this. It has been especially written for the over 50s, using plain English and avoiding technical jargon wherever possible. It is lavishly illustrated in full colour.

Among the many practical and useful subjects that are covered in this book are: Choosing the best computing system for your needs. Understanding the main hardware components of your computer. Getting your computer up and running in your home. Setting up peripheral devices like printers and routers. Connecting to the internet using wireless broadband in a home with one or more computers. Getting familiar with Windows Vista and XP the software used for operating and maintaining your computer. Learning about Windows built-in programs such as Windows Media Player, Paint and Photo Gallery.

Plus, using the Ease of Access Center to help if you have impaired eyesight, hearing or dexterity problems. Installing and using essential software such as Microsoft Office suite. Searching for the latest information on virtually any subject. Keeping in touch with friends and family using e-mail. Keeping your computer running efficiently and your valuable data files protected against malicious attack.

This book will help you to gain the basic knowledge needed to get the most out of your computer and, if you so wish, give you the confidence to even join a local computer class.

120 pages **Order code BP704** £8.49

THEORY AND REFERENCE

ELECTRONIC CIRCUITS – FUNDAMENTALS & APPLICATIONS Third Edition Mike Tooley

A comprehensive reference text and practical electronics handbook in one volume – at an affordable price!

New chapter on PIC microcontrollers – the most popular chip family for use in project work by hobbyists and in colleges and universities.

New companion website: spreadsheet design tools to simplify circuit calculations; circuit models and templates to enable virtual simulation; a bank of on-line questions for lecturers to set as assignments, and on-line self-test multiple choice questions for each chapter with automatic marking, to enable students to continually monitor their progress and understanding.

The book's content is matched to the latest pre-degree level courses, making this an invaluable reference for all study levels, and its broad coverage is combined with practical case studies, based in real-world engineering contexts throughout the text.

The unique combination of a comprehensive reference text, incorporating a primary focus on practical applications, ensures this text will prove a vital guide for students and also for industry-based engineers, who are either new to the field of electronics, or who wish to refresh their knowledge.

400 pages **Order code NE43** £25.99

BEBOP TO THE BOOLEAN BOOGIE Third Edition Clive (Max) Maxfield

This book gives the 'big picture' of digital electronics. This in-depth, highly readable, guide shows you how electronic devices work and how they're made. You'll discover how transistors operate, how printed circuit boards are fabricated, and what the innards of memory ICs look like. You'll also gain a working knowledge of Boolean Algebra and Karnaugh Maps, and understand what Reed-Muller logic is and how it's used. And there's much, MUCH more. The author's tongue-in-cheek humour makes it a delight to read, but this is a REAL technical book, extremely detailed and accurate.

Contents: Fundamental concepts; Analog versus digital; Conductors and insulators; Voltage, current, resistance, capacitance and inductance; Semiconductors; Primitive logic functions; Binary arithmetic; Boolean algebra; Karnaugh maps; State diagrams, tables and machines; Analog-to-digital and digital-to-analog; Integrated circuits (ICs); Memory

ICs; Programmable ICs; Application-specific integrated circuits (ASICs); Circuit boards (PWBs and DWBs); Hybrids; Multichip modules (MCMs); Alternative and future technologies.

500 pages **Order code BEB1** £32.99

BEBOP BYTES BACK (and the Bebobop Computer Simulator) CD-ROM Clive (Max) Maxfield and Alvin Brown

This follow-on to Bebob to the Boolean Boogie is a multimedia extravaganza of information about how computers work. It picks up where 'Bebop I' left off, guiding you through the fascinating world of computer design . . . and you'll have a few chuckles, if not belly laughs, along the way. In addition to over 200 megabytes of mega-cool multimedia, the CD-ROM contains a virtual microcomputer, simulating the motherboard and standard computer peripherals in an extremely realistic manner. In addition to a wealth of technical information, myriad nuggets of trivia, and hundreds of carefully drawn illustrations, the CD-ROM contains a set of lab experiments for the virtual microcomputer that let you recreate the experiences of early computer pioneers. If you're the slightest bit interested in the inner workings of computers, then don't dare to miss this!

Over 800 pages in Adobe Acrobat format
CD-ROM **Order code BEB2 CD-ROM** £21.95

FUNDAMENTAL ELECTRICAL AND ELECTRONIC PRINCIPLES Third Edition C. R. Robertson

Covers the essential principles that form the foundations for electrical and electronic engineering courses. The coverage of this new edition has been carefully brought in line with the core unit 'Electrical and Electronic Principles' of the 2007 BTEC National Engineering specification. This qualification from Edexcel attracts more than 10,000 students per year.

The book explains all theory in detail and backs it up with numerous worked examples. Students can test their

understanding with end of chapter assignment questions for which answers are provided. In this new edition, the layout has been improved and colour has been added. A free companion website with additional worked examples and chapters is also available.

368 pages **Order code NE47** £21.99

STARTING ELECTRONICS Third Edition Keith Brindley

A punchy practical introduction to self-build electronics. The ideal starting point for home experimenters, technicians and students who want to develop the real hands-on skills of electronics construction.

A highly practical introduction for hobbyists, students, and technicians. Keith Brindley introduces readers to the functions of the main component types, their uses, and the basic principles of building and designing electronic circuits.

Breadboard layouts make this very much a ready-to-run book for the experimenter, and the use of multimeter, but not oscilloscopes, and readily available, inexpensive components makes the practical work achievable in a home or school setting as well as a fully equipped lab.

Temporarily out of print



MUSIC, AUDIO AND VIDEO

MAKING MUSIC WITH YOUR COMPUTER

Stephen Bennett
Nearly everyone with musical aspirations also has a computer. This same computer can double as a high quality recording studio capable of producing professional recordings. This book tells you what software and hardware you will need to get the best results.

You'll learn about recording techniques, software and effects, mixing, mastering and CD production.

Suitable for PC and Mac users, the book is full of tips, "how to do" topics and illustrations. It's the perfect answer to the question "How do I use my computer to produce my own CD?"

92 pages

Order code PC120 £10.95



QUICK GUIDE TO MP3 AND DIGITAL MUSIC

Ian Waugh
MP3 files, the latest digital music format, have taken the music industry by storm. What are they? Where do you get them? How do you use them? Why have they thrown record companies into a panic? Will they make music easier to buy? And cheaper? Is this the future of music?

All these questions and more are answered in this concise and practical book which explains everything you need to know about MP3s in a simple and easy-to-understand manner. It explains:

How to play MP3s on your computer; How to use MP3s with handheld MP3 players; Where to find MP3s on the Web; How MP3s work; How to tune into Internet radio stations; How to create your own MP3s; How to record your own CDs from MP3 files; Other digital audio music formats.

Whether you want to stay bang up to date with the latest music or create your own MP3s and join the on-line digital music revolution, this book will show you how.

60 pages

Order code PC119 £7.45

DIGITAL AUDIO RECORDING

Ian Waugh
All modern music recordings use digital audio technology. Now everyone with a computer can produce CD-quality recordings and this book shows you how.

Written in a clear and straightforward style, it explains what digital audio recording is, how to use it, the equipment you need, what sort of software is available, and how to achieve professional results.

It explains:

- What computer system you need
- Sound and digital audio essentials
- What to look for in a sound card
- What effects to use
- The art of mixing
- Recording techniques
- How to use virtual instruments
- How to edit audio and create loops

Computer-based recording is the future of music and this book shows how you can join the revolution now.

60 pages

Order code PC121 £7.95

RADIO BYGONES

We also carry a selection of books aimed at readers of *EPE's* sister magazine on vintage radio *Radio Bygones*. These books include, the four volumes of our own *Wireless For the Warrior* by Louis Meulstee. These are a technical history of radio communication equipment in the British Army and clandestine equipment from pre-war through to the 1960s.

For details see the UK shop on our web site at www.epemag.com or contact us for a list of *Radio Bygones* books.

PROJECT BUILDING AND TESTING

ELECTRONIC PROJECT BUILDING FOR BEGINNERS

R. A. Penfold

This book is for complete beginners to electronic project building. It provides a complete introduction to the practical side of this fascinating hobby, including the following topics:

Component identification, and buying the right parts; resistor colour codes, capacitor value markings, etc; advice on buying the right tools for the job; soldering, making easy work of the hard wiring; construction methods, including stripboard, custom printed circuit boards, plain matrix boards, surface mount boards and wire-wrapping; finishing off, and adding panel labels; getting "problem" projects to work, including simple methods of fault-finding.

In fact everything you need to know in order to get started in this absorbing and creative hobby.

135 pages

Order code BP392 £5.99

BUILDING VALVE AMPLIFIERS

Morgan Jones

The practical guide to building, modifying, fault-finding and repairing valve amplifiers. A hands-on approach to valve electronics – classic and modern – with a minimum of theory. Planning, fault-finding, and testing are each illustrated by step-by-step examples.

A unique hands-on guide for anyone working with valve (tube in USA) audio equipment – as an electronics experimenter, audiophile or audio engineer.

Particular attention has been paid to answering questions commonly asked by newcomers to the world of the vacuum tube, whether audio enthusiasts tackling their first build, or more experienced amplifier designers seeking to learn the ropes of working with valves. The practical side of this book is reinforced by numerous clear illustrations throughout.

368 pages

Order code NE40 £29.00

PRACTICAL FIBRE-OPTIC PROJECTS

R. A. Penfold

While fibre-optic cables may have potential advantages over ordinary electric cables, for the electronics enthusiast it is probably their novelty value that makes them worthy of exploration. Fibre-optic cables provide an innovative interesting alternative to electric cables, but in most cases they also represent a practical approach to the problem. This book provides a number of tried and tested circuits for projects that utilize fibre-optic cables.

The projects include:- Simple audio links, F.M. audio link, P.W.M. audio links, Simple d.c. links, P.W.M. d.c. link, P.W.M. motor speed control, RS232C data links, MIDI link, Loop alarms, R.P.M. meter.

All the components used in these designs are readily available, none of them require the constructor to take out a second mortgage.

132 pages

Order code BP374 £5.45

GETTING THE MOST FROM YOUR MULTIMETER

R. A. Penfold

This book is primarily aimed at beginners and those of limited experience of electronics. Chapter 1 covers the basics of analogue and digital multimeters, discussing the relative merits and the limitations of the two types. In Chapter 2 various methods of component checking are described, including tests for transistors, thyristors, resistors, capacitors and diodes. Circuit testing is covered in Chapter 3, with subjects such as voltage, current and continuity checks being discussed.

In the main little or no previous knowledge or experience is assumed. Using these simple component and circuit testing techniques the reader should be able to confidently tackle servicing of most electronic projects.

102 pages

Order code BP239 £5.49

BOOK ORDERING DETAILS

All prices include UK postage. For postage to Europe (air) and the rest of the world (surface) please add £3 per book. Surface mail can take up to 10 weeks to some countries. For the rest of the world airmail add £4 per book. CD-ROM prices include VAT and/or postage to anywhere in the world. Send a PO, cheque, international money order (£ sterling only) made payable to **DIRECT BOOK SERVICE** or card details, Visa, Mastercard or Maestro to: **DIRECT BOOK SERVICE, WIMBORNE PUBLISHING LIMITED, 113 LYNWOOD DRIVE, MERLEY, WIMBORNE, DORSET BH21 1UU.**

Books are normally sent within seven days of receipt of order, but please allow 28 days for delivery – more for overseas orders. Please check price and availability (see latest issue of *Everyday Practical Electronics*) before ordering from old lists.

For a further selection of books see the next two issues of *EPE*.

Tel 01202 880299 Fax 01202 843233. E-mail: dbs@wimborne.co.uk

Order from our online shop at: www.epemag.com – go to the UK store

BOOK ORDER FORM

Full name:

Address:

.....

.....

..... Post code: Telephone No:

Signature:

☐ I enclose cheque/PO payable to DIRECT BOOK SERVICE for £

☐ Please charge my card £ Card expiry date:

Card Number Maestro Issue No.

Valid From Date Card Security Code (The last three digits on or just below the signature strip)

Please send book order codes:

.....

Please continue on separate sheet of paper if necessary

PCB SERVICE

Printed circuit boards for most recent *EPE* constructional projects are available from the *PCB Service*, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. Double-sided boards are **NOT plated through hole** and will require 'vias' and some components soldering to both sides. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to **The PCB Service, Everyday Practical Electronics, Wimborne Publishing Ltd., 113 Lynwood Drive, Merley, Wimborne, Dorset BH21 1UU.** Tel: 01202 880299; Fax 01202 843233; Email: orders@epemag.wimborne.co.uk. On-line Shop: www.epemag.com. Cheques should be crossed and made payable to *Everyday Practical Electronics* (Payment in £ sterling only).

NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail. Back numbers or photocopies of articles are available if required – see the Back Issues page for details. **WE DO NOT SUPPLY KITS OR COMPONENTS FOR OUR PROJECTS.**

Please check price and availability in the latest issue.
A large number of older boards are listed on, and can be ordered from, our website.

Boards can only be supplied on a payment with order basis.

PROJECT TITLE	ORDER CODE	COST
AUGUST '10		
★ PIC-Based Flexitimer (double-sided)	763	£12.91
DSP Musicolour – Remote Control Receiver	764	£5.93
★ UV Lightbox – Exposure Controller	765 } set	£9.77
– Display/Timer	766	
Ultra LD 200W Power Amplifier (double-sided)	767	£15.52
SEPTEMBER '10		
Ultra-LD 200W Power Amplifier – Power Supply	768	£8.37
Low-Voltage Adjustable Regulator	769	£6.81
Balanced/Unbalanced Converter	770	£7.68
Planet Jupiter Receiver (double-sided)	771	£15.00
OCTOBER '10		
Bridge Adaptor For Stereo Power Amps	770	£7.68
CDI Module For Small Motors	772	£6.63
★ LED Strobe and Tachometer – 1		
– Main Board	775 } pair	£8.37
– Switch Board	776	
NOVEMBER '10		
★ Railpower – Main Board	773 } pair	£14.83
– Display Board	774	
★ LED Strobe and Tachometer – 2		
– Photo-Interrupter	777 } pair	£7.15
– IR Reflect Amp	778	
★ USB Clock with LCD Readout – 1	779	£7.85
Balanced MIC Preamp for PCs and MP3 Players	780	£8.72
DECEMBER '10		
12V Speed Controller or 12V Lamp Dimmer	781	£6.99
★ Digital RF Level & Power Meter		
– Main Board	783 } set	£10.81
– Head-end Board	784	
– RF Attenuator Board	785	
JANUARY '11		
★ Multi-Purpose Car Scrolling Display		
– Main Board	786 } pair	£12.21
– Display Board	787	
USB-Sensing Mains Power Switch	788	£9.77
★ 433MHz UHF Remote Switch		
– Transmitter	789 } pair	£10.12
– Receiver	790	
FEBRUARY '11		
Time Delay Photoflash Trigger	791	£9.72
Tempmaster Mk.2	792	£8.59
MARCH '11		
★ GPS Synchronised Clock	793	£8.02
★ Digital Audio Millivoltmeter	794	£11.34
Theremin	795	£10.53
USB Printer Share Switch	796	£6.80
APRIL '11		
Multi-Message Voice Recorder	797	£7.53
PIR-Triggered Mains Switch	798	£8.00
★ Intelligent Remote-Controlled Dimmer	799	£6.97

PROJECT TITLE	ORDER CODE	COST
MAY '11		
★ 6-Digit GPS Clock	800	£10.69
Simple Voltage Switch For Car Sensors	801	£6.80
The μ Current (double-sided, surface mount)	802	£11.50
★ Digital Audio Oscillator (double-sided)	803	£11.83
JUNE '11		
230V AC 10A Full-Wave Motor Speed Controller	804	£8.91
Precision 10V DC Voltage Reference	805	£6.48
6-Digit GPS Clock Driver (Pt.2)	806	£6.80
Musicolour IRDA Accessory	807	£6.15
JULY '11		
Beam-Break Flash Trigger – IR Source	808 } pair	£8.10
– Detector	809	
Metal Locator	810	£7.13
Multi-Function Active Filter	812	£8.34
Active AM Loop Antenna and Amp		
– Antenna/Amp	813 } pair	£8.89
– Radio Loop (inc. Varicaps)	814	
AUGUST '11		
Input Attenuator for the Digital Audio Millivoltmeter	811	£6.32
★ SD Card Music & Speech Recorder/Player	815	£11.34
★ Deluxe 3-Chan. UHF Rolling Code Remote Control – Transmitter	816 } pair	£10.36
– Receiver	817	
SEPTEMBER '11		
★ Digital Megohm and Leakage Current Meter	818	£8.10
Auto-Dim for 6-Digit GPS Clock	819	£5.67




EPE SOFTWARE

★ All software programs for *EPE* Projects marked with a star, and others previously published can be downloaded free from the Library on our website, accessible via our home page at: www.epemag.com

PCB MASTERS

PCB masters for boards published from the March '06 issue onwards can also be downloaded from our website (www.epemag.com); go to the 'Library' section.

EPE PRINTED CIRCUIT BOARD SERVICE

Order Code	Project	Quantity	Price
Name			
Address			
Tel. No.			
I enclose payment of £ (cheque/PO in £ sterling only) to:			
Everyday Practical Electronics			
  			
Card No.			
Valid From		Expiry Date	
Card Security No.		Maestro Issue No.	
Signature			

Note: You can also order PCBs by phone, Fax or Email or via the Shop on our website on a secure server:

<http://www.epemag.com>

CLASSIFIED

ADVERTISEMENTS

Everyday Practical Electronics reaches more UK readers than any other UK monthly hobby electronics magazine, our sales figures prove it. We have been the leading monthly magazine in this market for the last twenty-five years.

If you want your advertisements to be seen by the largest readership at the most economical price our classified page offers excellent value. The rate for semi-display space is £10 (+VAT) per centimetre high, with a minimum height of 2.5cm. All semi-display adverts have a width of 5.5cm. The prepaid rate for classified adverts is 40p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. **VAT must be added.** Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, 113 Lynwood Drive, Merley, Wimborne, Dorset, BH21 1UU. Phone: 01202 880299. Fax: 01202 843233. Email: epeads@wimborne.co.uk. For rates and information on display and classified advertising please contact our Advertisement Manager, Stewart Kearn as above.

**LOOKING FOR
AN AUDIO TRANSFORMER**
Visit Section 4C
www.partridgeelectronics.co.uk

BOWOOD ELECTRONICS LTD
Suppliers of Electronic Components
Place a secure order on our website or call our sales line
All major credit cards accepted
Web: www.bowood-electronics.co.uk
Unit 10, Boythorpe Business Park, Dock Walk, Chesterfield,
Derbyshire S40 2QR. Sales: 01246 200222
Send 60p stamp for catalogue

CANTERBURY WINDINGS
UK manufacturer of toroidal transformers
(10VA to 3kVA)
All transformers made to order. No design fees.
No minimum order.
www.canterburywindings.co.uk
01227 450810

**ADVERTISE HERE FOR
JUST £25 +VAT CALL
STEWART KEARN
ON 01202 880299
STEWART.KEARN@WIMBORNE.CO.UK**

BTEC ELECTRONICS TECHNICIAN TRAINING

**NATIONAL ELECTRONICS
VCE ADVANCED ICT
HNC AND HND ELECTRONICS
FOUNDATION DEGREES
NVQ ENGINEERING AND IT
DESIGN AND TECHNOLOGY**

LONDON ELECTRONICS COLLEGE
20 PENYWERN ROAD
EARLS COURT, LONDON SW5 9SU
TEL: (020) 7373 8721
www.lec.org.uk

Spinvent
Invent with the
Propeller 8-core
32-bit microcontroller
www.spinvent.co.uk
01603 611 216



Robot Bits
Robots, Arduino & more!
www.RobotBits.co.uk
0845 5 191 282

CPS Solar
Solar panels, solar cells, and many more alternative energy products for battery charging etc, please visit our website for further info or call
Tel: 0870 765 2334.
www.solarpanelsonline.co.uk

LCD Displays & Controllers from
£2.50
Serial, I2C, VT100,
Full Colour, PIC32,
Touch Screen
www.byvac.com

MISCELLANEOUS

KITS, TOOLS, COMPONENTS. S.A.E.
Catalogue. SIR-KIT ELECTRONICS, 52
Severn Road, Clacton, CO15 3RB, <http://sir-kit.webs.com>

VALVES AND ALLIED COMPONENTS IN STOCK. Phone for free list. Valves, books and magazines wanted. Geoff Davies (Radio), tel. 01788 574774.

ADVERTISERS INDEX

CRICKLEWOOD ELECTRONICS	67	PICO TECHNOLOGY	45
CCS INFO	67	QUASAR ELECTRONICS	2/3
DISPLAY ELECTRONICS	80	SHERWOOD ELECTRONICS	67
ESR ELECTRONIC COMPONENTS	6	SPIRATRONICS	30/31
JAYCAR ELECTRONICS	4/5	STEWART OF READING	Cover (iii)
JPG ELECTRONICS	80	TECHNOBOTS	67
L-TEK POSCOPE	21		
LABCENTER	Cover (iv)	ADVERTISEMENT OFFICES:	
LASER BUSINESS SYSTEMS	73	113 LYNWOOD DRIVE, MERLEY, WIMBORNE,	
MATRIX MULTIMEDIA	66	DORSET BH21 1UU	
MICROCHIP	Cover (ii)	PHONE: 01202 880299 FAX: 01202 843233	
MIKROELEKTRONIKA	61	EMAIL: epeads@wimborne.co.uk WEB: www.epemag.com	
PEAK ELECTRONIC DESIGN	Cover (iii)	For editorial address and phone numbers see page 7	

CLASSIFIED

ADVERTISEMENTS

Everyday Practical Electronics reaches more UK readers than any other UK monthly hobby electronics magazine, our sales figures prove it. We have been the leading monthly magazine in this market for the last twenty-five years.

If you want your advertisements to be seen by the largest readership at the most economical price our classified page offers excellent value. The rate for semi-display space is £10 (+VAT) per centimetre high, with a minimum height of 2.5cm. All semi-display adverts have a width of 5.5cm. The prepaid rate for classified adverts is 40p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. **VAT must be added.** Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, 113 Lynwood Drive, Merley, Wimborne, Dorset, BH21 1UU. Phone: 01202 880299. Fax: 01202 843233. Email: epeds@wimborne.co.uk. For rates and information on display and classified advertising please contact our Advertisement Manager, Stewart Kearn as above.

**LOOKING FOR
A MAINS TRANSFORMER**
Visit Section 16C
www.partridgeelectronics.co.uk

BOWOOD ELECTRONICS LTD
Suppliers of Electronic Components
Place a secure order on our website or call our sales line
All major credit cards accepted
Web: www.bowood-electronics.co.uk
Unit 10, Boythorpe Business Park, Dock Walk, Chesterfield,
Derbyshire S40 2QR. Sales: 01246 200222
Send 60p stamp for catalogue

MISCELLANEOUS
VALVES AND ALLIED COMPONENTS IN STOCK. Phone for free list. Valves, books and magazines wanted. Geoff Davies (Radio), tel. 01788 574774.

BTEC ELECTRONICS TECHNICIAN TRAINING

**NATIONAL ELECTRONICS
VCE ADVANCED ICT
HNC AND HND ELECTRONICS
FOUNDATION DEGREES
NVQ ENGINEERING AND IT
DESIGN AND TECHNOLOGY**

LONDON ELECTRONICS COLLEGE
20 PENYWERN ROAD
EARLS COURT, LONDON SW5 9SU
TEL: (020) 7373 8721
www.lec.org.uk

Spinvent
Invent with the
Propeller 8-core
32-bit microcontroller
www.spinvent.co.uk
01603 611 216



Robot Bits
Robots, Arduino & more!
www.RobotBits.co.uk
0845 5 191 282

CANTERBURY WINDINGS
UK manufacturer of toroidal transformers
(10VA to 3kVA)
All transformers made to order. No design fees.
No minimum order.
www.canterburywindings.co.uk
01227 450810

**ADVERTISE HERE
CALL
STEWART KEARN
ON 01202 880299**
STEWART.KEARN@WIMBORNE.CO.UK

If you would like to advertise on the Classified page then please call:
**Stewart Kearn on
01202 880299**
or email stewart.kearn@wimborne.co.uk

ADVERTISERS INDEX

CRICKLEWOOD ELECTRONICS	67	QUASAR ELECTRONICS	2/3
DISPLAY ELECTRONICS	80	SHERWOOD ELECTRONICS	67
ESR ELECTRONIC COMPONENTS	6	STEWART OF READING	Cover (iii)
JAYCAR ELECTRONICS	4/5	TECHNOBOTS	67
JPG ELECTRONICS	80		
L-TEK POSCOPE	17		
LABCENTER	Cover (iv)		
LASER BUSINESS SYSTEMS	67		
MATRIX MULTIMEDIA	73		
MICROCHIP	Cover (ii)		
MIKROELEKTRONIKA	55		
PEAK ELECTRONIC DESIGN	Cover (iii)		
PICO TECHNOLOGY	66		

ADVERTISEMENT OFFICES:

113 LYNWOOD DRIVE, MERLEY, WIMBORNE,
DORSET BH21 1UU

PHONE: 01202 880299 **FAX:** 01202 843233

EMAIL: epeds@wimborne.co.uk **WEB:** www.epemag.com

For editorial address and phone numbers see page 7

Next Month

Wideband Air-Fuel Mixture Display

Running efficiently and not wasting fuel makes great sense. This Wideband Oxygen Sensor Display can show your car's air-fuel ratio as you drive. It's designed to monitor a wideband oxygen sensor and its associated wideband controller, but could be used to monitor a narrowband oxygen sensor instead.

Open-USB-IO: a universal I/O solution


This powerful digital project lets you drive a host of digital and analogue I/O (input/outputs) via the USB interface on your laptop or desktop computer. Based on an Atmel Atmega32 microprocessor and not much else, it works on Windows, Linux and Macs.

A high-quality stereo DAC for superb sound from your DVD player – Part 2

Last month, we introduced our new high-quality stereo DAC and described the circuit. This month, we show you how to build the various modules and make the header cables.

Twin Engine SpeedMatch Indicator

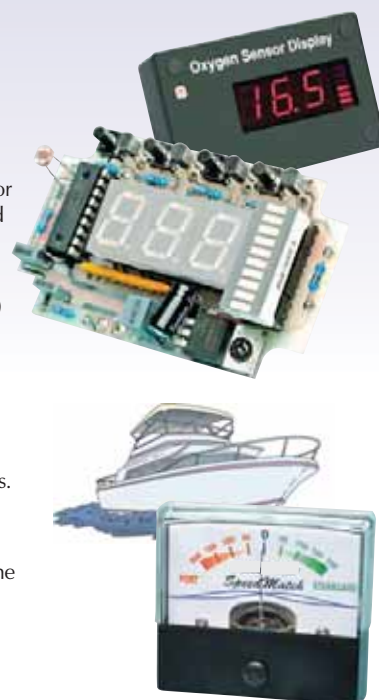Avoid unnecessary noise and vibration in twin-engine boats by using this Twin Engine SpeedMatch Indicator. It uses a meter that is centred when both motors are running at the same speed. When the motors are not matched in revs, the meter shows which motor is running faster and by how much.



OCTOBER '11 ISSUE ON SALE 8 SEPTEMBER

Content may be subject to change

Europe's Largest Surplus Store

20,000,000 Items on line NOW !
New items added daily

Established for over 25 years, UK company Display Electronics prides itself on offering a massive range of electronic and associated electro-mechanical equipment and parts to the Hobbyist, Educational and Industrial user. Many current and obsolete hard to get parts are available from our vast stocks, which include:

- ◆ 6,000,000 Semiconductors
- ◆ 5,000 Power Supplies
- ◆ 25,000 Electric Motors
- ◆ 10,000 Connectors
- ◆ 100,000 Relays & Contactors
- ◆ 2000 Rack Cabinets & Accessories
- ◆ 4000 Items of Test Equipment
- ◆ 5000 Hard Disk Drives

We Ship Worldwide

Surplus Wanted

www.distel.co.uk

Display Electronics
29 / 35 Osborne Road
Thornton Heath
Surrey UK CR7 8PD

Telephone
[44] 020 8653 3333
Fax **[44] 020 8653 8888**

Rechargeable Batteries With Solder Tags

NIMH

AA 2000mAh	£2.82
C 4Ah	£4.70
D 9Ah	£7.60
PP3 150mAh	£4.95


NICAD

AA 650mAh	£1.41
C 2.5Ah	£3.60
D 4Ah	£4.95

Instrument case with edge connector and screw terminals

Size 112mm x 52mm x 105mm tall

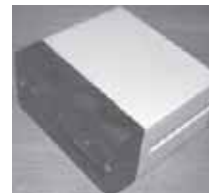This box consists of a cream base with a PCB slot, a cover plate to protect your circuit, a black lid with a 12 way edge connector and 12 screw terminals built in (8mm pitch) and 2 screws to hold the lid on. The cream bases have minor marks from dust and handling price £2.00 + VAT(=£2.35) for a sample or £44.00+VAT (=£51.70) for a box of 44.



866 battery pack originally intended to be used with an orbitel mobile telephone it contains 10 1.6Ah sub C batteries (42 x 22 dia. the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily £7.46 + VAT = **£8.77**



Please add £1.66 + VAT = £1.95 postage & packing per order

JPG Electronics
Shaws Row, Old Road, Chesterfield, S40 2RB.
Tel 01246 211202 Fax 01246 550959
www.JPGElectronics.com
Mastercard/Visa/Switch

Callers welcome 9.30 a.m. to 5.30 p.m. Monday to Saturday



Designed in the UK,
Made in the UK.

Tel. 01298 70012
www.peakelec.co.uk
sales@peakelec.co.uk

West Road House
West Road
Buxton
Derbyshire
SK17 6HF

PEAK[®]
electronic design ltd

Atlas DCA - Semiconductor Analyser with Carry Case!



Order Code
ATPK1



The famous Peak Atlas and even better value in this carry case!

Fitted with sturdy universal premium gold probes. Just connect any way round to identify the type of part, pinout and lots of parameters.

Supplied with battery, comprehensive user guide and padded hard carry case (choose either blue or black).

Supports bipolar transistors, darlingtons, MOSFETs, diodes, LEDs and more...

£42.50 + VAT

=£51 inc VAT. Limited Offer.

Please add £3 for UK P&P

Case available in black or blue.

www.stewart-of-reading.co.uk

Check out our website, 1,000's of items in stock.



HP8563E SPECTRUM ANALYSER
9KHZ - 26.5GHZ Synthesised..... £POA



HP33120A FUNCTION GENERATOR
100 MicroHZ - 15MHZ
Unused Boxed £595
Used, No Moulding, No Handle £395



MARCONI 2955 RADIO
COMMUNICATION TEST SET
ONLY £625
Also available Marconi 2955A & 2955B



ENI 3200L RF POWER AMPLIFIER
250KHZ-150MHZ 200W 55db

AGILENT E4402B Spectrum Analyser
100KHZ - 3GHZ with Option 1DN Tracking
Gen; 1 DR Narrow Res; A4H GPIB,
UKB.....£5800
HP 35670A FFT Dynamic Signal Analyser
2 Channel. Unused in original box.....£4000
AGILENT 83752B Synthesised Sweeper
0.01-20GHZ.....£6000
HP83711B Synthesised 1-20GHZ with
Opt IEL Attenuator.....£5000
AGILENT/HP E4431B Signal Generator
250KHZ-2GHZ Digital Modulation.....£2750
MARCONI 2024 Signal Generator 9KHZ-
2.4GHZ Opt 04.....£1250
MARCONI/IFR 2030 Signal Generator
10KHZ-1.35 GHz.....£995
MARCONI 2022E Synthesised AM/FM
Signal Generator 10KHZ-1.01GHZ.....£500
HP8566A Spectrum Analyser 100KHZ-
22GHZ.....£1950
HP8566A Spectrum Analyser 100KHZ-
1500MHZ.....£1250
AVCOM PSA-37D Spectrum Analyser
1MHZ-4.2GHZ.....£-
IFR 1200G Service Communication
Monitor.....£1500
HP6624A Power Supply 0-20V 0-2A
Twice, 0-7V 0-5A; 0-50V 0.8A
Special price.....350
AVO/MEGGER FT6/12 AC/DC
breakdown tester.....£-
MARCONI/IFR/AEROFLEX 2025 Signal
Gen 9KHZ-2.51GHZ Opt 04 High Stab
Opt 11 High Power etc As New.....£2500
SOLARTRON 1250 Frequency Response
Analyser 10uHZ-65KHZ.....£995
HP3324A Synthesised Function
Generator 21MHZ.....£500
HP41800A Active Probe 5HZ-500MHZ
.....£750
ANRITSU MS2601A Spectrum Analyser
10KHZ-2.2GHZ 50ohm.....£750



AGILENT E4421B 250KHZ-3GHZ
Signal Generator £2500

HP53131A Universal Counter Opt 001
Unused Boxed 3GHZ.....£850
Unused Boxed 225MHZ.....£595
Used 225MHZ.....£495
HP8569B Spectrum Analyser 0.01-
22GHZ.....£1000
HP54616C Oscilloscope Dual Trace
500MHZ 2GS/S Colour.....£1250
QUART LOCK 10A-R Rubidium
Frequency Standard.....£1000
PENDULUM CNT90 Timer/Counter
/Analyser 200GHZ.....£1950
ADVANTEST R3465 Spectrum
Analyser 9KHZ-5GHZ.....£-
HP Programmable Attenuators £300
each
33320H DC-18GHZ 11db
33321G DC-18GHZ 70db
Many others available
AGILENT E3610A Power Supply 0-8V
0-3A/0-15V 0-2A Unused
AGILENT E3611A Power Supply 0-20V
0-1.5A/0-35V 0-0.85V Unused
CIRRUS CRL254 Sound Level Meter
with Calibrator.....£95
CEL328 Digital Sound Level Meter with
CEL294/2 Acoustical Calibrator.....
CEL 269 Digital Sound Level Meter with
CEL282 Acoustical Calibrator

STEWART of READING

17A King Street, Mortimer,
Near Reading RG7 3RS
Telephone: 0118 933 1111
Fax: 0118 933 2375
9am - 5pm Monday - Friday

Used Equipment - GUARANTEED
Prices plus Carriage and VAT

Please check availability before
ordering or CALLING IN



MARCONI 2945 RADIO
COMMUNICATION TEST

SET with...

Opt 01 - 600 ohm Matching Unit
Opt 03 - High Stability CCKO
Opt 06 - Memory Card Drive with Real
Time Clock Opt 08 - SSB Demodulator
Opt 21 Demodulation Filters
Opt 22 POC/SAG Decode
Only £3,000



HP 8569B
Spectrum Analyser 0.01-22GHZ
£995



HP6269B Power Supply
0-40V 0-50A £400

AMPLIFIER RESEARCH
POWER AMPLIFIER 1000LAM8 £POA



PRE-PRODUCTION CHECK

Board Edge Defined - **CHECK**

All Components Placed - **CHECK**

All Connections Routed - **CHECK**

Power Planes Generated - **CHECK**

No Design Rule Violations - **CHECK**

PROTEUS 7

Design with Confidence:

The latest version of the Proteus PCB Design Software provides a multi-stage Pre-Production Check which will detect and prevent a variety of common mistakes prior to your boards being sent for manufacture.

PROTEUS DESIGN SUITE Features:

- Hardware Accelerated Performance.
- Unique Thru-View™ Board Transparency.
- Over 35k Schematic & PCB library parts.
- Integrated Shape Based Auto-router.
- Flexible Design Rule Management.
- Polygonal and Split Power Plane Support.
- Board Autoplacement & Gateswap Optimiser.
- Direct CAD/CAM, ODB++, IDF & PDF Output.
- Integrated 3D Viewer with 3DS and DXF export.
- Mixed Mode SPICE Simulation Engine.
- Co-Simulation of PIC, AVR, 8051 and ARM7.
- Direct Technical Support at no additional cost.

All levels of the **Proteus Design Suite** include a world class, fully integrated shape-based autorouter at no additional cost - prices start from just £150 exc. VAT & delivery

labcenter  www.labcenter.com
Electronics

Labcenter Electronics Ltd. 53-55 Main Street, Grassington, North Yorks. BD23 5AA.
Registered in England 4692454 Tel: +44 (0)1756 753440, Email: info@labcenter.com

Visit our website or
phone 01756 753440
for more details